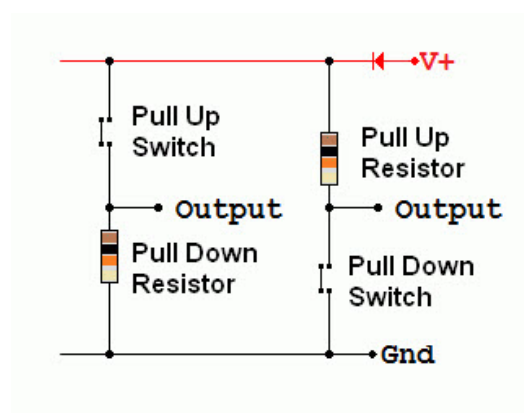


# Difference Between Pull-up and Pull-down Resistors and Practical Examples

• ELECTRONICS 4 COMMENTS


A microcontroller in any **embedded system** utilizes I/O signals to communicate with the external devices. The simplest form of I/O is usually stated to as GPIO(General Purpose Input/Output). When the GPIO voltage level is low, then it is in high or high impedance state, then the pull up and pull-down resistors are used to ensure GPIO which is always in a valid state. Usually, the GPIO is arranged on a **microcontroller** as I/O. As an input, the microcontroller pin can take one of these states: high, low and floating or high impedance. When an i/p is driven above the i/p is high threshold, it is a logic one. When the I/P is driven below the I/P, which is low threshold, the input is logic 0. When in a floating or high impedance state, the I/P level is not constantly high nor low. To ensure the values of an I/P is always in a known state, pull up and pull-down resistors are used. The main function of pull-up and pull-down resistors is that the pull up resistor pulls the signal to high state unless it is driven low; and, a pull-down resistor pulls the signal to low state unless it is driven high.




Pull-up and Pull-down resistors
 
## What is a Resistor?

The Resistor is a most commonly used component in many **electronic circuits** and electronic devices. The main function of the resistor is, it restricts the flow of current to other components. The resistor works on the principle of ohms law which states that dissipation due to the resistance. The unit of resistance is ohm and the symbol of ohm shows resistance in a circuit. There are **numerous resistor types** are available in the market with different sizes and rating. They are Metal film resistors, thin film resistors and thick film resistors, wire wound resistors, network resistors, surface resistors, mount resistors, variable resistors and special resistors.




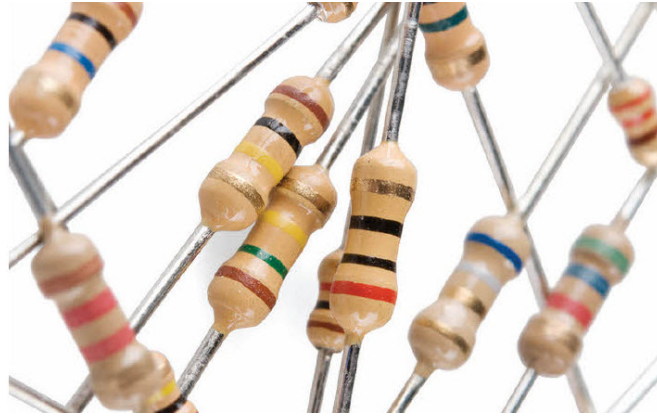*Resistor*

Consider a two resistors in series connection, then the same current  $I$  flows through the two resistors and the direction of the current is indicated by an arrow. When the two resistors are in parallel connection, then the potential drop  $V$  across the two resistors is the same.
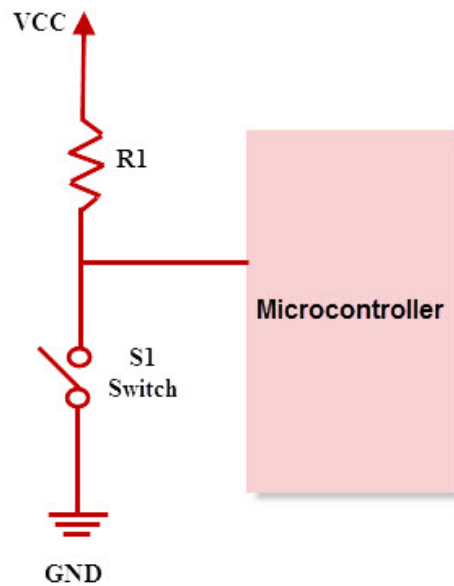
## Pull-up Resistors

Pull-up resistors are simple fixed value resistors, that are connected between the voltage supply and the particular pin. These resistors are used in **digital logic circuits** to ensure a logic level at a pin, which results in state wherein the input/output voltage is nonexistence driving signal. Digital logic circuits consist of three states like high, low and floating or high impedance. When the pin is not pulled to a lower or a high logic level, then the high impedance state occurs. These resistors are used to solve the problem for the microcontroller by pulling the value to a high state, as seen in the figure. When the switch is open, the microcontrollers input would be floating and brought down only when the switch is closed. A typical pull-up resistor value is 4.7kilo Ohms, but can change depending on the application.



Pull-up Resistor


### NAND Gate Circuit using Pull Up Resistor

In this project, the pull-up resistor is wired up to a logic chip circuit. These circuits are the best circuits to test pull up resistors. Logic chip circuits work based on low or high signals. In this project, the NAND gate is taken as an example of logic chip. The main function of the NAND gate is, when any one of the NAND gate input is low, then the output signal is high. In the same way, when the inputs of the NAND gate are high, then the output signal is low.

The required components for AND gate circuit using pull-down resistors are NAND gate chip (4011), 10Kilo Ohm resistors-2, Pushbuttons-2, 330ohm resistor and LED.

- Each NAND gate consists of two I/P and one O/P pin.
- Two push buttons are used as an inputs to the AND gate.
- The pull-up resistor value is 10 kilo Ohm and the remaining components are 330 Ohm resistor and LED. The 330 Ohm resistor is connected in series to limit the current to the LED

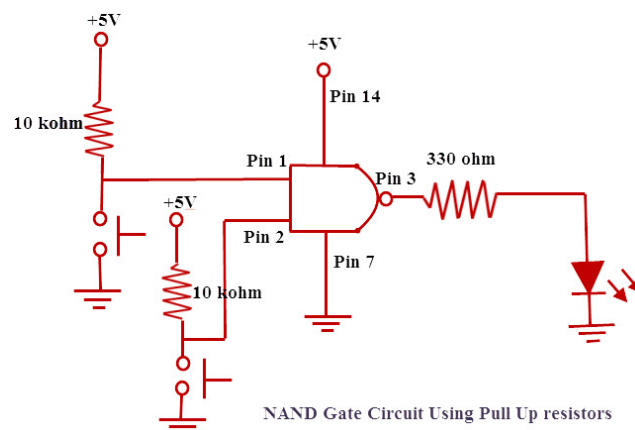The circuit diagram of the NAND gate using 2-pull-down resistors at the i/ps to the NAND gate is shown below.



NAND Gate Circuit Using Pull Up resistors


NAND Gate Circuit using Pull -up Resistor

In this circuit, to give power to the chip it is fed with 5V. So, +5V is given to the pin 14 and the pin7 is connected to the ground. Pull-up resistors are connected to the NAND gate inputs. A pull up resistor is connected to the first input of the NAND gate and positive voltage. A push button is connected to GND. When the push button is not pressed, the NAND gate input is high. When a push button is pressed, the NAND gate input is low. For the NAND gate, both I/Ps must be

low to get an output high. In order to work the owl circuit, you must press down on both buttons. This shows the great usefulness of pull-up resistors.
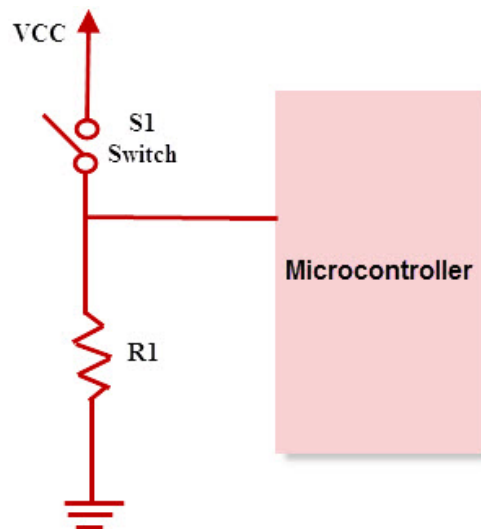
## Pull-Down Resistors

As pull up resistors, Pull-down resistors also works in the same way. But, they pull the pin to a low value. Pull-down resistors are connected between a particular pin on a microcontroller and the ground terminal. An example of a pull down resistor is a digital circuit shown in the figure below. A switch is connected between the VCC and the microcontroller pin. When the switch is closed in the circuit, the input of the microcontroller is logic 1, but when the switch is open in a circuit, the pull down resistor pulls down the input voltage to the ground (logic 0 or logic low value). The pull down resistor should have a higher resistance than the impedance of the logic circuit.



*Pull-down Resistor*

## And Gate Circuit using Pull Down Resistor

In this project, the pull-down resistor is wired up to a logic chip circuit. These circuits are the best circuits to test pull-down resistors. The Logic chip circuits work based on the low or high signals. In this project, AND gate is taken as an example of the logic chip. The main function of the AND gate is, when both inputs of the AND gate are high, then the output signal is high. In the same way when the inputs of the AND gate are low, then the output signal is low.

The required components for AND gate circuit using a pull-down resistors are AND gate chip(SN7408), 10Kilo Ohm resistors-2, Push buttons-2, 330 Ohm resistor and LED.

- Each AND gate consists of two I/P and one O/P
- Two push buttons are used as an inputs to the AND gate.
- The pull-down resistor value is 10 kilo Ohm and the remaining components are 330 Ohm resistor and LED. The 330 Ohm resistor is connected in series to limit the current to the LED.

The circuit diagram of the AND gate using 2-pull down resistors at the i/ps to the AND gate is shown below.


## And Gate Circuit using Pull Down Resistor

In this project, the pull-down resistor is wired up to a logic chip circuit. These circuits are the best circuits to test pull-down resistors. The Logic chip circuits work based on the low or high signals. In this project, AND gate is taken as an example of the logic chip. The main function of the AND gate is, when both inputs of the AND gate are high, then the output signal is high. In the same way when the inputs of the AND gate are low, then the output signal is low.

The required components for AND gate circuit using a pull-down resistors are AND gate chip(SN7408), 10Kilo Ohm resistors-2, Push buttons-2, 330 Ohm resistor and LED.

- Each AND gate consists of two I/P and one O/P
- Two push buttons are used as an inputs to the AND gate.
- The pull-down resistor value is 10 kilo Ohm and the remaining components are 330 Ohm resistor and LED. The 330 Ohm resistor is connected in series to limit the current to the LED.

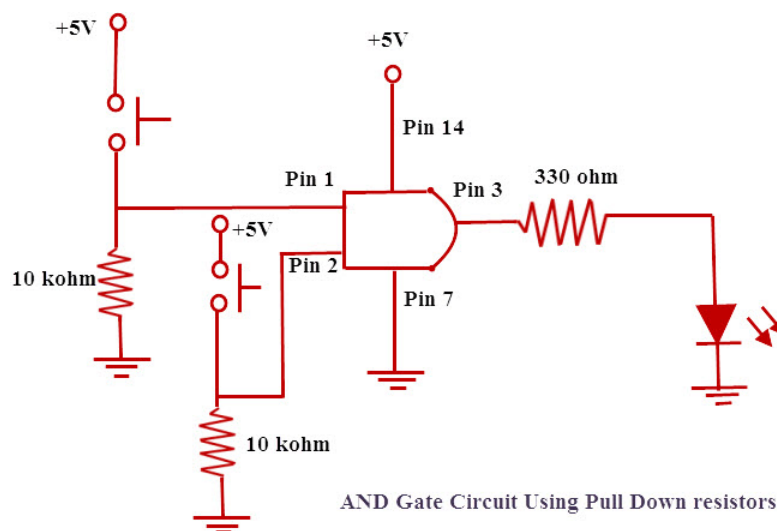The circuit diagram of the AND gate using 2-pull down resistors at the i/ps to the AND gate is shown below.



*And Gate Circuit using Pull Down Resistor*

In this circuit, to give power to the chip, it is fed with 5V. So, +5V is given to pin 14 and pin 7 is connected to the ground. The Pull-down resistors are connected to the AND gate inputs. One pull down resistor is connected to the first input of the AND gate. The pushbutton is connected to the positive voltage, and then, a pull-down resistor is connected to GND. If the push button is not pressed, AND gate input will be low. If the push button is pressed, AND gate input will be high. For AND gate, both I/Ps must be high to get an output high. In order to work the owl circuit, you must press down both the buttons. This shows the great usefulness of pull-down resistors.

## Applications of Pull-Up and Pull-Down Resistors

- Pull-up and pull-down resistors are frequently used in **interfacing devices** like interfacing a switch to microcontroller.
- **Most of the microcontrollers** have inbuilt programmable pull up/pull down resistors. So Interfacing a switch with a microcontroller directly is possible.
- In general, pull up resistors are often used than pull down resistors, although some microcontroller families have both pull-up and pull-down resistors.
- These resistors are often used in **A/D converters** to provide a controlled flow of current into a resistive sensor
- Pull-up and pull-down resistors are used in I2C protocol bus, wherein the pull-up resistors are used to allow a single pin to act as an I/P or O/P.
- When it is not connected to a I2C protocol bus, the pin floats in a high impedance state. Pull down resistors are also used for outputs to afford a known O/P

Therefore, this is all about the working and the difference between pull-up and pull-down resistors with practical example. We believe that you have got a better idea about this concept. Furthermore, for any queries regarding this article or **Electronics projects**, you can contact us by commenting in the comment section below.