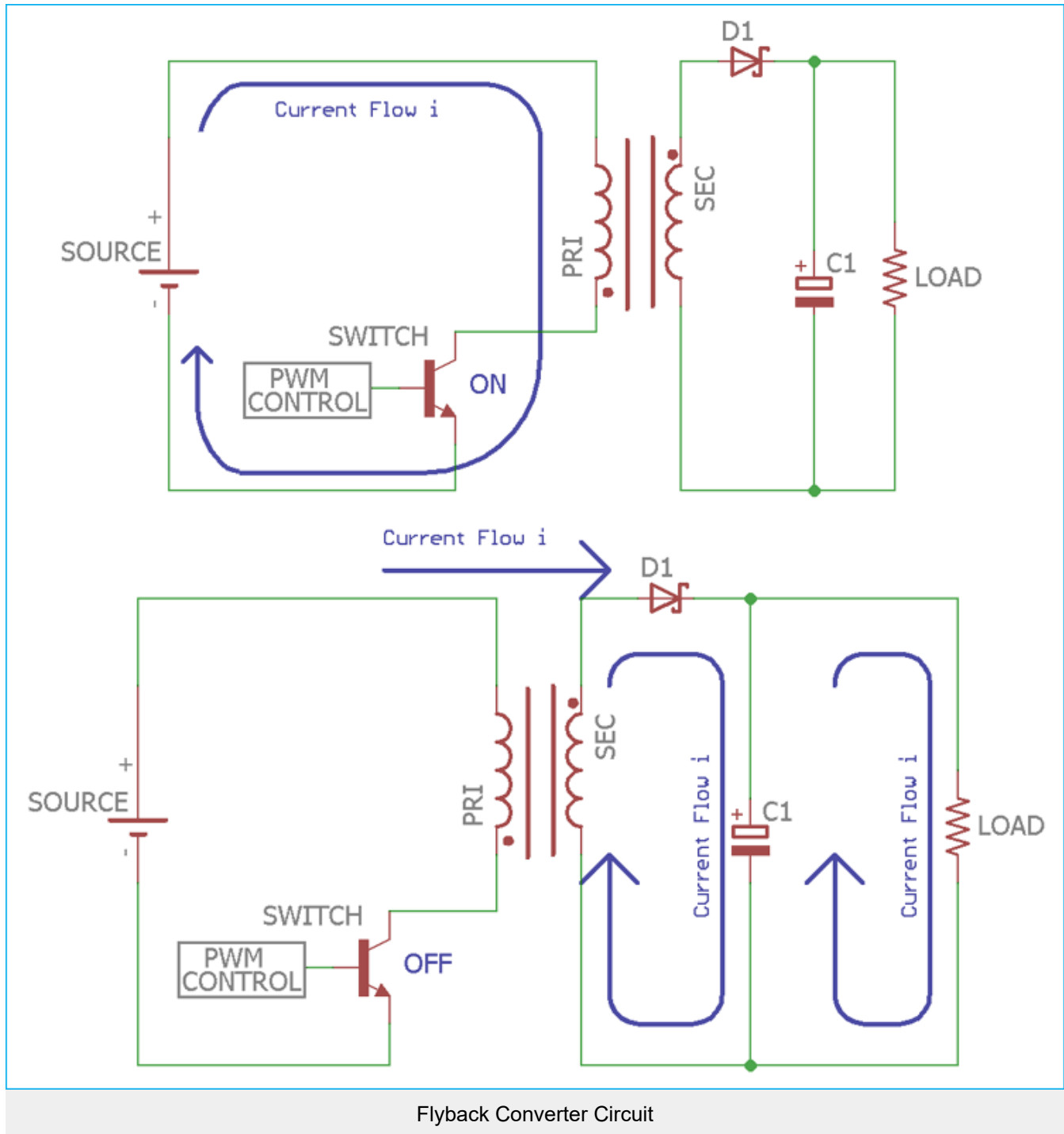


# Flyback Converter Circuit

By [Sourav Gupta](#) Feb 27, 2019

1



In electronics, a regulator is a device or mechanism which can regulate the power output constantly. There are different kinds of regulators available in the power supply domain. But mainly, in the case of DC to DC conversion, there are two types of regulators available: **Linear** or **Switching**.

A **linear regulator** regulates the output using a resistive voltage drop. Due to this Linear regulators provide lower efficiency and lose power in the form of heat. The **switching regulator** use inductor, Diode, and a power switch to transfer energy from its source to the output.

## Types of Switching Regulator

There are three types of switching regulators available.

1. **Step-up converter (Boost Regulator)**
2. **Step-Down converter (Buck regulator)**
3. **Flyback Converter (Isolated Regulator)**

We already explained [Boost Regulator](#) and [Buck Regulator circuit](#). In this tutorial, we will describe the **Flyback Regulator circuit**.


The **difference between the buck and boost regulator** is, in the buck regulator the placement of inductor, diode and the switching circuit is different than the boost regulator. Also, in case of boost regulator the output voltage is higher than the input voltage, but in the buck regulator, the output voltage will be lower than the input voltage. **A buck topology or buck converter is one of the most used basic topology used in SMPS.** It's a popular choice where we need to convert a higher voltage to a lower output voltage.

Other than those regulators, there is another regulator exists which is a popular choice among all designers, which is **Flyback regulator or Flyback converter**. This is a versatile topology which can be used where multiple outputs are needed from a single output supply. Not only that, a flyback topology allows the designer to change the polarity of the output at the same time. For example, we can create +5V, +9V and -9V output from a single converter module. The conversion efficiency is high in both cases.

Another thing in Flyback converter is the **electrical isolation** in both input and output. Why we need isolation? In some special cases, for minimizing the power noise, and safety-related operations, we need an isolated operation, where the input source is completely isolated from the output source. Let's explore basic single output flyback operation.
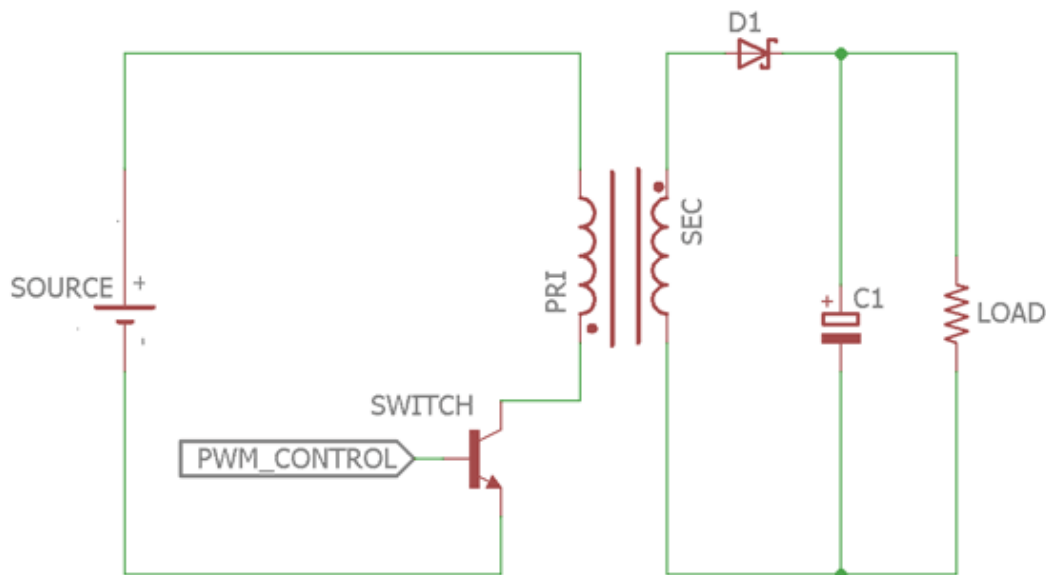
## Circuitry Operation of Flyback Converter

If we see the basic single output flyback design like the image below we will identify the basic main components which are required to build one.



A basic flyback converter requires a switch, which can be a FET or transistor, a Transformer, an output Diode, a Capacitor.


The main thing is the **transformer**. We need to understand the proper [working of a transformer](#) before understanding the actual circuitry operation.

The transformer consists of minimum two inductors, known as secondary and primary coil, wound up in a coil former with a core in between. The core determines the flux density which is an important parameter for transferring electrical energy from one winding to the other. Another most important thing is the **transformer**

**phasing**, the dots shown in the primary and secondary winding.


Also, as we can see, a PWM signal is connected across the transistor switch. It is due to the frequency of turning off and turning on time of the switch. [PWM stands for Pulse Width modulation technique](#).

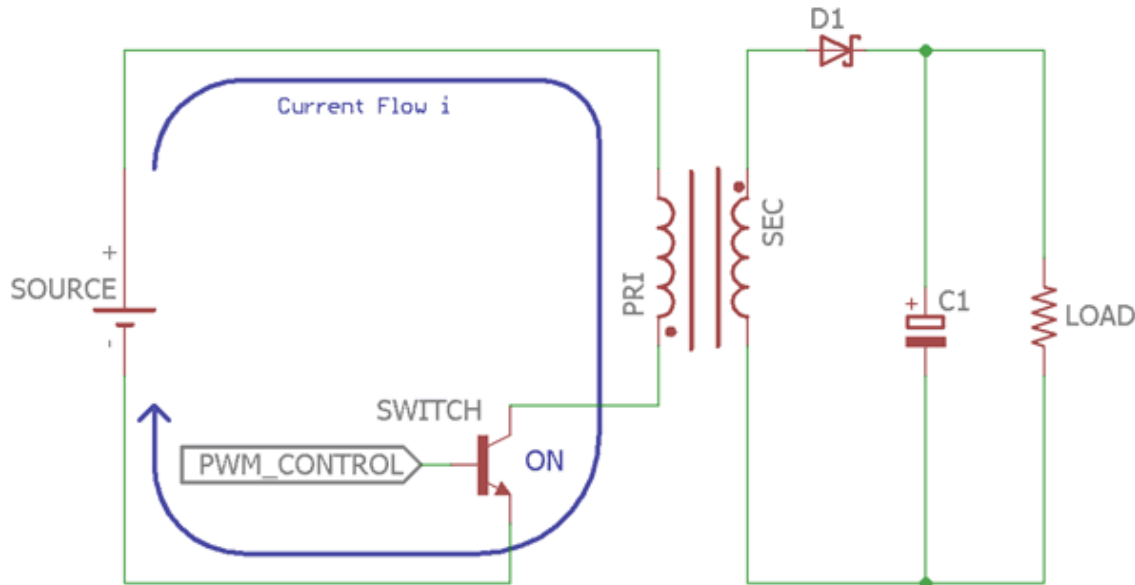In Flyback regulator, there is two circuitry operation, **One is Switch On phase** when the primary winding of the transformer charged up, and **another one is Switch off or the transfer phase** of the transformer when the electrical energy gets transferred from primary to the secondary and finally to the load.



If we assume that the switch has been turned OFF for a long time, the current in the circuit is 0 and there is no voltage present.

In this situation, **If the switch is turned ON** then the current will increase and the inductor will create a voltage drop, which is dot-negative as the voltage is more negative across the primary dotted end. During this situation, the energy flows to the secondary due to the flux generated in the core. On the secondary coil, a voltage is created in the same polarity but the voltage is directly proportional to the Secondary to Primary coil turns ratio. Due to the dot negative voltage, the diode gets turned off and no current will flow in the secondary. If the Capacitor was charged in the previous switch-OFF-ON cycle, the output capacitor will only provide the output current to the load.

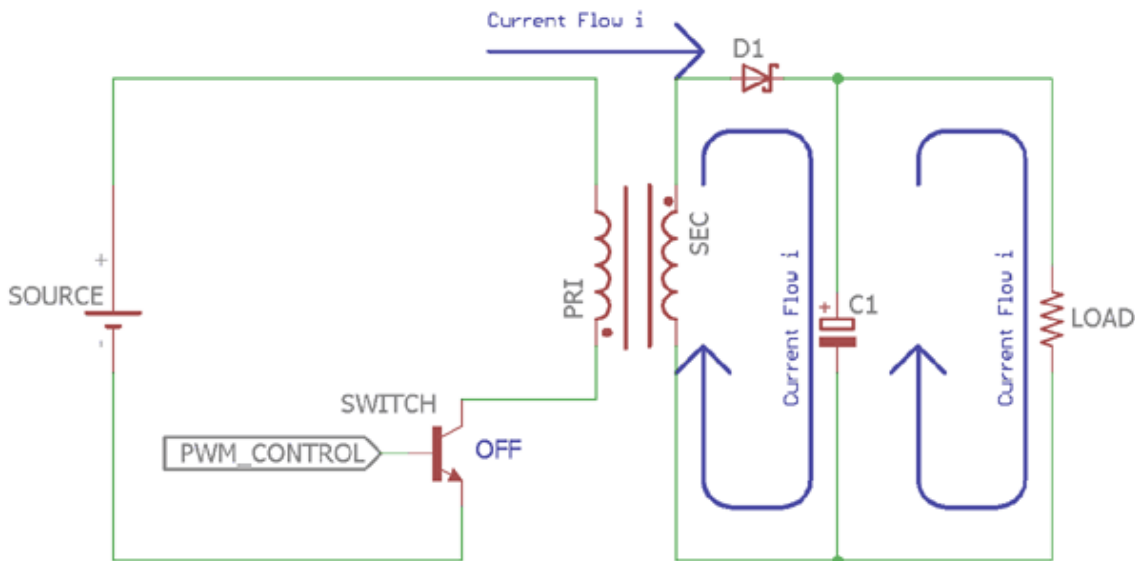

On the very next stage, **when the switch is turned off**, the current flow across primary gets decreased and thus making the secondary dot end more positive. Same as the previous switch ON stage, the primary voltage polarity create the same polarity on the secondary too, whereas the secondary voltage is proportional with the primary and secondary winding ratio. Due to the dot positive end, the diode gets turned on and the secondary inductor of the transformer provide current to the output capacitor and the load. The capacitor was lost the charge in ON cycle, now it is refilled again and capable to provide charge current to the load during the switch ON time.

In the entire Switch ON and OFF cycle, there were no electrical connections are present between input power supply to the output power source. Thus, the transformer isolates the Input and Output.

There are **two modes of operation** depending on the switch on and off timing. Flyback converter can operate in **continuous mode or discontinuous mode**.

In **continuous mode**, before the Primary charge, current goes to Zero, the cycle repeat. On the other hand, in **discontinuous mode**, the next cycle only begins when the primary inductor current goes to Zero.

## Efficiency of Flyback Converter

Now, if we investigate the efficiency, which is the ratio of output to input power:

$$(\text{Pout} / \text{Pin}) \times 100\%$$

As energy cannot be created nor destroyed, it can only be converted, most electrical energies loose unused powers into heat. Also, there is no ideal situation in the practical field. Efficiency is a large factor for selecting Voltage regulators.

One of the main power-loss factors for a switching regulator is the diode. The forward voltage drop multiply by current ( $V_f \times i$ ) is the unused wattage which is converted into heat and reduces the efficiency of the switching regulator circuit. Also, it is the additional cost to the circuitry for thermal/heat management technics like using a heatsink, or Fans to cool down the circuitry from dissipated heat. Not only the forward voltage drop, Reverse recovery for silicon diodes also produce unnecessary power loss and reduction of the overall efficiency.

One of the best way to avoid a standard recovery diode is to use Schottky diodes which have low forward voltage drop and better reverse recovery. In another aspect, the switch has been changed to modern MOSFET design where the efficiency is improved in a compact and smaller package.

Despite the fact that Switching Regulators has Higher efficiency, Stationary design technic, smaller component, they are noisy than a linear regulator but still they are widely popular.

## Example Design of Flyback Converter using LM5160

We would use a flyback topology from Texas Instruments. The circuit can be available in the datasheet.


The **LM5160** consists following features-

- Wide 4.5V to 65V Input Voltage Range
- Integrated High-Side and Low-Side Switches
  - No External Schottky Diode Required
- 2-A Maximum Load Current
- Adaptive Constant On-Time Control
  - No External Loop Compensation
  - Fast Transient Response
- Selectable Forced PWM or DCM Operation
  - FPWM Supports Multi-output Fly-Buck
- Nearly Constant Switching Frequency
  - Resistor Adjustable upto 1 MHz
- Program Soft Start Time
- Prebiased Start-up
- $\pm 1\%$  Feedback Voltage Reference
- LM5160A Allows External VCC Bias
- Inherent Protection Features for Robust Design

- Peak Current Limiting Protection
  - Adjustable Input UVLO and Hysteresis
  - VCC and Gate Drive UVLO Protection
  - Thermal Shutdown Protection With Hysteresis
- 
- Create a Custom Design Using the LM5160A With the WEBENCH® Power Designer

It supports a wide input voltage range from 4.5V to 70V as input and provides 2A of output current. We can also select the forcible PWM or DCM operations.

Pinout of LM5160

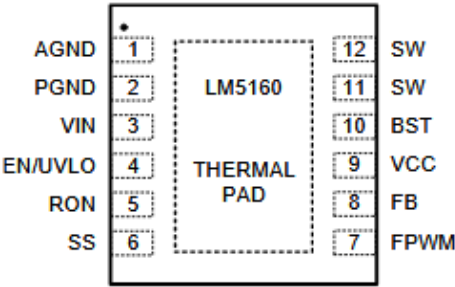

PIN		I/O <sup>(1)</sup>	DESCRIPTION
NO.	NAME		
1	AGND	—	Analog Ground. Ground connection of internal control circuits.
2	PGND	P	Power Ground. Ground connection of the internal synchronous rectifier FET.
3	VIN	P	Input supply connection. Operating input range is 4.5 V to 65 V.
4	EN/UVLO	I	Precision enable. Input pin of undervoltage lockout (UVLO) comparator.
5	RON	I	On-time programming pin. A resistor between this pin and VIN sets the switch on-time as a function of input voltage.
6	SS	I	Soft start. Connect a capacitor from SS to AGND to control output rise time and limit overshoot.
7	FPWM	I	Forced PWM logic input pin. Connect to AGND for discontinuous conduction mode (DCM) with light loads. Connect to VCC for continuous conduction mode (CCM) at all loads and Fly-Buck configuration.
8	FB	I	Feedback input of voltage regulation comparator.
9	VCC	O	Internal high voltage start-up regulator bypass capacitor pin.
10	BST	P	Bootstrap capacitor pin. Connect a capacitor between BST and SW to bias gate driver of high-side buck FET.
11,12	SW	P	Switch node. Source connection of high-side buck FET and drain connection of low-side synchronous rectifier FET.
—	NC	—	No Connection.
—	EP	—	Exposed Pad. Connect to AGND and printed-circuit board ground plane to improve power dissipation.

(1) P = Power, G = Ground, I = Input, O = Output.

The IC is not available at DIP package or an easy solderable version, although it is a problem but the IC save a lot of PCB space as well as a greater thermal performance over PCB heatsink. The pin diagram is shown in the above image.

Absolute Maximum Ratings

We need to be careful about the absolute maximum rating of the IC.

Over the recommended operating junction temperature of  $-40^{\circ}\text{C}$  to  $125^{\circ}\text{C}$  (unless otherwise noted).<sup>(1)(2)</sup>


		MIN	MAX	UNIT
Input voltages	VIN to AGND	-0.3	70	V
	EN/UVLO to AGND	-0.3	70	
	RON to AGND	-0.3	70	
	BST to AGND	-0.3	84	
	VCC to AGND	-0.3	14	
	FPWM to AGND	-0.3	14	
	SS to AGND	-0.3	7	
	FB to AGND	-0.3	7	
Output voltages	BST to SW	-0.3	14	V
	BST to VCC		70	
	SW to AGND	-1.5	70	
	SW to AGND (20-ns transient)	-3		
Operating junction temperature, $T_J$ <sup>(3)</sup>		-40	150	$^{\circ}\text{C}$
Storage temperature, $T_{\text{stg}}$		-65	150	$^{\circ}\text{C}$

The SS and FB pin has low voltage tolerance.

## Flyback Converter Circuit Diagram and working

By using this LM5160 we will simulate a 12V isolated power supply based on the following spec. We chose the circuit as everything is available in the manufacturer website.

DESIGN PARAMETER	EXAMPLE VALUE
Input voltage range	18 V to 32 V
Isolated output	12 V
Isolated load current range	0 mA to 400 mA
Nominal switching frequency	300 kHz
Peak Efficiency	88%

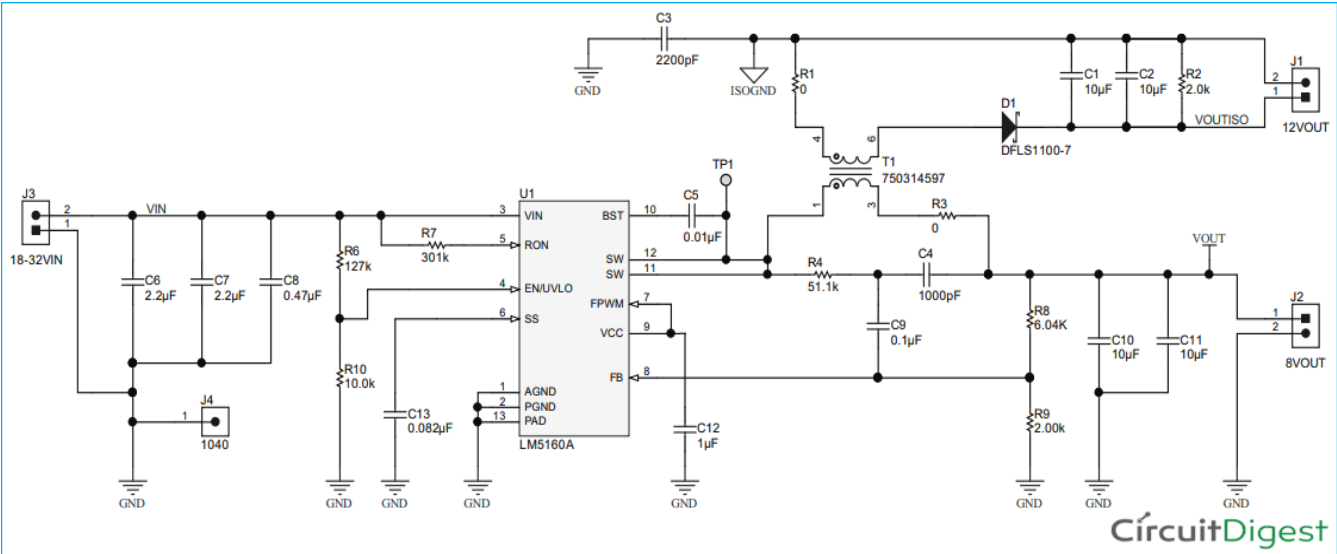

The schematic uses plenty of components but it is not complicated to understand. The C6, C7, and C8 on the input are used for filtration of the input supply. Whereas R6 and R10 are used for the Under voltage lockout related purposes. The R7 resistor is for the On time related purpose. This pin is programmable using a simple

resistor. C13 capacitor connected across the SS pin is a soft start capacitor. The AGND (Analog Ground) and PGND (Power Ground) and the PAD is connected with the supply GND. On the Right side, C5, 0.01 uF capacitor is a Bootstrap capacitor which is used for the biasing of the gate driver. R4, C4 and C9 are the ripple filter where as R8 and R9 providing the feedback voltage to the feedback pin of the LM5160. This two resistors ration determine the output voltage. C10 and C11 are used for primary non isolated output filtration.


A major component is the T1. It is a coupled inductor with a 60uH inductor on both sides, primary and secondary. We can choose any other coupled inductor or sepic inductor with the following specification-

1. Turns Ratio SEC:PRI = 1.5 : 1
2. Inductance = 60uH
3. Saturation Current = 840mA
4. DC Resistance PRIMARY = 0.071 Ohms
5. DC Resistance SECONDARY = 0.211 Ohms
6. Freq = 150 kHz


C3 is used for EMI stability. D1 is the forward diode which converts the output and C1, C2 are the filter caps, R2 is the minimum load which is required for the startup.

Those who want to make the power supply for custom specifications and want to calculate the value, the manufacturer provides excellent [Excel tool](#) where you just simply put the data and the excel will calculate the components value depending on the formulas provided in the datasheet.

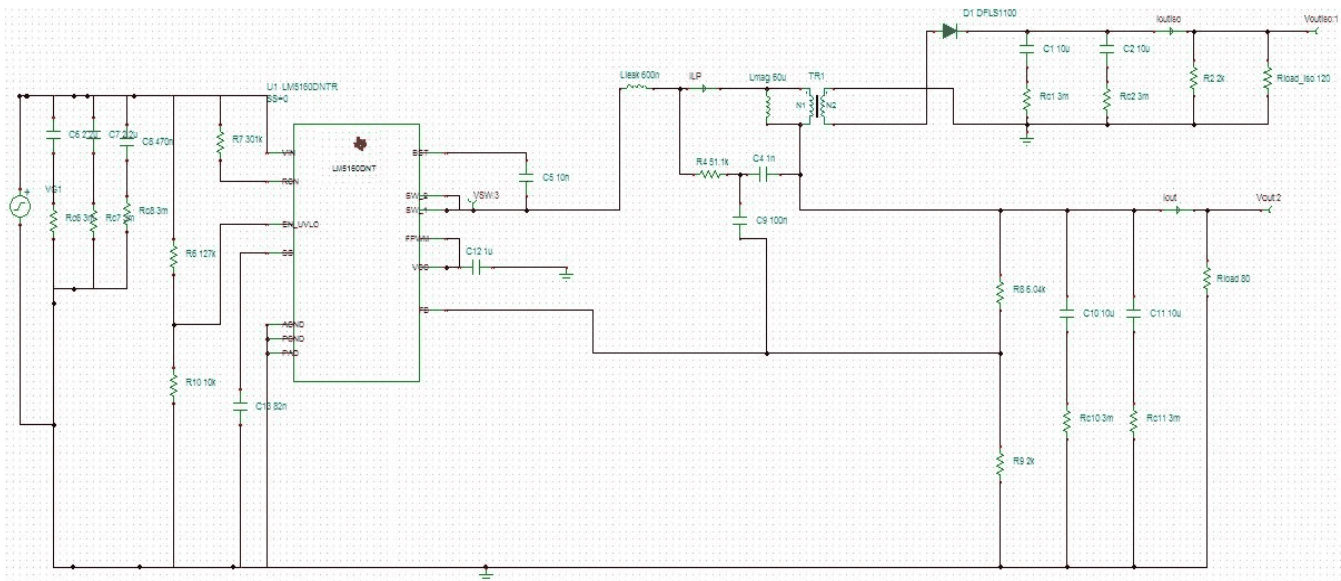The manufacturer has also provided the spice model as well as complete schematic which can be simulated using Texas Instrument's own SPICE-based simulation tool TINA-TI. Below is the Schematic drawn using TINA-TI tool provided by the manufacturer.



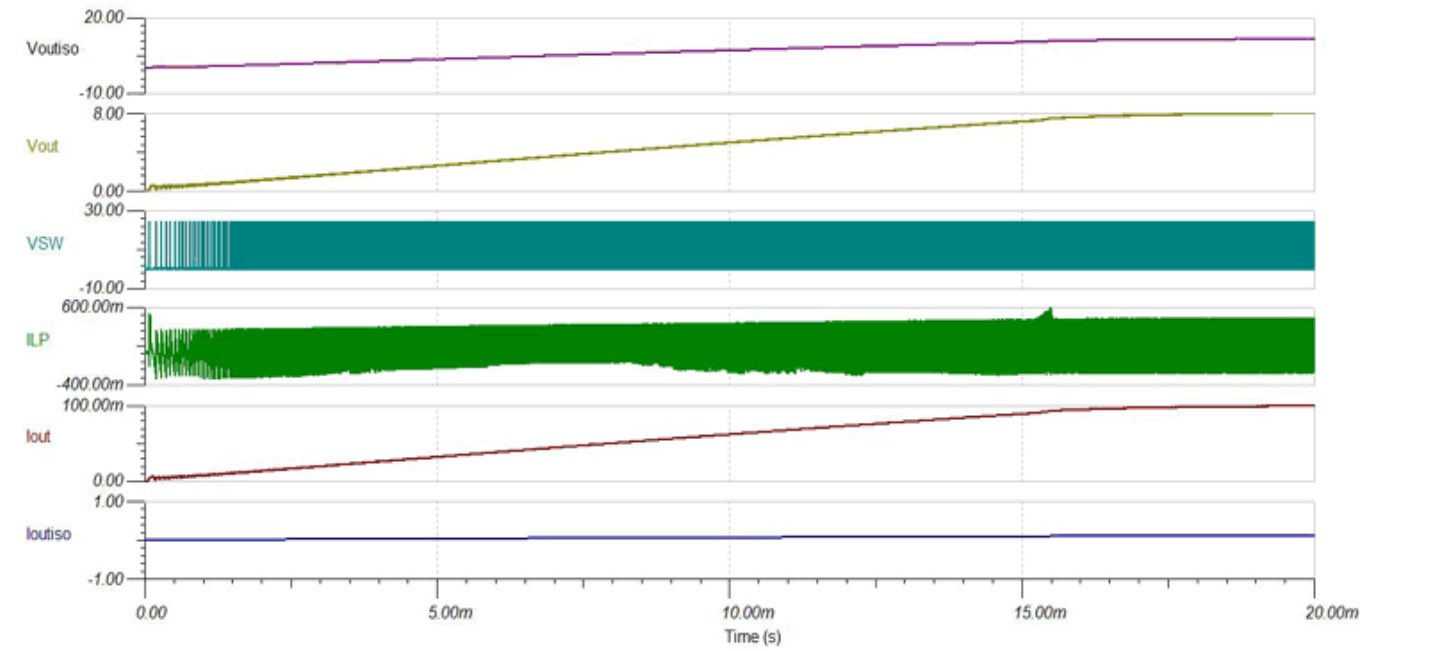The simulation result can be shown in the next image where perfect load current and voltage can be shown-



Tags

- POWER ELECTRONICS
- TRANSFORMER
- DC DC CONVERTER
- PWM