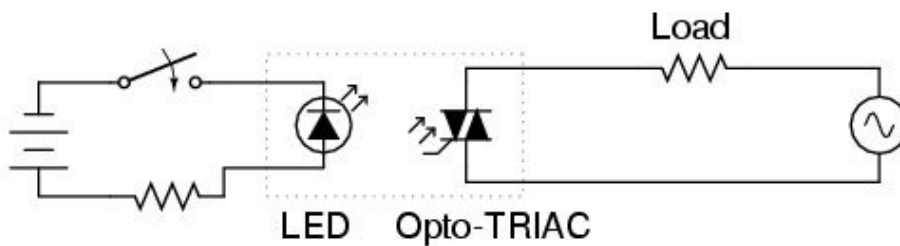


Technology Remaking the World

[Webmaster](#)[Environmentalism](#)[Science & Technology](#)[Hobby Electronics](#)[US Constitution](#)[Religion & History](#)[E-Mail](#)

A photo-triac uses light instead of a small current from T2 to trip on the gate. While seldom used alone the LED emitter and photo-triac detector are used in opto-couplers.

www.bristolwatch.com


The most basic solid state relay.

Solid State AC Relays Using Triacs

The most basic solid state relay (SSR) is shown above being a light source and a triac with a photosensitive gate. For more information on how triacs and SCRs operate see [Basic Triac and SCR Projects and Circuits](#). A solid state relay (SSR) consists of four main parts:


1. An opto-isolator or opto-coupler to isolate the low voltage DC control, often from a microcomputer, from the high voltage AC. The input opto-coupler is often a light emitting diodes while the output is often a photo transistor or photo Diac for switching on a triac.
2. The SSR often has an internal zero-crossing detector circuit to switch on the triac during the time the sin wave is a little past zero or 180 degrees. This helps prevent damage the load and needless power surges.

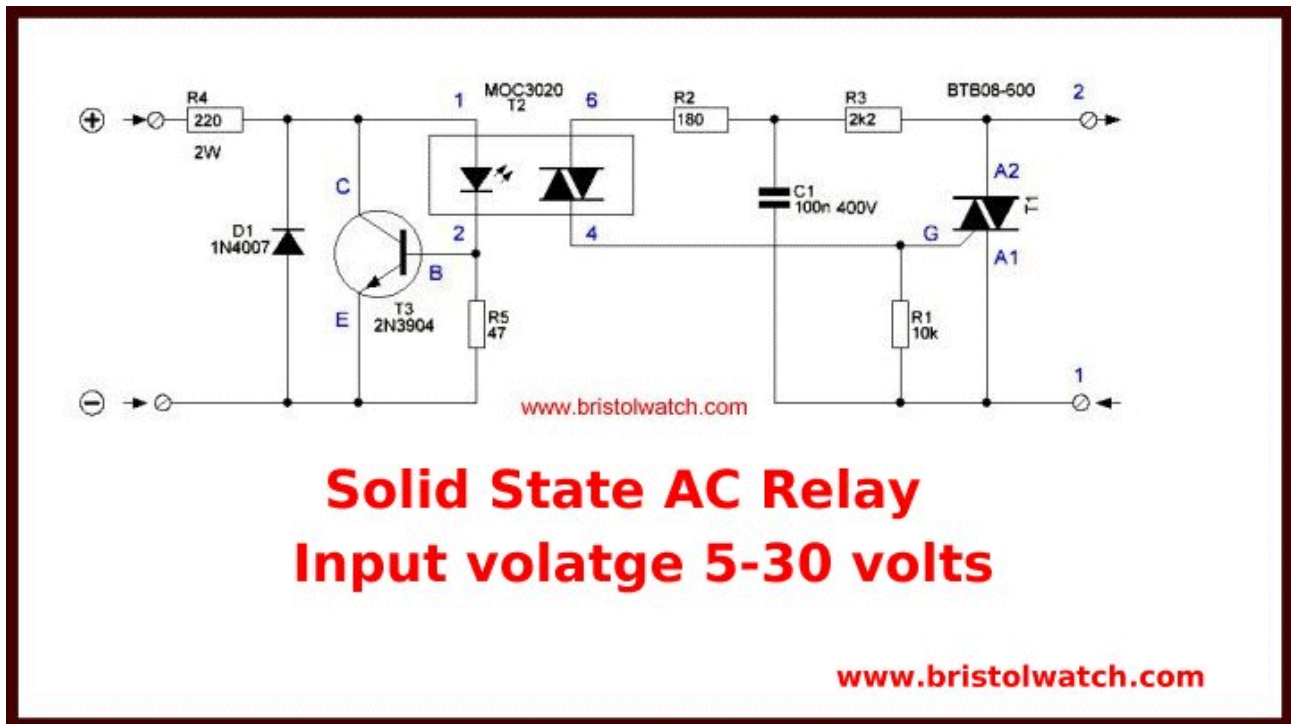3. A triac acting as an AC switch. If the SSR is for DC the output is a power transistor.
4. A snubber circuit(s) to prevent false firing of the triac from noise spikes generated with magnetic loads.



A more practical SSR.

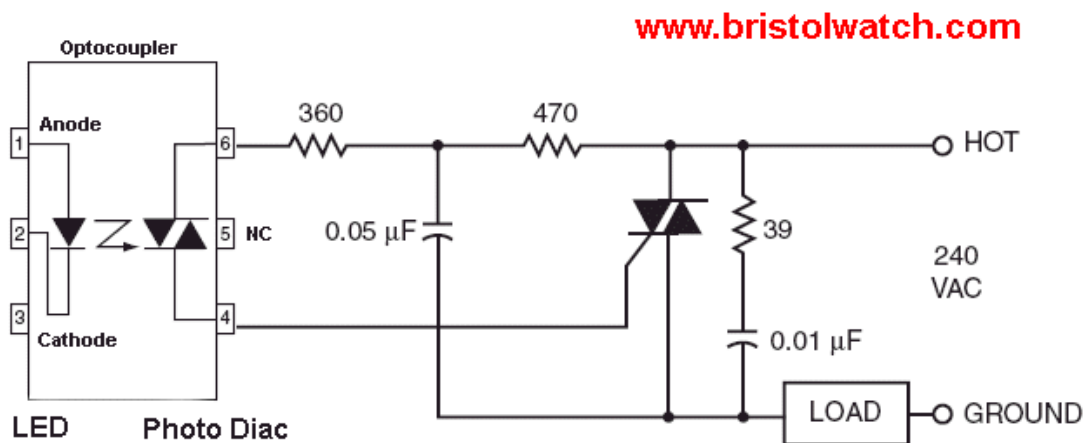Also see [Using Opto-Couplers](#) An important note is the output has no electrical connection to the input and can provide up to several thousand volts isolation. Also see [More sample circuits](#).



Opto-Isolators with Diacs


An opto-isolator is a solid state device designed to provide electrical isolation between input and output. The input consists of a light emitting diode (LED) in a six or eight pin dip (IC)

package depending on type. The output can be a photo transistor, photo Diac, etc. There is no electrical contact between input and output. When the LED is turned on, the Diac, transistor, etc. will conduct from the light emitted from the diode thus turning on the triac like a switch. The MOC3011 series is made to connect to triacs, the MOC301x types for 110 volts, and the MOC302x types for 240 volts. [View the schematic.](#)

The zero crossing circuit assures triac switches at say 10 degrees.

The prevents surge damage to the load.

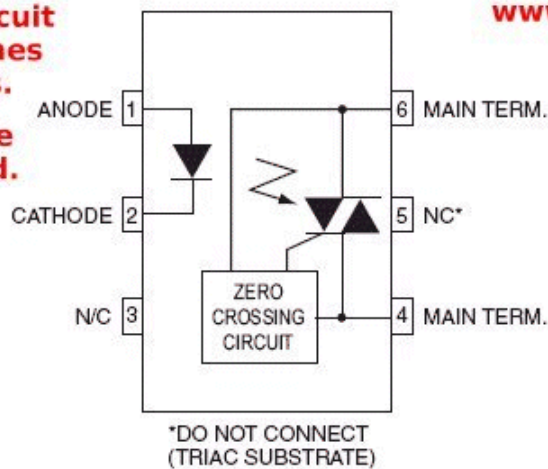
Can't be used with AC phase control circuits.



www.bristolwatch.com

MOC3042 Opto-coupler contains a LED emitter and photo triac with zero-crossing circuits.

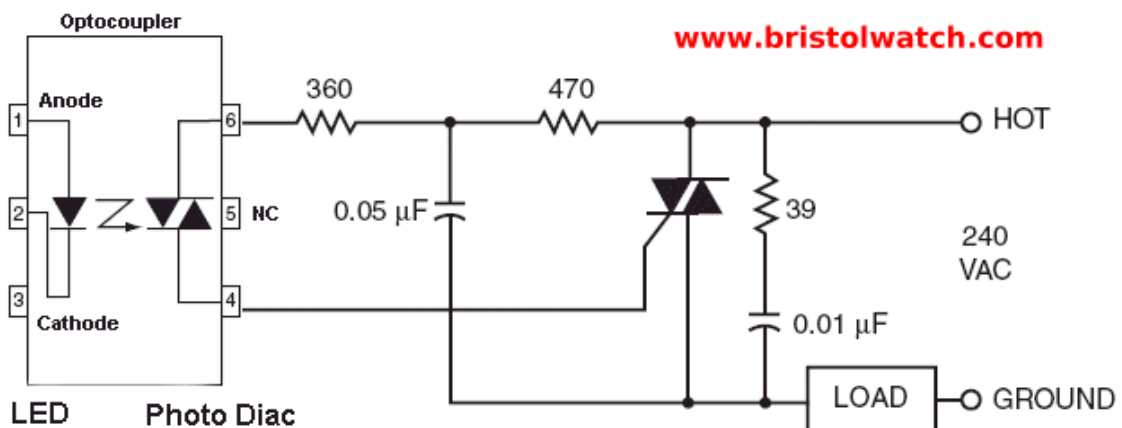(above) MOC3042 Other opto-couplers have a built in zero-crossing detector.



www.bristolwatch.com

Triac with Opto-coupler. This includes "snubbing" circuits on the triac and Opto-coupler to assure stable operation with inductive loads.

Snubbers

A snubber circuit (usually of the RCA type) is often used between Mt1 and Mt2. Snubber circuits are used to prevent premature triggering caused for example by voltage spikes in the AC supply or those produced by inductive loads such as motors. Also, a gate resistor or capacitor (or both in parallel) may be connected between gate and Mt1 to further prevent false

triggering. That could increase the required trigger current and perhaps a delay in turnoff as the capacitor discharges.

In this circuit above the "hot" side of the line is switched and the load connected to the cold or ground side. The 39-ohm resistor and 0.01uF capacitor are for snubbing of the triac, and the 470 ohm resistor and 0.05 uF capacitor are for snubbing the coupler. These components may or may not be necessary depending upon the particular and load used.

For more on the above opto-coupler see [moc30xx series opto-isolator](#) and [MOC3042 with zero-crossing circuits](#). (both pdf files)

- New Nov. 2014
- [Using the ULN2003A Transistor Array with Arduino](#) YouTube
- [ULN2003A Darlington Transistor Array with Circuit Examples](#)
-
- [Using the TIP120 & TIP120 Darlington Transistors with Arduino](#) YouTube
- [Tutorial Using TIP120 and TIP125 Power Darlington Transistors](#)
- [Driving 2N3055-MJ2955 Power Transistors with Darlington Transistors](#)
-
- [Using Power MOSFETS with Arduino](#) YouTube
- [N-Channel Power MOSFET Switching Tutorial](#)
- [P-Channel Power MOSFET Switch Tutorial](#)
-
- [Using PNP Bipolar Transistors with Arduino, PIC](#) YouTube
- [Using NPN Bipolar Transistors with Arduino, PIC](#) YouTube
- [Understanding Bipolar Transistor Switches](#)
-
- [How to build a Transistor H-Bridge for Arduino, PIC](#) YouTube
- [Build a High Power Transistor H-Bridge Motor Control](#)
-
- [Build a Power MOSFET H-Bridge for Arduino, PIC](#) YouTube
- [H-Bridge Motor Control with Power MOSFETS](#)
- [More Power MOSFET H-Bridge Circuit Examples](#)
-
- [Basic Triacs and SCRs](#)
- [Constant Current Circuits with the LM334](#)
- [LM334 CCS Circuits with Thermistors, Photocells](#)
- [LM317 Constant Current Source Circuits](#)
- [TA8050P H-Bridge Motor Control](#)
- [All NPN Transistor H-Bridge Motor Control](#)
- [Basic Triacs and SCRs](#)
- [Comparator Theory Circuits Tutorial](#)
-
- [Constant Current Circuits with the LM334](#)
- [LM334 Constant Current Source with Resistive Sensors](#)
- [LM317 Constant Current Source Circuits](#)
- [Introduction Hall Effect Switches, Sensors, and Circuits](#)
- [Using Ratiometric Hall Effect Sensors](#)
- [Pulse Width Modulation Power Control for Microcontrollers](#)
- [Introduction to PIC12F683 Programming](#)
- [Basic Transistor Driver Circuits for Micro-Controllers](#)
- [Opto-Isolated Transistor Drivers for Micro-Controllers](#)
-
- Added Nov. 16, 2014

- [ULN2003A Darlington Transistor Array with Circuit Examples](#)
- [Tutorial Using TIP120 and TIP125 Power Darlington Transistors](#)
- [Driving 2N3055-MJ2955 Power Transistors with Darlington Transistors](#)
- [Understanding Bipolar Transistor Switches](#)
- [N-Channel Power MOSFET Switching Tutorial](#)
- [P-Channel Power MOSFET Switch Tutorial](#)
- [H-Bridge Motor Control with Power MOSFETS](#)
- [More Power MOSFET H-Bridge Circuit Examples](#)
- [Build a High Power Transistor H-Bridge Motor Control](#)

- [Comparator Theory Circuits Tutorial](#)
- [Arduino Projects Revisited Revised](#)
- [Schematic for Following Projects](#)
- [Programming ADS1115 4-Channel I2C ADC with Arduino](#)
- [Arduino uses ADS1115 with TMP37 to Measure Temperature](#)
- [Connect Arduino to I2C Liquid Crystal Display.](#)
- [Arduino Reads Temperature Sensor Displays Temperature on LCD Display.](#)
- [Arduino with MCP4725 12-bit Digital-to-Analog Converter Demo](#)

© Copyright 2018 Lewis Loflin [E-Mail](#)