

Lecture 5 – Homework Examples

Constant Voltage Drop Model


- Forward Bias Example
- Reverse Bias Example
- Diode OR-ing Example
- Thevenin Equivalent Example

Exponential Model

Q: What change in diode voltage corresponds to a factor of 10 change in current?

HOMEWORK EXAMPLES


HW#1. i) P3.2 (a)

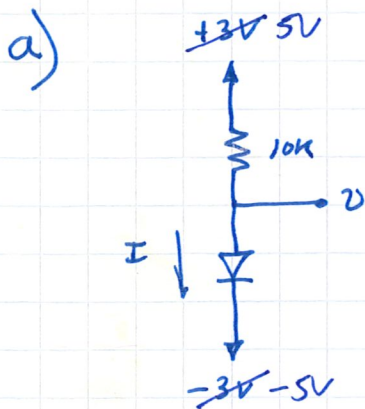• FIND I, V (USING 0.7 VOLT MODEL)

• Q1. IS THE DIODE ON OR OFF? (i.e. F.B. OR R.B.)

ON

• OK, REDRAW FOR ANALYSIS

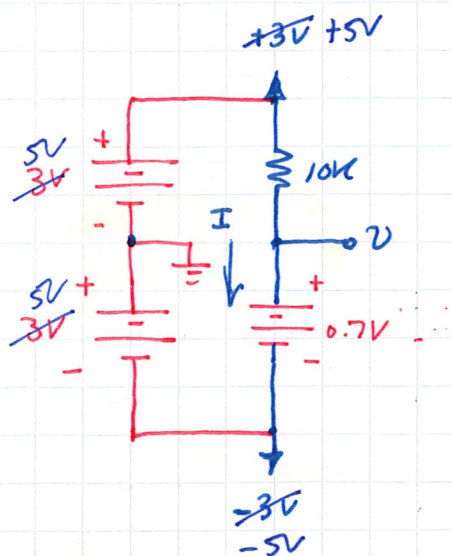

• KVL

$$+3V - I(10k) - 0.7 + 5V = 0$$

$$9.3V - I(10k) = 0$$

$$I = \frac{9.3}{10k} = \boxed{0.93 \text{ mA}}$$

• FIND V :

$$+3V - (10k)I = V$$

$$+3V - (10k)(0.93 \text{ mA}) = V$$

$$3V - 9.3V = V$$


$$\boxed{V = -6.3V}$$

W.R.T. GROUND!

HW#1. i) P.3.2 (b)

REVERSE THE DIRECTION OF THE DIODE.


b)

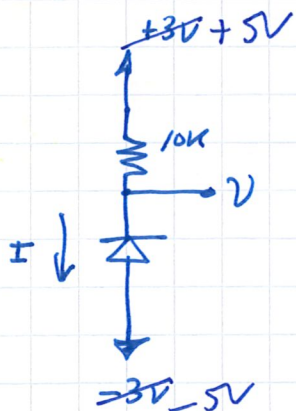

• Φ_1 : ON OR OFF? OFF (R.B.)

• MODEL? OPEN CIRCUIT!

• REDRAW

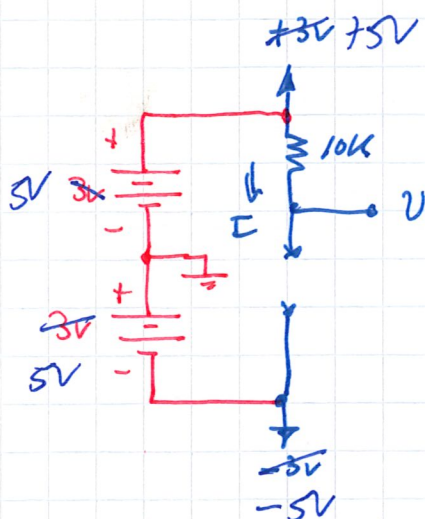

$$I = ? \underline{\underline{0!}} \quad \text{WHY?}$$

$$V = ?$$

$$+3V + \cancel{5V} I = V$$


$$\therefore \boxed{V = +3V} + 5V$$

NO VOLTAGE DROP ACROSS THE RESISTOR!

$$I = 0!$$

P3.3

FIND I, V :

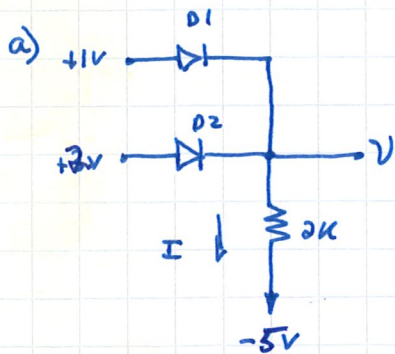

Q. IF $D1$ IS ON, WHAT WOULD V BE?

$$V = 1 - 0.7 = 0.3V$$

Q. WOULD $D2$ BE F.B. OR R.B.?

F.B.

Q. WHAT WOULD THE VOLTAGE ACROSS $D2$ BE?

$$2V - 0.3V = 1.7 \text{ VOLTS} \Leftarrow$$

Q. DOES THIS MAKE SENSE OR NOT? NO!

Q. IF $D2$ IS ON, WHAT WOULD V BE?

$$V = 2 - 0.7 = 1.3V$$

Q. WOULD $D1$ BE F.B. OR R.B.?


R.B.



IS THIS OK? YES!

\therefore

$D1$	OFF
$D2$	ON

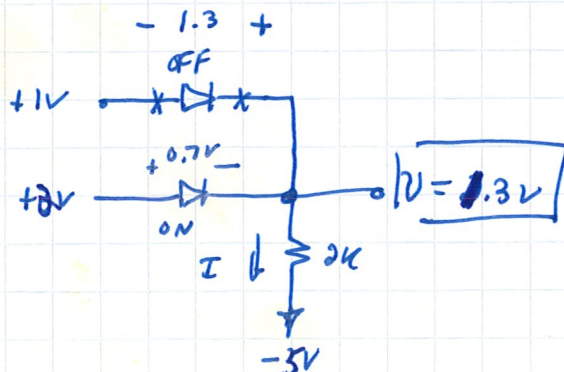


$$\therefore I = (1.3V - (-5V)) / 2k = 6.3V / 2k = \boxed{3.15 \text{ mA}}$$


✓ OBSERVATION, THIS CIRCUIT FOLLOWS THE "HIGHER" VOLTAGE...
 Q. PART b) ... WHAT DO YOU THINK IT WILL DO... -3-

HW EXAMPLES:

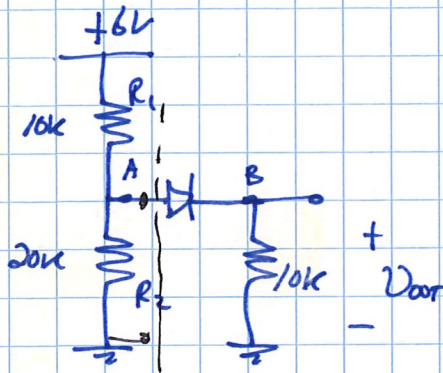1) ILLUSTRATING USE OF THEVENIN EQUIVALENT




FIND V_{OUT}

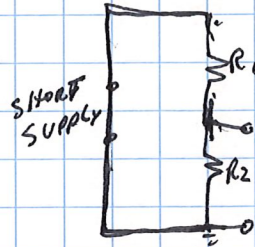

To Find R_{TH} ,

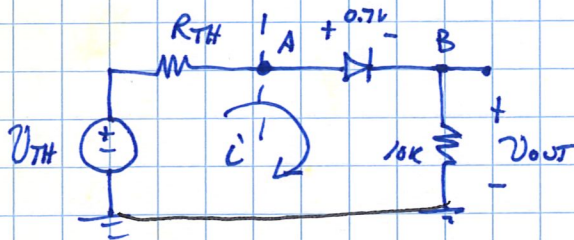- 1) Let $V_{SOURCE} = 0$
- 2) FIND R_{TH} BETWEEN OUTPUT NODES.
- 3) $R_{TH} = R_1 \parallel R_2$



$$V_{TH} = V_{OPEN\ CIRCUIT} = \left(\frac{20k}{10k+20k} \right) \cdot 6V = \left(\frac{2}{3} \right) 6V = \underline{4V}$$

$$R_{TH} = R_1 \parallel R_2 = 10k \parallel 20k = \underline{6.67k\Omega}$$



KVL:

$$4V = \overset{(6.67k)}{R_{TH}} \cdot i + 0.7V + 10k \cdot i$$

$$\therefore i = \frac{3.3V}{16.67k} = \underline{0.198mA}$$

$$\therefore V_{OUT} = (10k)(0.198mA) = \underline{1.98V}$$

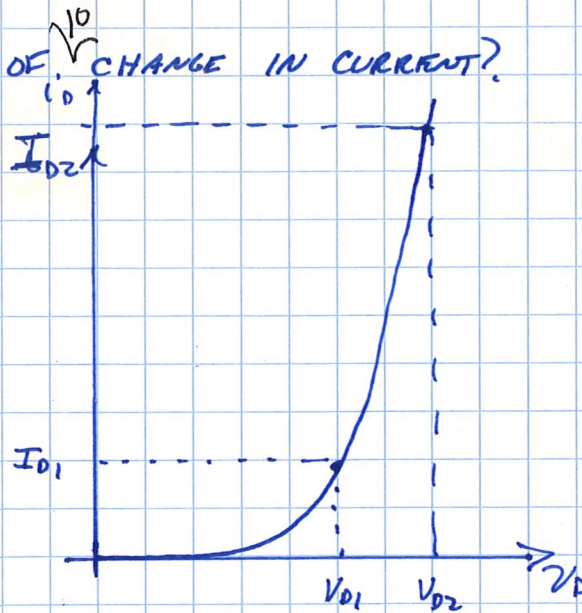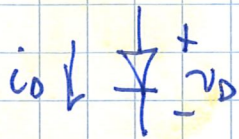2) WHAT CHANGE IN DIODE VOLTAGE CORRESPONDS TO A FACTOR OF 10 CHANGE IN CURRENT?



$$i_D \approx I_S (e^{v_D/nV_T} - 1)$$

$$I_{D2} \approx I_S e^{V_{D2}/nV_T}$$

$$I_{D1} \approx I_S e^{V_{D1}/nV_T}$$

RATIO FORM OF EQ:

$$\frac{I_{D2}}{I_{D1}} \approx e^{\overbrace{(V_{D2} - V_{D1})}^{\Delta V} / nV_T}$$

$$\Delta V = nV_T \ln\left(\frac{I_{D2}}{I_{D1}}\right)$$

$$= (1)(25\text{mV}) \underbrace{\ln(10)}_{2.3} = 57.6\text{mV} \quad \text{FOR } n=1$$

$$= (2)(25\text{mV})(2.3) = 115.1\text{mV} \quad \text{FOR } n=2$$

CONCLUSION:

* A SMALL CHANGE IN v_D CORRESPONDS TO A LARGE CHANGE IN i_D !

FOR $\Delta V = 60\text{mV}$ FACTOR OF 10 CHANGE IN i_D !