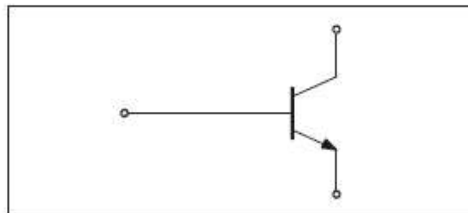


42. Fundamentals of Transistor With Built-In Resistors


The transistor with built-in resistor is the one that resistors equipped to bipolar transistor, oftenly called as digital transistor.

Here is the product list of the transistor. (http://www.chip1stop.com/search.do?classCd=011000&classLv=2&searchType=2&dispAllFlg=true&_ga=2.90469022.523109363.1540771289-365662499.1539562411)


Common bipolar transistor ▶



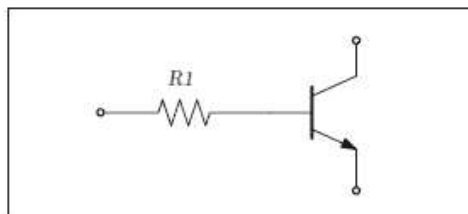Addition of resistance R1 ▶
(Input resistance)




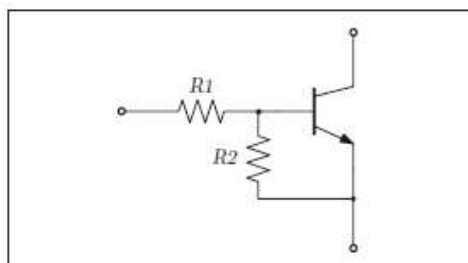Addition of resistance R2 ▶
(Resistance between EB)



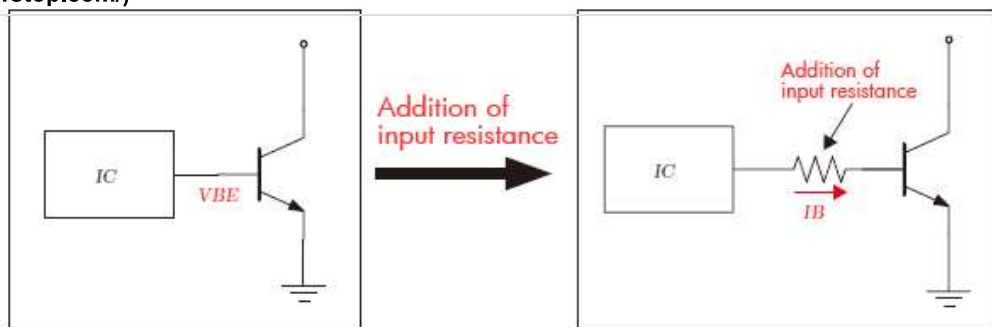(1) About resistance R1

The role of resistor R1: The performance of the transistor is stabilized by converting the input voltage into the current. The performance of bipolar transistor is unstable if voltage such as output of IC is directly applied on the base terminal. The operation can be stabilized when it is made to operate as current control by putting resistor (input resistor) between




Operation is unstable.

Operation is unstable in the input voltage (The output current changes exponentially in the input voltage).

Operation is stable.

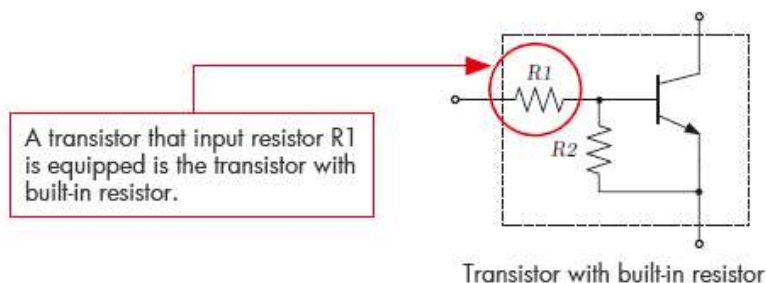
The operation stabilize when adding input resistance and made the input to electric current (Base current: I_B). (The output current changes into linear for the input current.)





Compares the operation of transistor when the input is the voltage, and when the input is current.

	Voltage control Input: Voltage V_{BE} between emitter-base	Current control Input: Base current I_B
Measurement circuit diagram		
Theoretical formula	$I_C = I_s \cdot e^{\frac{V_{BE}}{kT/q}}$ <p> I_s: Constant determined by device k: Boltzmann constant T: Absolute temperature q: Charge of electron Exponential changes </p>	$I_C = hFE \cdot I_B$ <p> hFE: Amplification factor It is almost constant according to the device. Linear changes </p>
Input output characteristic		

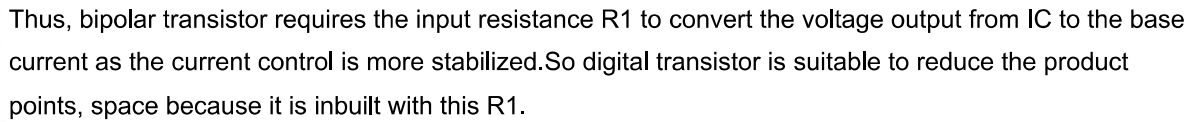An Arrow Company
current is greatly changed
(<https://www.chip1stop.com>)



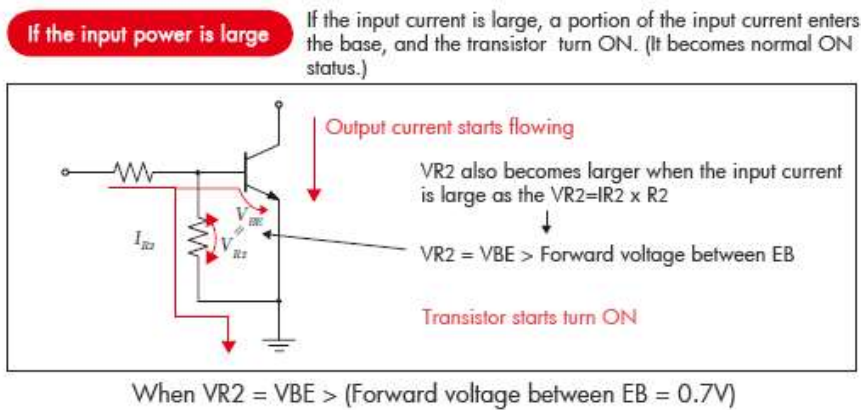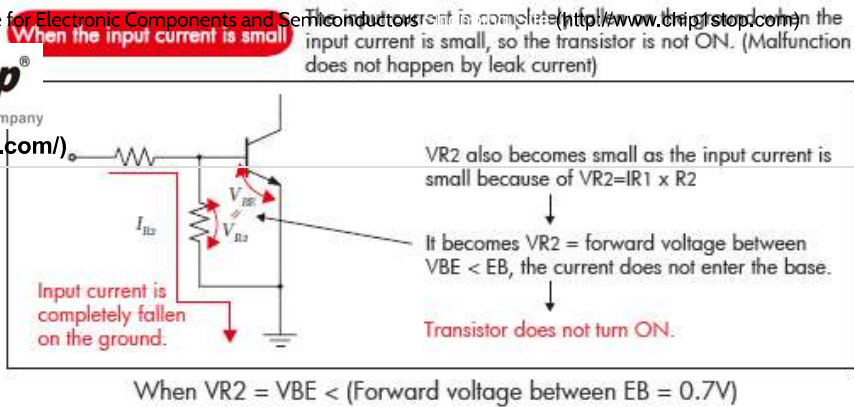Input currents will all fall on the ground if it is a minute current, if the input current is large, then a large portion of the input current will start entering the the base of the transistor, and ON the transistor.



Thus, the stable operation is achieved by resistance R2, although voltage of certain level is required to turn on the transistor.

Here is the product list of the transistor. (http://www.chip1stop.com/search.do?classCd=011000&classLv=2&searchType=2&dispAllFlg=true&_ga=2.90469022.523109363.1540771289-365662499.1539562411)