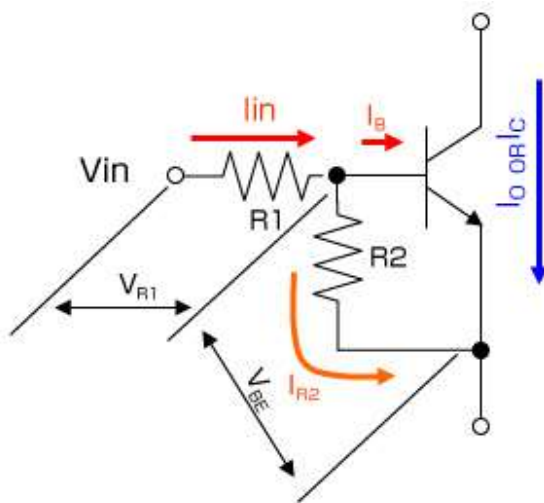


Digital Transistor

< Understanding the Principles of Digital Transistors >

Selection Method

- 1) The I_C/I_B ratio needed in order to saturate the transistor is 20/1
- 2) Input resistor R_1 : $\pm 30\%$, E-B resistor R_2 : $R_2/R_1 = \pm 20\%$
- 3) V_{BE} : 0.55V to 0.75V



Equations Used for Digital Transistors

- The relationship of the DC current gain of digital transistors

GI: Digital transistor DC current gain

$$GI = I_o / I_{in}$$

$$h_{fe} = I_c / I_B$$

$$I_o = I_c, I_{in} = I_B + I_{R2}, I_B = I_c / h_{fe},$$

$$I_{R2} = V_{BE} / R_2$$

$$\text{Voltage relationship: } V_{in} = V_{R1} + V_{BE}$$

$$G_I = \frac{I_c}{(I_c / h_{fe}) + (V_{BE} / R_2)}$$

- The relationship with collector current:

$$I_c = I_B \times h_{fe} \quad I_{R2} = V_{BE} / R_2$$

$$I_B = I_{in} - I_{R2}$$

$$I_{in} = (V_{in} - V_{BE}) / R_1$$

$$\therefore I_c = h_{fe} \times ((V_{in} - V_{BE}) / R_1) - (V_{BE} / R_2) \quad \dots (1)$$

The value of h_{fe} mentioned here is not saturated at $V_{CE} = 5V / I_C = 1mA$.

When using as a switch the current ratio for saturation $I_C/I_B=20/1$ is required.

$$\therefore I_C = 20 \times ((V_{in} - V_{BE})/R_1) - (V_{BE}/R_2) \quad (2)$$


Replace the h_{fe} in (1) with 20/1.

Calculations are carried out taking into account variations.

The worst-case values for R_1 (+30% max.), R_2 (-20% min.), and V_{BE} (0.75V max) are utilized in equation (2). Select R_1 and R_2 of the digital transistor from the below equation in order to exceed the output current I_{omax} .

$$\therefore I_{omax} \leq 20 \times ((V_{in} - 0.75)/(1.3 \times R_1) - 0.75/(1.04 \times R_2))$$

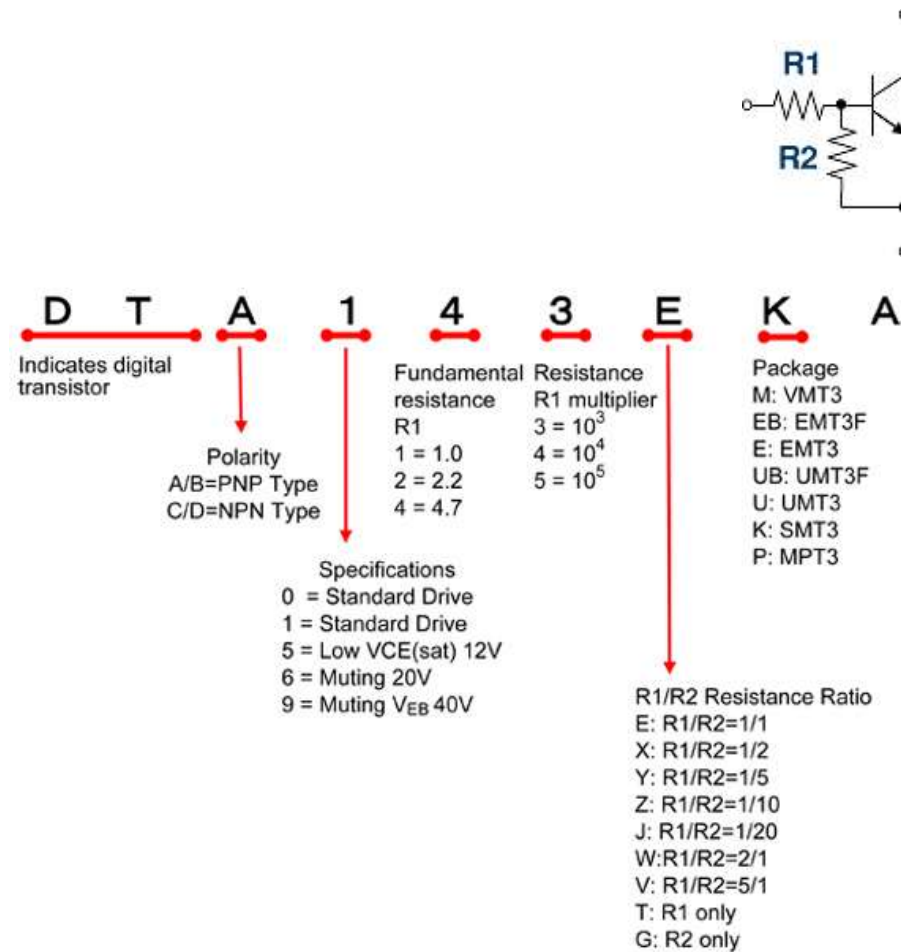Digital Transistor Part Number Explanation




The Difference Between I_o and I_c

I_c : The maximum theoretical current that can flow through a transistor

I_o : The maximum current that can be used for a digital transistor

Notes

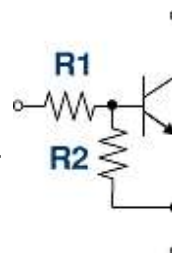The DTA/C series of digital transistors support 100mA of current flow. For these products, I_c is defined as 100mA. Connecting resistors R_1 and R_2 makes it a digital transistor. $I_c=100mA$ operation requires a high input voltage V_{in} to ensure sufficient base current I_B .



However, the maximum input voltage $V_{in(max)}$ is defined by the power tolerance (package power) of the input resistor R_1 , which is determined on the absolute maximum ratings. Therefore, since this rating may be

exceeded when $I_c=100\text{mA}$, I_o is defined as the current value that can flow through the digital transistors without exceeding $V_{in}(\text{max})$.

As you may know, the absolute maximum ratings stipulate that 2 or more parameters cannot be simultaneously supplied, so there is no problem with a notation using only I_c . However, I_o may also be listed in accordance with actual usage conditions.

From the above, after taking into account circuit design, I_o can be considered the absolute maximum rating.


The difference between G_I and h_{FE}

h_{FE} : DC current gain in general transistors

G_I : DC current gain in digital transistors

Notes

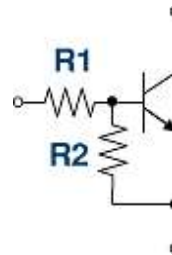G_I and h_{FE} both represent DC current gain in common-emitter configurations. Digital transistors are conventional transistors that incorporate 2 internal resistors.




Here since the DC current gain = output current/input current the gain is not reduced by the input resistor $R1$. Therefore, for types that integrate only an input resistor $R1$, gain is represented by h_{FE} , and will be equivalent to the h_{FE} of the configured transistor.

However, when connecting a resistor ($R2$) between the emitter and base, the input current is diverted away from the base and safely directed to the emitter. As a result, amplification is reduced. This value is represented as G_I .

The Difference Between $V_{I(\text{on})}$ and $V_{I(\text{off})}$


It is easy to mistake $V_{I(\text{on})}$ with $V_{I(\text{off})}$ and vice versa.

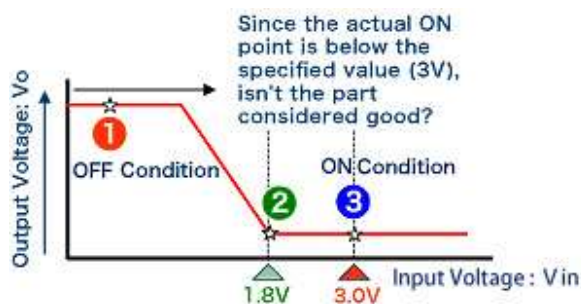$V_{I(\text{on})}$: The minimum voltage required to turn the transistor ON.



Common misunderstanding:

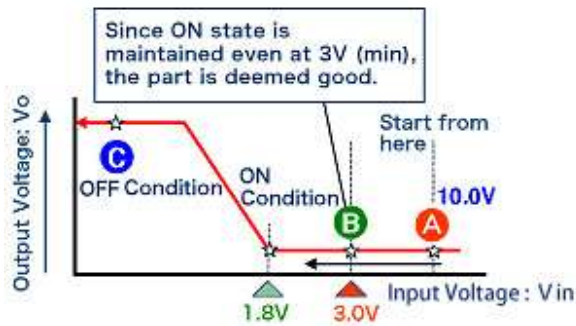- ① : The input voltage increases constantly from 0V
- ② : After a short time the voltage will reach 1.8V, turning the digital transistor ON
- ③ : Since this voltage is below the 3V listed in the specifications, it is considered no good.



Actual operation:


- A** : First, increase the input voltage V_{in} to a level sufficient to turn ON the transistor (i.e. 10V)
- B** : Gradually lower the voltage to the level noted in the specifications (i.e. 3V). If the transistor remains ON it is considered good.
- C** : Continue to decrease the voltage supplied to the base until the transistor turns OFF. Since this point is below 3V, the transistor works.

Digital Transistor Temperature Characteristics


V_{BE} , h_{FE} , R_1 , and R_2 will vary depending on the ambient temperature.

h_{FE} will change by: 0.5%/°C (approx.)

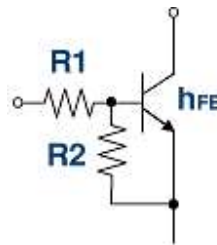V_{BE} will vary by around -2mV/°C (within the range of -1.8 to -2.4mV/°C)



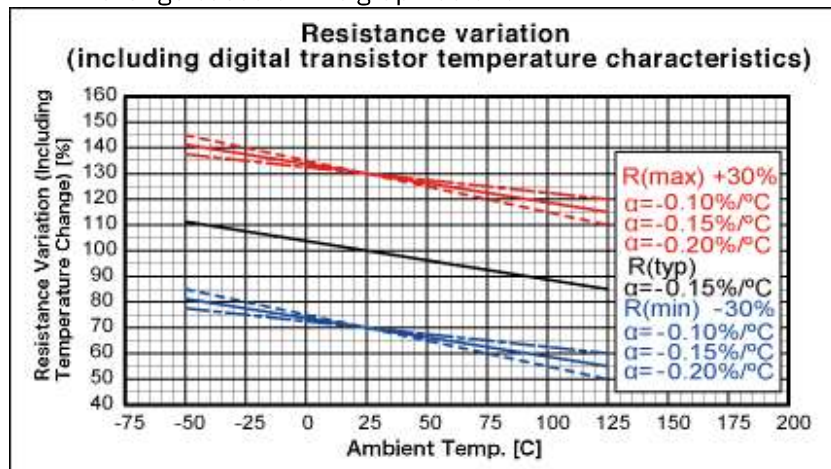R_1 will change based on the graph below.




Output Voltage - Output Current Characteristics in the Low-Current Region


The output voltage-output current characteristics of digital transistors are measured using the following method.

For DTC114EKA measurement is performed using $I_o/I_i = 20/1$

$i = I_B + I_{R2}$ from ($I_{R2} = V_{BE}/10k = 0.65V/10k = 65\mu A$)

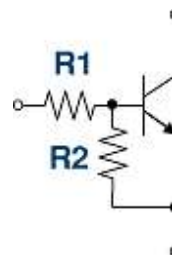If $I_B = I_i - I_{R2} = I_i - 65\mu A$ (if I_i becomes less than 65μA) I_B will not flow, and V_o [$V_{CE}(\text{sat})$] will increase. If this happens V_o cannot be measured in the low current region.



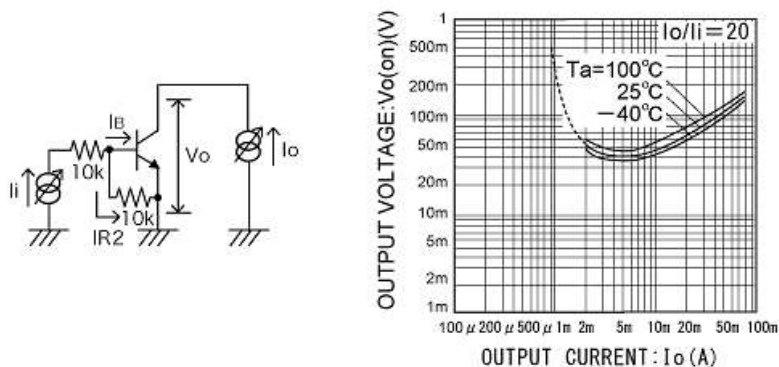

If the input current to the base is too small (for example, it cannot overcome the $65\mu\text{A}$ in the example above), then no current will flow through the base and thus the transistor will never conduct. This will cause the output voltage V_o ($V_{CE(sat)}$) to rise in the low current region

Digital Transistor Switching Operation

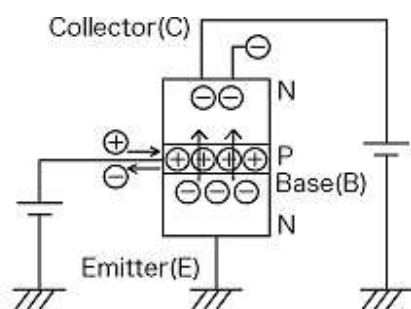


Figure 1

Transistor Operation

For NPN transistor operation, voltage is supplied as in Diagram 1. In this circuit, the base (B) - emitter (E) region is forward biased which results in current flow through the base. In other words, the base is injected with holes.

When this happens the free electrons in the emitter (E) are drawn towards the base. However, since the base region is extremely narrow, free electrons flow through the base region to the collector due to voltage bias from the collector. Because of this, current flows from the collector to the emitter.

⊕

Switching Operation

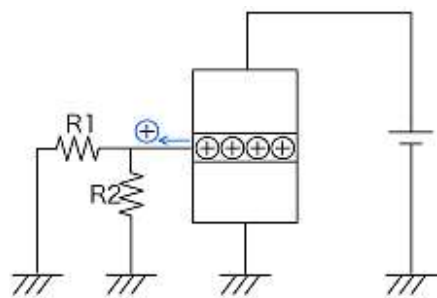


Figure 2

Transistor operation consists of both amplification and switching. During amplification, I_c , equivalent to h_{FE} times the base current, flows. The output current in the active region can be controlled by adjustment of the

input current.

Switching operation ensures saturation conditions while ON (smallest collector-emitter voltage possible). In this saturation region, there is an excessive number of \oplus holes, which then exit through the base terminal from the base region. Collector current flows until all of the \oplus holes exit from the base region. The time it takes for this to occur is referred to as t_{stg} (OFF time). The quicker the \oplus holes exit the base region the shorter the OFF time.

In digital transistors, R1 and R2 act in series as a path for the holes \oplus to exit the base region while the transistor is OFF. R2 should be made as small as possible (with a given fixed R1) in order to minimize OFF time.

Digital Transistor Terminology

- $V_{I(on)min}$: Minimum Input ON Voltage
Forward voltage V_o applied between the OUT and GND pins - the minimum input voltage required for output current (I_o) flow. Or the minimum input voltage needed to turn ON a digital transistor.
Therefore, since a voltage lower than this minimum input voltage is required to switch from ON to OFF, the value for actual products will be less than this.
- $V_{I(off)max}$: Maximum Input OFF Voltage
The maximum input voltage obtained between the IN and GND pins while supplying supply voltage V_{cc} and output current I_o between the OUT and GND pins. In other words, this is the maximum input voltage that will maintain an OFF condition.
However, since a voltage greater than this is required when turning the transistor from OFF to ON, the value for actual products will be higher.
- $V_{O(on)}$: Output Voltage
The output terminal voltage under any input conditions that do not exceed the maximum ratings. The condition where the IN/OUT junctions are forward biased and the output voltage is reduced when sufficient input current flows through the GND amplification circuit. Measured as an integer fraction of I_i (normally 10-20) in V_o , I_o .
- $I_{I(max)}$: Maximum Input Current
The maximum permissible input current that can continuously flow to the IN pin (while forward voltage V_i is supplied between the IN and GND pins).
- G_I : DC Current Gain
The I_o/I_i ratio stipulated in V_o , I_o .
- R1: Input Resistance
The resistance connected between the IN terminal and transistor Base, with a permissible range of $\pm 30\%$. This value will vary depending on the temperature.
- R2/R1: Resistance Ratio
The ratio of the internal Base-Emitter resistor to the input resistor.

Electronics Basics

What is a Transistor?

- Transistors Functions
- Outline of a Transistor
- Understanding Transistors
- Understanding the Principles of Digital Transistors
- Understanding MOSFET Characteristics
- ON Resistance
- Total Gate Charge
- Selecting Transistors to Ensure Safe Operation
- Calculating Transistor Chip Temperature
- What is a Load Switch?
- FAQ: Transistors

Technical Data

- Part Explanation
- Taping Specifications
- Storage Conditions

[Back](#) >>