

DC-DC Converter TPS5430: Description, Pinout, and Application

Electronic Component Parts Articles Author : Cecelia January-18-2022

General Description

TPS5430/TPS5431 **dc/dc converter** integrating high side N-channel MOSFETs with low resistance, which is designed to provide up to 3A output from an input voltage source of 5.5V to 36V (TPS5430) or 5.5V to 23V (TPS5431). The substrate includes a voltage error amplifier with high performance which is used to provide tight voltage regulation accuracy under transient conditions, an undervoltage lockout circuit used to prevent start-up until the input voltage reaches 5.5V, an internally programmed slow-start circuit designed to limit surge current, and a voltage feedforward circuit designed to improve transient response. It also provides a sensitive high enable, overcurrent protection, and thermal shutdown. It has a ninternal feedback compensation loop to reduce design complexity and external component count.

The **TPS5430**/TPS5431 devices are packaged in a thermally enhanced, easy-to-use 8-pin SOIC Power Strip[™]. TI offers evaluation modules and design software tools to help quickly implement high-performance power designs to meet intens e device development cycles. The TPS5430/TPS5431 has a switch enable pin with only 17µA quiescent current in the of state. Compared with other DC switching power conversion chips of the same type, the high conversion efficiency of T PS5430/TPS5431 is particularly noteworthy.

TPS5430/TPS5431 can be used to power the A/D conversion module and data processing module of the data acquisition system.

Introduction to TPS5430

(1) Features of TPS5430

TPS5430 has good characteristics, and its performance and main parameters are as follows:

High current output: 3A (peak 4A); Wide voltage input range: 5.5~36V;

High conversion efficiency: the best condition can reach 95%;

Wide voltage output range: the lowest can be adjusted down to 1.221V;

Internal compensation minimizes external component count;

Fixed 500kHz conversion rate;


With over-current protection and thermal shutdown function;

With switch enable pin, only 17uA quiescent current in an off state;

Compared with other DC switching power conversion chips of the same type, the high conversion efficiency of TPS5430 is particularly noteworthy.

The figure below shows the relationship between TPS5430 conversion efficiency and output current at 12V input voltage and 5V output voltage.


×

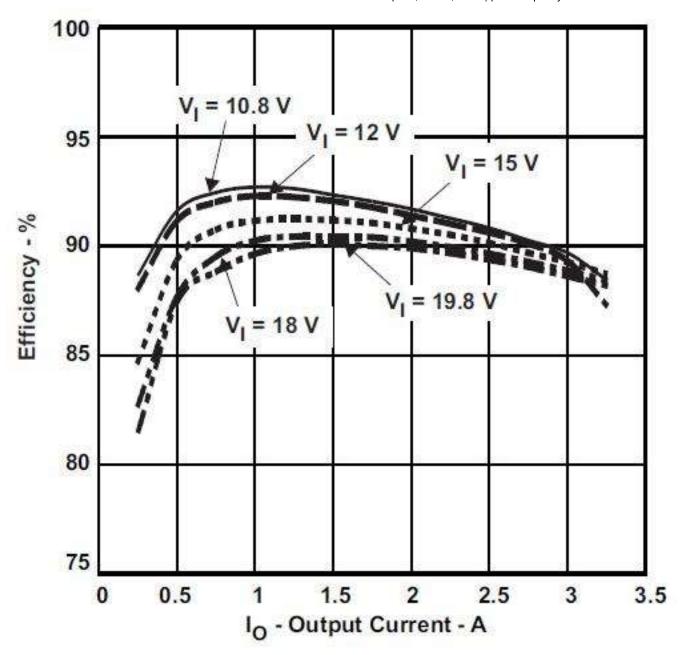

(2) Function and Structure

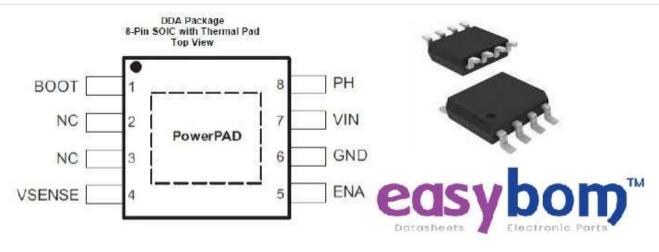a. Pin description

TPS5430 adopts 8-pin SO IC PowerPADTM package, and the form is as shown below.



PIN			
NAME	NO.	1/0	DESCRIPTION
воот	1	0	Boost capacitor for the high-side FET gate driver. Connect 0.01 µF low ESR capacitor from BOOT pin to Phipin.
NC	2,3	-	Not connected internally.
VSENSE	4		Feedback voltage for the regulator. Connect to output voltage divider.
ENA	5	- 1	On/off control. Below 0.5 V, the device stops switching. Float the pin to enable.
GND	6	770	Ground. Connect to PowerFAD.
VIN	7	77 5555	Input supply voltage. Bypass VIN pin to GND pin close to device package with a high quality, low ESR ceramic capacitor.
PH	8	. 1	Source of the high side power MOSFET. Connected to external inductor and diode
PowerPAD		5752	GND pin must be connected to the exposed pad for proper operation.

b. Internal structure and function

Oscillator frequency

A fixed slew rate of 500kHz results in a smaller output inductance for the same output ripple requirement.

② Reference voltage

Scale the temperature to stabilize the output range of a bandgap circuit, making the quasi-voltage system produce an ac curate reference signal. After testing, within the allowable temperature range, the bandgap and scaling circuit remain bal anced when the 1.221V voltage is output.

③ ENA (enable pin) and (SlowStart) internal soft-start

When the voltage on the pin ENA exceeds the limit voltage, the **converter** and the internal soft-start begin working, and when the voltage is lower than the limit voltage, the converter stops working and the soft-start begins resetting. The converter stops working when the pin ENA is grounded or the voltage is less than 015V. The ENA pin can be left floating.

④ UVLO (Under Voltage Lockout)

TPS5430 has a UVLO circuit. No matter in the power-up or power-down process as long as V IN (input voltage) is lower than the limit voltage, the conversion chip does not work. The typical hysteresis value of the UVLO comparator is 330m V.

⑤ Boost Capacitor (start capacitor)

Connect a 0.01µF ceramic capacitor between the BOOT pin and the PH pin to provide the gate voltage for the high side of the **MOSFET**.

® VSENSE (external feedback) and Internal Compensation (internal compensation)

The output voltage is fed back to the VSENSE pin through an external resistor divider. In a steady-state, the voltage of the VSENSE pin is equal to the voltage reference value of 1.221V. The TPS5430 has an internal compensation circuit, which simplifies the chip design.

⑦ Voltage Feed Forward

The internal voltage positive feedback ensures that the power chip has a constant gain no matter how the input voltage. We use cookies to offer you a better experience. Detailed information on the use of cookies on this website is provided in our Privacy Policy. By using this site, you consent to the use of our cookies.

S5430 is typically 25.

® Pulse - Width - Modulation Control

The converter adopts a fixed frequency control method.

Overcurrent Protection

The overcurrent protection circuit makes the internal overcurrent indicator set to true when the current exceeds the limit value, and the overcurrent protection is triggered.

1 Thermal Shutdown

The junction temperature exceeds the temperature shutdown point, the voltage parameter is set to ground, and the high -side MOSFET turns off. Controlled by the soft-start circuit, when the contact temperature drops to 14°C lower than the t emperature shutdown point, the chip restarts.

Application of TPS5430

In the power supply design process, the design parameters should be determined first according to the work requirements, and then the circuit and peripheral components should be designed according to the parameters.

(1) Design parameter requirements


Input voltage range: 10.8~19.8V;

Output voltage: 5V;


Input ripple voltage: 300mV; Output ripple voltage: 30mV; Output rated current: 3A.

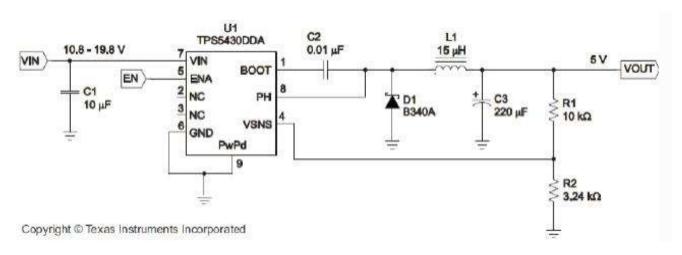(2) Application circuit

The power supply design of this system selects the classic circuit of TPS5430, as shown in the figure below.



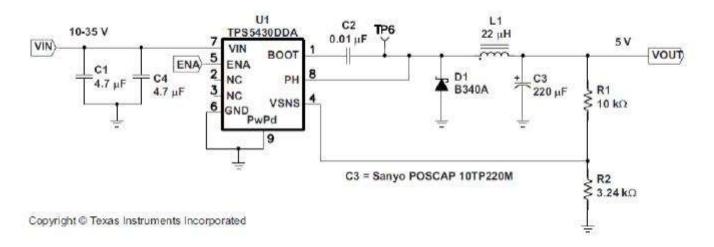5V output voltage application circuit diagram



5V output voltage application circuit diagram under wide voltage input

(3) Selection of components

①Input capacitor

The TPS5430 requires a slightly larger decoupling capacitor. A high-performance ceramic capacitor of 10µF (C1) is recommended here. Smaller capacitors can also be selected, subject to the input voltage and rated current ripple requirements.

2 output filter device

The output filter device, namely L1, C2. TPS5430 has an internal compensation circuit. The output inductance is related to the maximum output current, and a 15µH inductor is selected here.

Output capacitance is an important design factor that affects voltage rating, ripple current rating, and equivalent resistan ce (ESR). In this application, a $220\mu\text{F}$ output capacitor is selected. At this time, the RMS ripple current generated in the circuit is 143mA, and the maximum ESR required is $40\text{M}\Omega$.

③ Output voltage setting

The output voltage is determined by the resistors (R1, R2) of the VSENSE pin. If the output voltage is 5.0V, the reference voltage is 1.221V, and R1 is $10k\Omega$, then R2 is determined to be $3.24k\Omega$.

$$R2 = \frac{R1 \times 1.221}{V_{OUT} - 1.221}$$

④ BOOT capacitor

BOOT capacitor C2 select 0.01µF.


⑤ Capture diode

TPS5430 needs an external capture diode, choose B340A, its reverse voltage is 40V, forward current is 3A, and forward voltage is 0.5V.

TI recommends the circuit board wiring and component placement diagram of the 10.8~19.8V input to 5V output voltage of the TPS5430, as shown in the figure.

In the circuit board design process of TPS5430, the design principles of general power conversion chip circuits should be followed to achieve the expected results. There are two other things to note:

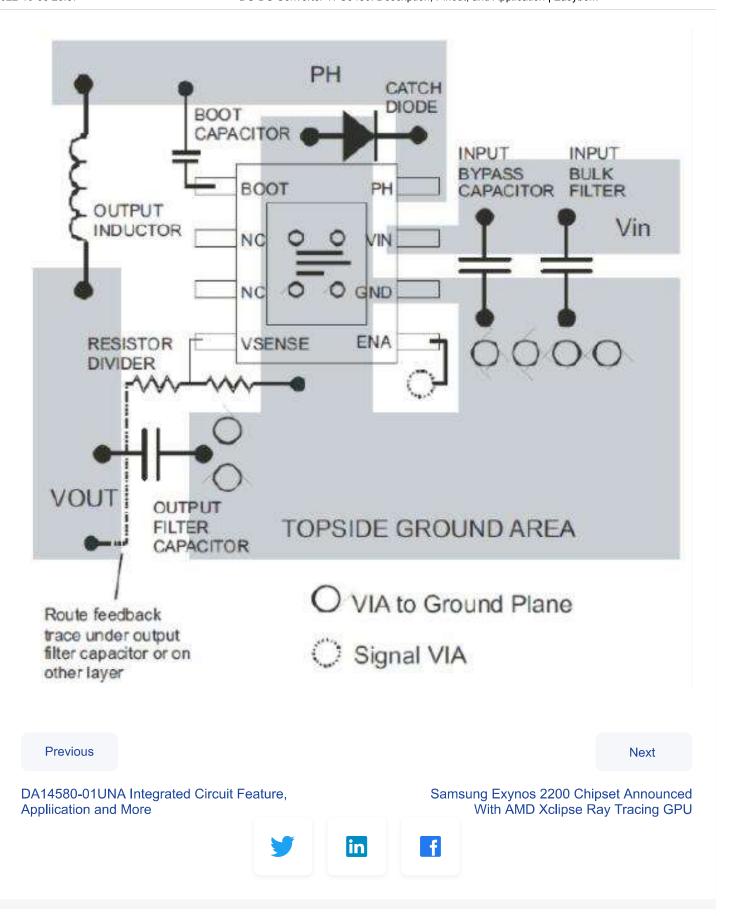① PowerPAD is required to be connected to the ground. The Pads can be placed directly under the chip, and vias can be drilled to facilitate heat dissipation.



Related reading



MAX232 IC: Pinout, Datasheet, Equivalent, and Circuit

Electronic Component Parts Articles

Author: Anita March-21-2022

The MAX232 IC is a type of dual receiver. It is used for TTL/CMOS to RS232 conversion. Most microcontrollers operate on TTL/CMOS logic. Therefore, it communicates through either 0V or +5V.

Read More >




TPA3118D2 Amplifier: #TOP 10 Best Amplifier

Electronic Component Parts Articles

Author: Anita February-25-2022

The TPA3118D2 is a stereo-efficient, digital amplifier. The high efficiency of the unit allows it to run 2 x 15W without an external heat sink on one layer of PCB. It can run without a heat sink on a 2 \times 30 W / 8 Ω dual-layer PCB.

Read More >

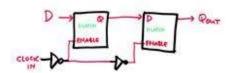

CD4042BE D Latch: What You Need to Know

Electronic Component Parts Articles

Author: Anita February-22-2022

The CD4042BE is a kind of d latch. The types include four latch circuits that are being triggered by a common timer. The outputs of the buffered version are also available in each circuit.

Read More >



Publish your ideas...

Name* Name

E-mail* E-mail

Press Enter to publish or

Publish

Hot Labels

Edge computing

Machine vision

artificial intelligence

The third generation semiconductor

Test and measurement

LT1085

Core-making

infrastructure

wifi 7

Thyristors

Popular Posts

What is an Electrolytic Capacitor

September-16-2021

An analysis of resistor color code

August-25-2021

PC817 Optocoupler Datasheet, Pinout, Circuits, Arduino Examples

January-19-2022

How to Test an Inductor Using a Multimeter?

November-2-2021

How to Tell if Your Ceiling Fan Capacitor is Bad

October-16-2021

SR621SW Battery: What is the SR621SW Battery Equivalent?

March-2-2022

How to Tell if a Coil Has an Internal Resistor

October-18-2021

LR44 Battery Equivalent: What Battery is Equivalent to LR44?

April-1-2022

JRC4558 Dual Operational Amplifier: Equivalent, Pinout, Circuit, and Datasheet

March-15-2022

ATMEGA328P Microcontroller: Datasheet, Pinout, Equivalent, ATMEGA328P Arduino

April-14-2022

Recommended Parts

More >

Popular Parts

CMF60500R00BEEK 824-22-001-00-005000

LX8117-33CDD 97-3107A18-22P-417-940

BFC237051223 7211L2Y9CBE

TMM-103-04-S-S-SM-P-TR TVP00DT-25-19JA-LC

SDR0503-122JL MTMM-122-05-G-D-078

1856740000

View More ∨

