What is Contactor and how it's Works

Last update : year ago 3 Minutes to read

table of contents



Contactor

What is Contactor and how it's Works

Welcome, visitors and followers of the Electron Tips blog. In today's topic, we will learn about the most important element in electricity, especially the automatic control electricity, which is the Contactor, so what is the Contactor? And how does the contactor work? And what are the components of the contactor?

Contactor definition

The contactor is an electromagnetic switch, as it has an electric file that controls the connection and disconnection of the power circuit, and the contactor element is used to control electric motors and pumps, by executing many types of operation, and these are the most important types of operation in which the contactor device is used.

Direct start .


start star delta.

Soft start.

Each type of operation has advantages, but it is widely used according to the type of electric motor, and the purpose for which it was designed, but this is not our topic today, as we will limit ourselves in this topic to getting to know what is the definition of a contactor, its working principle, as well as its internal structure, and In another topic, we will explain the types of operating systems for single and three-phase electric motors, and what is the benefit of each of them.


Contactor Symbol:

This is the Contactor Symbol:

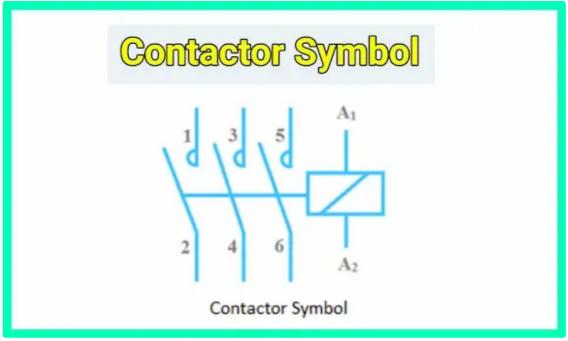

Contactor Symbol

Contactor components:

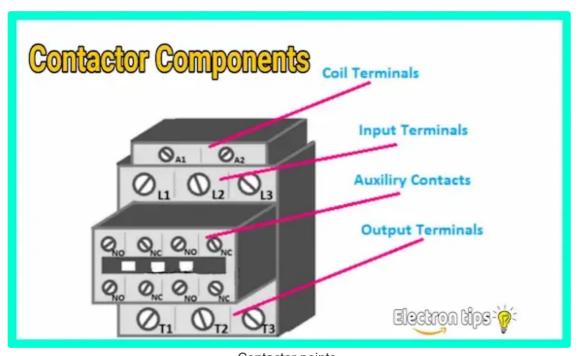

Contactor points


In general, the work of the contactor is similar to the way the relay complex works, but the contactor is mostly available at three main entrances and exits, and this is numbered, respectively, with: 1.3.5 for the entrances and 2.4.6 for the exits, in addition to another outlet called the auxiliary contact point. It is used for control, and we have the option to install

separately from the contactor, and it is recorded on the auxiliary points of the contactor (13,14), and is often open in the normal state ON. And also closed points written on it (11,12), in addition to To the fixed iron mold, and another moving end that allows the contact of the contactor at the moment his file is lunched, and he returns to his place when the feeding is separated by a pulsating action.

The working principle of the contactor

The control circuit allows feeding the coil of the contactor device, which results in the attraction and connection of the main points of the contactor device, thus closing the open auxiliary points and opening the closed points, which leads to the passage and flow of electric current to the load, a pump or an electric motor.

The internal structure of the contactor:

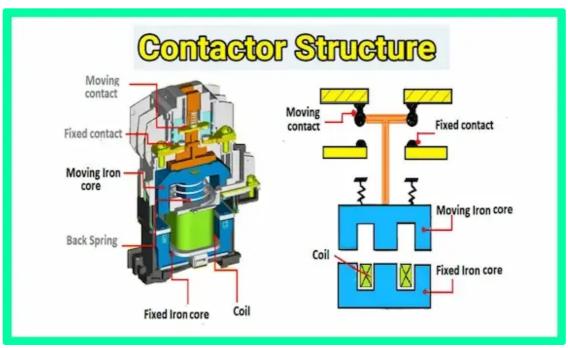

Contactor Structure

compound This image shows all the components and structure of the contact element, which is the basis for the operation and control of electric motors and pumps. 110V, 220V, 380V.

Conclusion:

In the end, this was a simple explanation of the components and the working principle of the contactor device, in addition to illustrative pictures of this electrical compound. If you have any questions or inquiries about this topic or something else related to this field, you can ask it in the comments section or on our Facebook page Electrical Engineering Tips.