

March 20, 2015

# 7V to 25V Input with 5V and 1.5A Output Buck Converter Design Using LT1376-5 Controller

This design reference is for 7V to 25V input with 5V and 1.5A output buck converter using LT1376-5 controller. LT1376-5 is monolithic buck mode switching regulator which has a fixed frequency of 500 kHz. The switching element is internal on the controller thus lower component count. The internal switch can able to handle 1.5A current. The controller can be used with a wide range of input voltage from 6V to 25V. The output is fixed to 5V. There is also an adjustable variant that will be discussed in another article. This design example is concentrating to 7V to 25V input with 5V and 1.5A output buck converter.

This controller uses high switching frequency so smaller inductor and output capacitor size is possible. It uses a current mode control mechanism for better and fast transient response and has a good loop stability.

## 1. Design Specifications

Vin : 7V to 25V


Vout : 5V fixed

$I_{out\_max} : 1.5A$

Output Ripple Voltage : 1% of the output voltage (peak to peak)
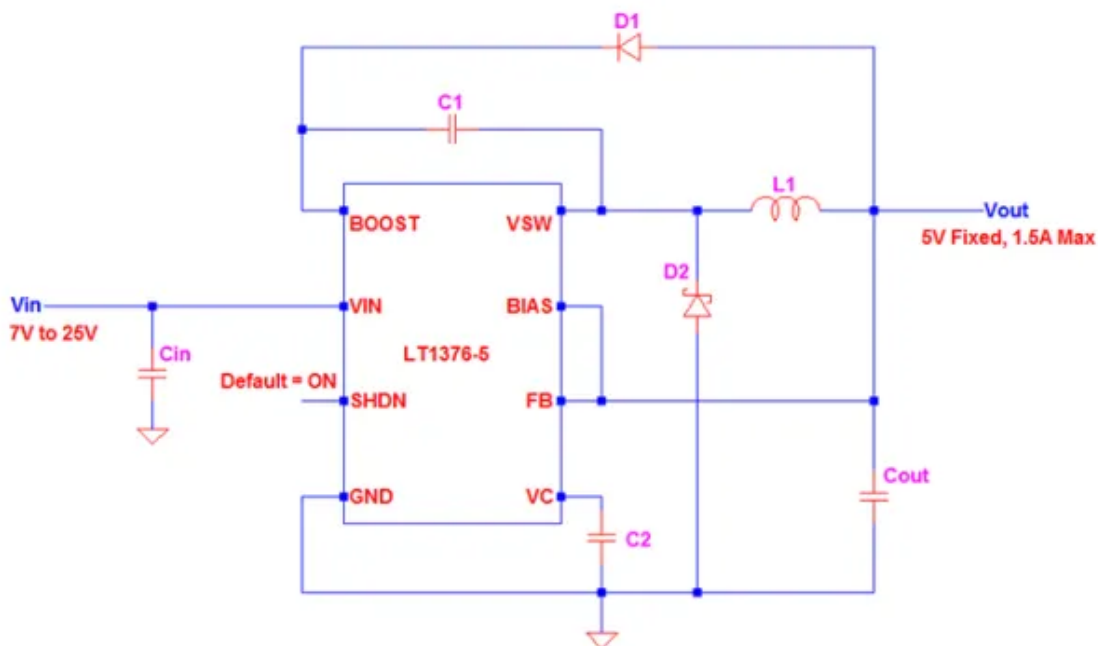
## 2. Circuit Schematic

Below is the circuit schematic of this design. For  $C_1$ , the recommended value is  $0.1\mu F$ . For  $C_2$ , the recommended value is  $3.3nF$ . We can use  $33\mu F$  for  $C_{in}$  as a starting value and just trim in your actual design if the response is not perfect for your needs. You can use a diode with a current rating of at least  $200mA$  for  $D_1$ , for instance 1N914. We will select  $L_1$ ,  $D_2$  and  $C_{out}$  based from the computation results and also check the stress on the controller.



## 3. Compute for Duty Cycle

We will compute the duty cycle for 7V and 25V inputs.

$$Duty_{7V} := \frac{V_{out} + V_D}{V_{in\_min} - V_{Q1} + V_D}$$

$$Duty_{7V} = 71.429\%$$

$$\text{Duty\_25V} := \frac{V_{\text{out}} + V_D}{V_{\text{in\_max}} - V_{Q1} + V_D}$$

$$\text{Duty\_25V} = 20\%$$

## 4. Frequency and Period

LT1376-5 Controller has a fixed 500 kHz switching frequency. The corresponding period is 2µsec.

$$F_{\text{sw}} := 500\text{kHz}$$

$$T_{\text{sw}} := \frac{1}{F_{\text{sw}}}$$

$$T_{\text{sw}} = 2\cdot\mu\text{s}$$

## 5. Compute for the Minimum Inductance

To compute for the minimum inductance, the inductor ripple current must be declared. A rule of thumb for ripple current is 20-40% of the load current. If you want a very small ripple, you must set it as low as possible. Let us use here 20% only.

$$di_{\text{assumed}} := 0.2 \cdot I_{\text{load}}$$

$$di_{\text{assumed}} = 0.3\text{ A}$$

Compute for the Inductance Value using 7V Input

$$L_{\text{value\_7V}} := \frac{\text{Duty\_7V} \cdot T_{\text{sw}} \cdot (V_{\text{in\_min}} - V_{\text{out}} - V_{Q1})}{di_{\text{assumed}}}$$

$$L_{\text{value\_7V}} = 9.524\cdot\mu\text{H}$$

Compute for the Inductance Value using 25V Input

$$L_{\text{value\_25V}} := \frac{\text{Duty\_25V} \cdot T_{\text{sw}} \cdot (\text{Vin\_max} - \text{Vout} - V_{\text{Q1}})}{di_{\text{assumed}}}$$

$$L_{\text{value\_25V}} = 26.667 \mu\text{H}$$

The computed minimum inductance at 25V input is to be used. If we will select the computed value using 7V input, the ripple at 25V input is high.

Let us use 27μH standard value inductor.

## 6. Recheck the Inductor Ripple Current using the Selected Inductor Value

$$di_{\text{actual\_25V}} := -\frac{\text{Duty\_25V} \cdot T_{\text{sw}} \cdot (V_{\text{Q1}} - \text{Vin\_max} + \text{Vout})}{L_{\text{value\_actual}}}$$

$$di_{\text{actual\_25V}} = 0.296 \text{ A}$$

$$di_{\text{actual\_7V}} := -\frac{\text{Duty\_7V} \cdot T_{\text{sw}} \cdot (V_{\text{Q1}} - \text{Vin\_min} + \text{Vout})}{L_{\text{value\_actual}}}$$

$$di_{\text{actual\_7V}} = 0.106 \text{ A}$$

With the selected inductance value, the maximum inductor ripple current is happening at the maximum input voltage.

## 7. Compute for the Peak Current

We will compute for the peak current of the switch, inductor and the diode. Their peak currents are the same.

$$I_{\text{max\_7V}} := I_{\text{load}} + \frac{di_{\text{actual\_7V}}}{2}$$

$$I_{\text{max\_7V}} = 1.553 \text{ A}$$

$$I_{\text{max\_25V}} := I_{\text{load}} + \frac{di_{\text{actual\_25V}}}{2}$$

$$I_{\text{max\_25V}} = 1.648 \text{ A}$$

## 8. Check the Operation Mode

For applications that are requiring smaller ripple current, CCM mode is more applicable. In CCM mode the inductor current is not touching zero in any switching cycle. In order to know of the operation is CCM, the minimum value of the inductor current must be above zero.

$$I_{\min\_7V} := I_{\max\_7V} - di\_actual\_7V$$

$$I_{\min\_7V} = 1.447 \text{ A}$$

$$I_{\min\_25V} := I_{\max\_25V} - di\_actual\_25V$$

$$I_{\min\_25V} = 1.352 \text{ A}$$

The minimum inductor current is above zero using minimum and maximum input voltage. The operation is CCM indeed.

## 9. Check the Diode Current

DC Value

$$I_{DC\_diode\_7V} := \frac{di\_actual\_7V \cdot (1 - Duty\_7V)}{2} + (I_{\max\_7V} - di\_actual\_7V) \cdot (1 - Duty\_7V)$$

$$I_{DC\_diode\_7V} = 0.429 \text{ A}$$

$$I_{DC\_diode\_25V} := \frac{di\_actual\_25V \cdot (1 - Duty\_25V)}{2} + (I_{\max\_25V} - di\_actual\_25V) \cdot (1 - Duty\_25V)$$

$$I_{DC\_diode\_25V} = 1.2 \text{ A}$$

RMS Value

$$I_{\text{RMS\_diode\_7V}} := \sqrt{1 - \text{Duty\_7V}} \cdot \left( I_{\text{max\_7V}} - \text{di\_actual\_7V} + \frac{\sqrt{3} \cdot \text{di\_actual\_7V}}{3} \right)$$

$$I_{\text{RMS\_diode\_7V}} = 0.806 \text{ A}$$

$$I_{\text{RMS\_diode\_25V}} := \sqrt{1 - \text{Duty\_25V}} \cdot \left( I_{\text{max\_25V}} - \text{di\_actual\_25V} + \frac{\sqrt{3} \cdot \text{di\_actual\_25V}}{3} \right)$$

$$I_{\text{RMS\_diode\_25V}} = 1.362 \text{ A}$$

## 10. Select a Diode

The maximum RMS current of the diode is only 1.35A. We will use here SSC54. This diode has a rated current of 5A and a voltage of 40V. Its maximum junction temperature is 150°C.

ELECTRICAL CHARACTERISTICS (T <sub>A</sub> = 25 °C unless otherwise noted)								
PARAMETER	TEST CONDITIONS		SYMBOL	SSC53L		SSC54		UNIT
				TYP.	MAX.	TYP.	MAX.	
Maximum instantaneous forward voltage <sup>(1)</sup>	5.0 A	T <sub>J</sub> = 25 °C	V <sub>F</sub>	0.42	0.45	0.45	0.49	V
		T <sub>J</sub> = 125 °C		0.33	0.38	0.36	0.42	
Maximum reverse current at rated V <sub>R</sub> <sup>(2)</sup>		T <sub>J</sub> = 25 °C	I <sub>R</sub>	-	0.7	-	0.5	mA
		T <sub>J</sub> = 125 °C		45	65	40	60	

### Notes

<sup>(1)</sup> Pulse test: 300 μs pulse width, 1 % duty cycle

<sup>(2)</sup> Pulse test: Pulse width ≤ 40 ms

THERMAL CHARACTERISTICS (T <sub>A</sub> = 25 °C unless otherwise noted)				
PARAMETER	SYMBOL	SSC53L	SSC54	UNIT
Typical thermal resistance <sup>(1)</sup>	R <sub>θJA</sub>	60		°C/W
	R <sub>θJL</sub>	20		

### Note

<sup>(1)</sup> Aluminum substrate mounted

The maximum power dissipated by the diode is

$$V_{F\_max} := 0.49 \text{ V}$$

$$P_{\text{diss\_diode}} := I_{\text{RMS\_diode\_25V}} \cdot V_{F\_max}$$

$$P_{\text{diss\_diode}} = 0.667 \text{ W}$$

Considering the design is exposed to a 60°C maximum ambient temperature, the de-rated power capability of the diode is

$$T_{j\_max} := 150\Delta^{\circ}\text{C} \quad T_{a\_max} := 60\Delta^{\circ}\text{C} \quad R_{thja} := 60 \frac{\Delta^{\circ}\text{C}}{\text{W}}$$

$$P_{diss\_capability\_60C} := \frac{T_{j\_max} - T_{a\_max}}{R_{thja}}$$

$$P_{diss\_capability\_60C} = 1.5 \text{ W}$$

The power stress of the diode at maximum operating ambient temperature is

$$P_{stress\_diode} := \frac{P_{diss\_diode}}{P_{diss\_capability\_60C}}$$

$$P_{stress\_diode} = 44.497\%$$

## 11. Check the Switch Current

DC Value

$$I_{DC\_switch\_7V} := \frac{Duty\_7V \cdot di\_actual\_7V}{2} + Duty\_7V \cdot (I_{max\_7V} - di\_actual\_7V)$$

$$I_{DC\_switch\_7V} = 1.071 \text{ A}$$

$$I_{DC\_switch\_25V} := \frac{Duty\_25V \cdot di\_actual\_25V}{2} + Duty\_25V \cdot (I_{max\_25V} - di\_actual\_25V)$$

$$I_{DC\_switch\_25V} = 0.3 \text{ A}$$

RMS Value

$$I_{\text{RMS\_switch\_7V}} := di\_actual\_7V \cdot \sqrt{\frac{\text{Duty\_7V}}{3}} + (Imax\_7V - di\_actual\_7V) \cdot \sqrt{\text{Duty\_7V}}$$

$$I_{\text{RMS\_switch\_7V}} = 1.275 \text{ A}$$

$$I_{\text{RMS\_switch\_25V}} := di\_actual\_25V \cdot \sqrt{\frac{\text{Duty\_25V}}{3}} + (Imax\_25V - di\_actual\_25V) \cdot \sqrt{\text{Duty\_25V}}$$

$$I_{\text{RMS\_switch\_25V}} = 0.681 \text{ A}$$

From the datasheet, the minimum switch current limit is 1.5A for duty cycle less than 50% while 1.35A for duty cycle equal to 80%. Since the maximum computed duty cycle is 71%, we will use 1.35A as the reference.

PARAMETER	CONDITIONS	MIN	TYP	MAX	UNITS
Switch Current Limit $V_{\text{BOOST}} = V_{\text{IN}} + 5V$	$V_C$ Open, $V_{\text{FB}} = 2.1V$ or $V_{\text{SENSE}} = 4.4V$ , DC ≤ 50%	1.50	2	3	A
	DC = 80%	1.35		3	A

The maximum computed switch current is only 1.272A, so the current limit will not hit and the converter can operate normally.

## 12. Check the Inductor Current

### RMS Current

$$I_{\text{RMS\_inductor\_7V}} := \frac{di\_actual\_7V}{\sqrt{3}} + Imax\_7V - di\_actual\_7V$$

$$I_{\text{RMS\_inductor\_7V}} = 1.508 \text{ A}$$

$$I_{\text{RMS\_inductor\_25V}} := \frac{di\_actual\_25V}{\sqrt{3}} + Imax\_25V - di\_actual\_25V$$

$$I_{\text{RMS\_inductor\_25V}} = 1.523 \text{ A}$$

### DC Current



$$I_{DC\_inductor\_7V} := I_{load}$$

$$I_{DC\_inductor\_7V} = 1.5 \text{ A}$$

$$I_{DC\_inductor\_25V} := I_{load}$$

$$I_{DC\_inductor\_25V} = 1.5 \text{ A}$$

## 13. Select Inductor

The chosen inductance value in section 5 is 27 $\mu$ H. The computed peak current through the inductor is 1.648A as derived in section 7 while the maximum RMS current is 1.523A. From the table below, we can use 27 $\mu$ H with a RMS and saturation current rating of 2A which give us around 25% margin.

Bourns Part No.	Inductance L ( $\mu$ H) $\pm 20\%$	DCR (m $\Omega$ ) Max.	I rms (A)	I sat (A)
SRP6540-R56M	0.56	4.4	18	18
SRP6540-R68M	0.68	5.0	16.5	17
SRP6540-R82M	0.82	5.5	15	15
SRP6540-1R0M	1.0	7.2	12	13.5
SRP6540-1R5M	1.5	10.0	11	11
SRP6540-2R2M	2.2	15.5	9	9
SRP6540-3R3M	3.3	23.0	6.5	7
SRP6540-4R7M	4.7	33.5	6	6.5
SRP6540-5R6M	5.6	38.0	5.5	6
SRP6540-6R8M	6.8	49.5	5	5.5
SRP6540-8R2M	8.2	50.5	4.5	5
SRP6540-100M	10	78.5	4	4
SRP6540-150M	15	121	2.9	2.9
SRP6540-220M	22	133	2.5	2.5
SRP6540-270M	27	290	2	2
SRP6540-390M	39	322	1.8	1.8
SRP6540-470M	47	366	1.6	1.6

## 14. Select the Minimum Output Capacitance Needed

$$V_{\text{ripple\_spec}} := 1\% \cdot V_{\text{out}}$$

$$V_{\text{ripple\_spec}} = 0.05 \text{ V}$$

$$C_{\text{out\_7V}} := \frac{d_{\text{i\_actual\_7V}} \cdot \frac{1}{F_{\text{sw}}}}{V_{\text{ripple\_spec}}}$$

$$C_{\text{out\_7V}} = 4.233 \mu\text{F}$$

$$C_{\text{out\_25V}} := \frac{d_{\text{i\_actual\_25V}} \cdot \frac{1}{F_{\text{sw}}}}{V_{\text{ripple\_spec}}}$$

$$C_{\text{out\_25V}} = 11.852 \mu\text{F}$$

We can use 33μF for more margin.

## 15. Final Schematic with Values

