

Diode Clampers Principle

A clamper adds a dc level to an ac voltage. Clampers are sometimes known as dc restorers. Below Figure shows a diode clamper that inserts a positive dc level in the output wave form. The operation of this circuit can be seen by considering the first negative half-cycle of the input voltage.

When the input voltage initially goes negative, the diode is forward biased, allowing the capacitor to charge to near the peak of the input ($V_{p(in)} - 0.7 \text{ V}$), as shown in Figure (a). Just after the negative peak, the diode is reverse-biased. This is because the cathode is held near $V_{p(in)} - 0.7 \text{ V}$ by the charge on the capacitor. The capacitor can only discharge through the high resistance of R_L . So, from the peak of one negative half-cycle to the next, the capacitor discharges very little. The amount that is discharged, of course, depends on the value of R_L .

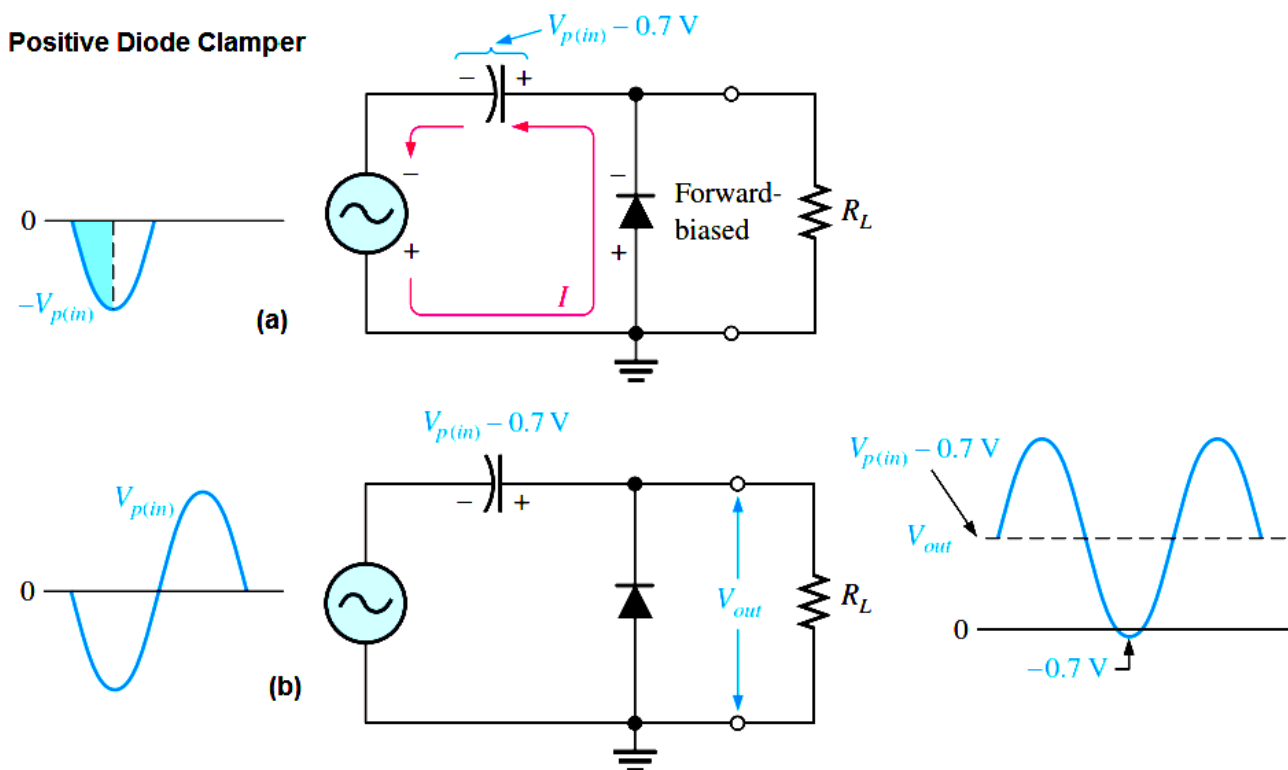


Fig : Positive Diode Clamper Operation

If the capacitor discharges during the period of the input wave, clamping action is affected. If the RC time constant is 100 times the period, the clamping action is