

How to Design an RC Snubber



Updated April 24, 2017 By Mike Wallace

A snubber is an electrical device that prevents voltage spikes due to sudden changes in current. These voltage spikes, or transients, can damage the circuit and cause arcing and sparks. One type of electrical snubber is the RC snubber, which is composed of a resistor in parallel with a capacitor. Transients are usually caused by switches in the circuit. When designing a snubber, you should design it with the characteristics of the switch in mind. The exact switch and its switching frequency must be known before designing the RC snubber.

Verify that the electrical switch is in the “Off” position and connected to a power source.

Measure the voltage across the switch by placing the voltmeter probes across the input and output terminals of the switch. Turn the switch to the “On” position and read the value on the voltmeter. This is the voltage across the switch. Write this value down.

Determine the maximum current that the switch can handle. This data is contained in the data sheet for the switch.

Calculate the minimum value for the resistor in the RC snubber by dividing the voltage across the switch by the maximum current rating. For example, suppose the voltage

measurement is 160 volts and the maximum current is 5 amps. Dividing 160 volts by 5 amps gives you 32 ohms. Your snubber must use a resistor that has a minimum resistance of 32 ohms.

Determine the switching frequency, in switches per second. For example, suppose the switch changes states 50,000 times per second, or 50 KHz. This value is determined by the designers of the circuit, and should be available in the circuit documentation.

Calculate the capacitance for the snubber by multiplying the switching frequency by the squared value of the voltage measurement acquired in Step 2. Take the inverse of this number (i.e. divide 1 by the value). For example, given a switching frequency of 50 KHz and a voltage of 160 volts, your equation looks like this:

$$C = 1 / (160^2) * 50,000 = 780 \text{ pF}$$

+ References

+ About the Author

+ Photo Credits

[Science](#)[About Us](#)[Math](#)[Accessibility Statement](#)[Projects](#)[Terms of Use](#)[News](#)[Privacy Policy](#)[Copyright Policy](#)[Contact Us](#)[AdChoices](#)

Copyright 2019 Leaf Group Ltd. / Leaf Group Media, All Rights Reserved.