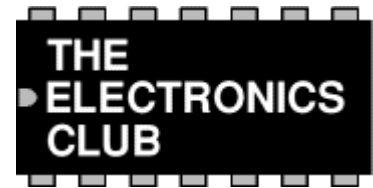


[Home](#) | [Map](#) | [Projects](#) | [Construction](#) | [Soldering](#) | [Study](#) | [Components](#) | [555](#) | [Symbols](#) | [FAQ](#) | [Links](#)

Simple Electronic Lock Project



A kit for this project is available from [RSH Electronics](#).

[Download PDF version of this page](#)

There are six (or more) push switches. To 'unlock' you must press all the correct ones at the same time, but **not** press any of the cancel switches. Pressing just one cancel switch will prevent the circuit unlocking. When the circuit unlocks it actually just turns on an LED for about one second, but it is intended to be adapted to turn on a relay which could be used to switch on another circuit.


Please Note: This circuit just turns on an LED for about one second when the correct switches are pressed. It does not actually lock or unlock anything!

This project uses a [555 monostable](#) circuit.


Parts Required

- resistors: 470, 100k ×2, 1M
 - capacitors: 0.1μF, 1μF 16V radial
 - red LED
 - 555 timer IC
 - 8-pin DIL socket for IC
 - on/off switch
 - push-switch ×6 (or more)
 - battery clip for 9V PP3
 - stripboard 12 rows × 25 holes
-

Stripboard Layout

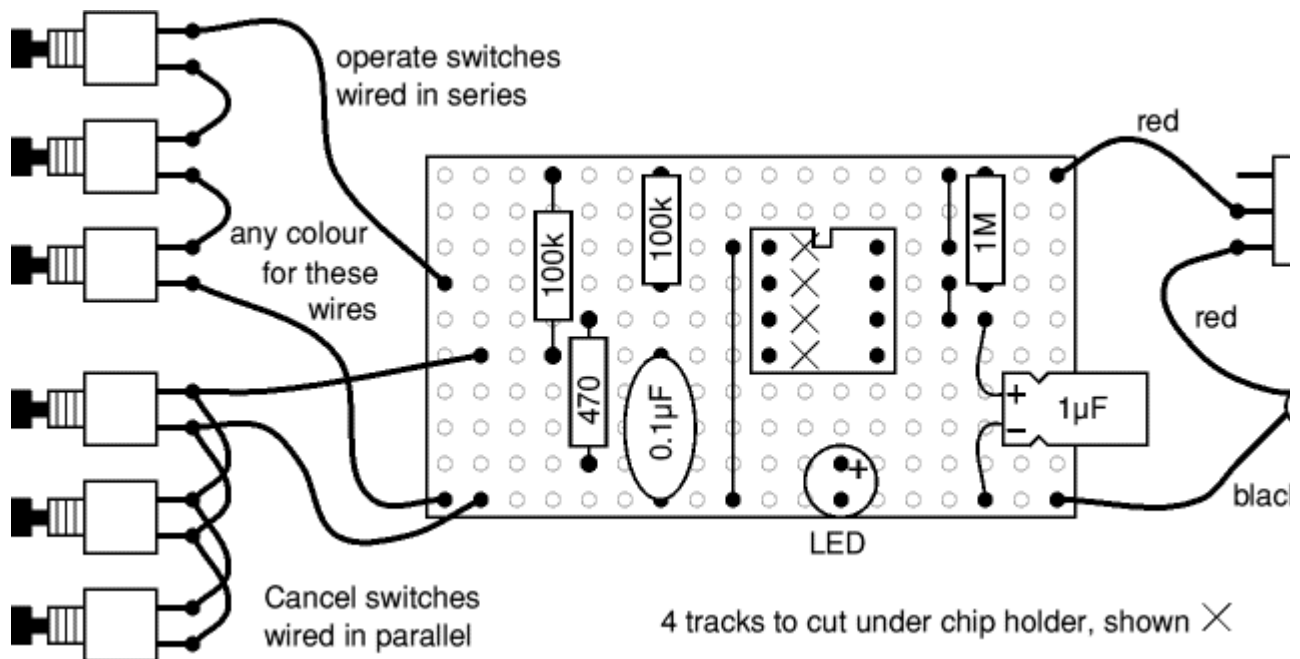

Circuit diagram

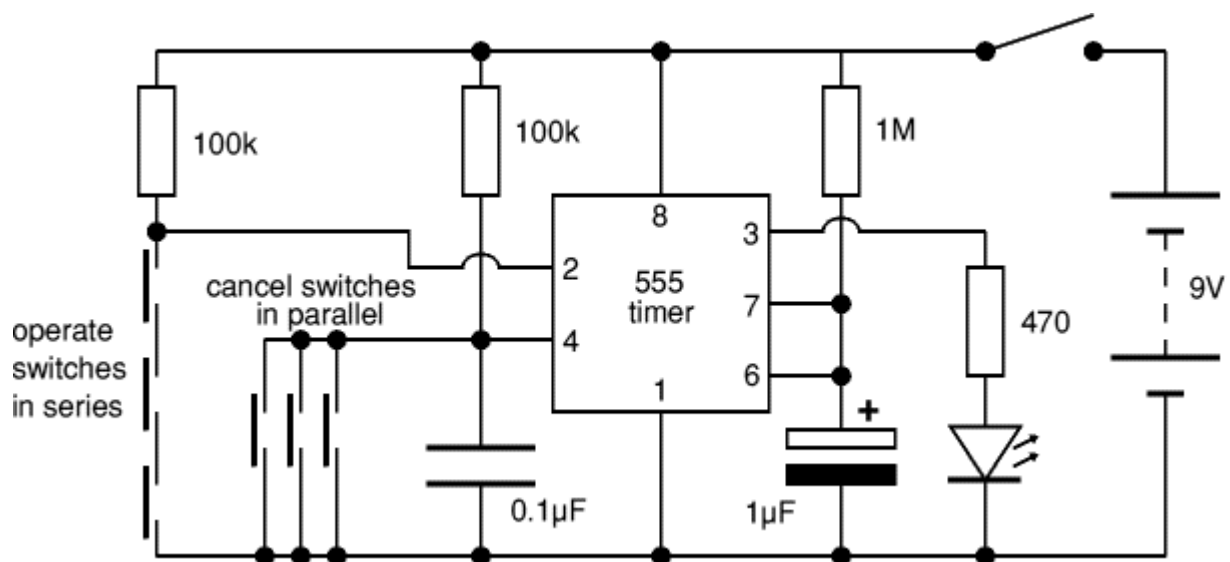

A kit for this project is available from [RSH Electronics](#). If you are new to electronics buying a kit is a good way to be sure you have the correct parts for the project.



[Return to Projects page](#)

- [Electronics Club Home Page](#)
- [Site Map](#)
- [Example Projects](#)
- [Construction of Projects](#)
- [Soldering Guide](#)
- [Study Electronics](#)
- [Electronic Components](#)



- [555 Timer](#)
- [Circuit Symbols](#)
- [Frequently Asked Questions](#)
- [Links to other Electronics sites](#)

© John Hewes 2007, The Electronics Club, www.kpsec.freeuk.com