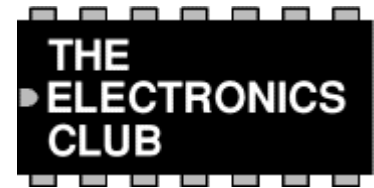


[Home](#) | [Map](#) | [Projects](#) | [Construction](#) | [Soldering](#) | [Study](#) | [Components](#) | [555](#) | [Symbols](#) | [FAQ](#) | [Links](#)


Valentine Heart Project



A kit for this project is available from [RSH Electronics](#).

[Download PDF version of this page](#)
[Download Valentine Heart template](#)

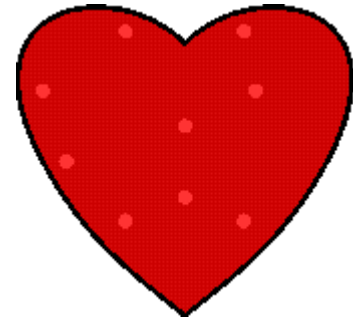This project flashes 18 LEDs at three different rates and you can use these to create an eye-catching Valentine Heart. The circuit is kept simple (and low cost) by using the 4060B chip which is a counter and oscillator (clock) in one package. The circuit requires a 9V supply, such as a PP3 battery. It will not work with lower voltages and a higher voltage will destroy the LEDs.



The preset variable resistor can be used to adjust the oscillator frequency and this determines the flash rate of the LEDs. The chip limits the current to and from its outputs so the LEDs can be safely connected without resistors in series to limit the current. The stripboard part of the circuit is easy to build but the wiring for the LEDs needs care so detailed instructions are provided below.

You can download our [Valentine Heart template](#) to print out and glue onto thick card, hardboard etc.

The Valentine Heart template is supplied as a PDF file. To view and print PDF files you need an Acrobat Reader which may be downloaded free for [Windows](#), [Mac](#), [RISC OS](#), or [UNIX/Linux](#) computers. If you are not sure which type of computer you have it is probably Windows.

Warning!


Using a battery (or power supply) with a voltage higher than 9V will destroy the LEDs.

You can see from the circuit diagram (below) that 6 LEDs are connected in series between the +9V supply and 0V. Each LED requires about 2V across it to light, so using a voltage of about 12V (= 6 × 2V) or more will make the LEDs conduct directly, regardless of the 4060B chip. With no series resistor to limit the current this will destroy the LEDs.

Parts Required

- resistors: 10k, 470k
 - preset: 47k (this could be 100k if necessary)
 - capacitor: 0.1µF
 - 4060B IC
 - 16-pin DIL socket for IC
 - LEDs × 18, 5mm diameter, red (or any mix of red, orange, yellow and green)
 - on/off switch
 - battery clip for 9V PP3
 - stripboard 13 rows × 18 holes
-

Stripboard Layout

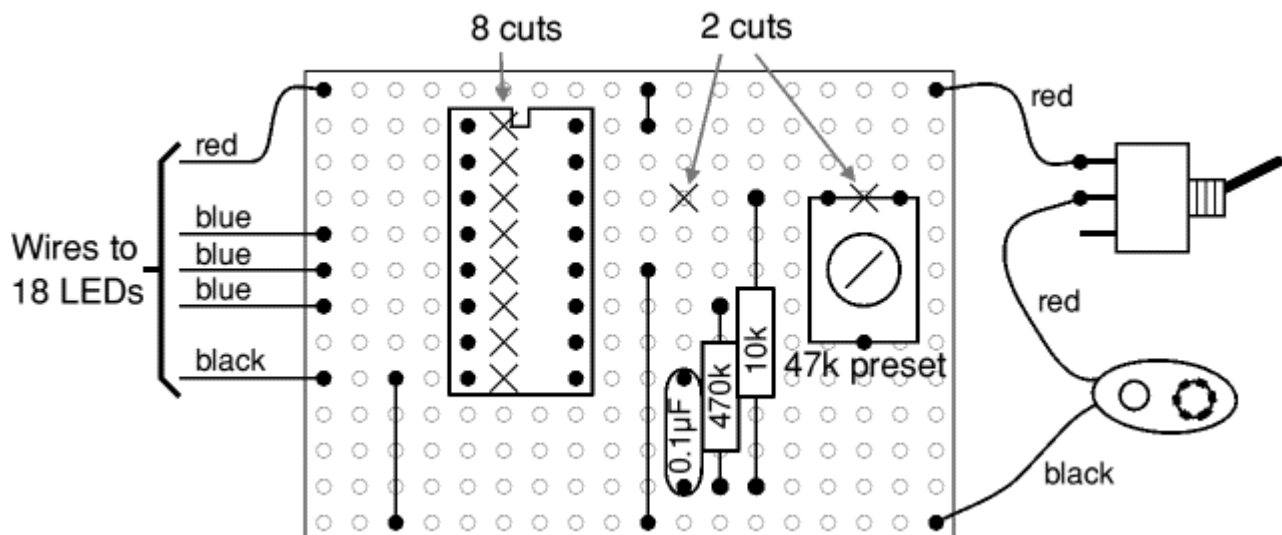

Building the Circuit

1. Begin by soldering the components onto the stripboard as shown in the diagram above. Do **not** insert the 4060B chip at this stage.


Arranging the LEDs:

2. Cut out a suitable shape from stiff card (or similar material), such as the [Valentine Heart](#) template. Paint or colour the card at this stage if necessary.
3. Plan the layout of the 18 LEDs (suggested positions are marked on the template).
4. Drill 5mm holes for the LEDs - put the card on a piece of scrap wood to do this without damaging the card or the table.
5. Push LEDs into the holes, they should be a fairly tight fit and glue should not be necessary.
6. Label the LEDs D1 - D18 at random on the back of the card.

Wiring of the LEDs:


Use stranded wire for all the connections to the LEDs and solder all wires near to the LED body so the leads can be trimmed short later on.

The wire colours are suggested to avoid confusion but you can use other colours if you wish, the electricity won't mind! For example you could use red and black as suggested but substitute yellow and white for the blue and green suggested.

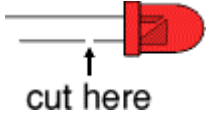7. Cut all the LED short leads to be very short to make identification easier:
 
8. Connect **RED** wire to link up all the LONG leads of D1, D2 and D3. Remember to solder wires near to the LED body so the long lead can be trimmed short later on.
9. Connect **BLACK** wire to link up all the SHORT leads of D16, D17 and D18.
10. Use 3 pieces of **BLUE** wire to connect:
 - o D7 short - D10 long
 - o D8 short - D11 long

- D9 short - D12 long
- 11. Use 12 pieces of **GREEN** wire to connect:
 - D1 short - D4 long
 - D4 short - D7 long
 - D2 short - D5 long
 - D5 short - D8 long
 - D3 short - D6 long
 - D6 short - D9 long
 - D10 short - D13 long
 - D13 short - D16 long
 - D11 short - D14 long
 - D14 short - D17 long
 - D12 short - D15 long
 - D15 short - D18 long
- 12. Connect the **RED** wire from the circuit board to the **RED** wiring on the Valentine heart (connect it to any convenient point).
- 13. Connect the **BLACK** wire from the circuit board to the **BLACK** wiring on the Valentine heart (connect it to any convenient point).
- 14. Connect the 3 **BLUE** wires from the circuit board to each of the 3 **BLUE** wires on the Valentine heart, they may be connected in any order.
- 15. Carefully check all wiring.
- 16. Trim the long LED leads.
- 17. Plug the 4060B into its holder.
- 18. Connect a 9V battery and switch on.
- 19. Using a small screwdriver, adjust the 47k preset variable resistor to give a suitable flash rate for the LEDs.

Circuit diagram

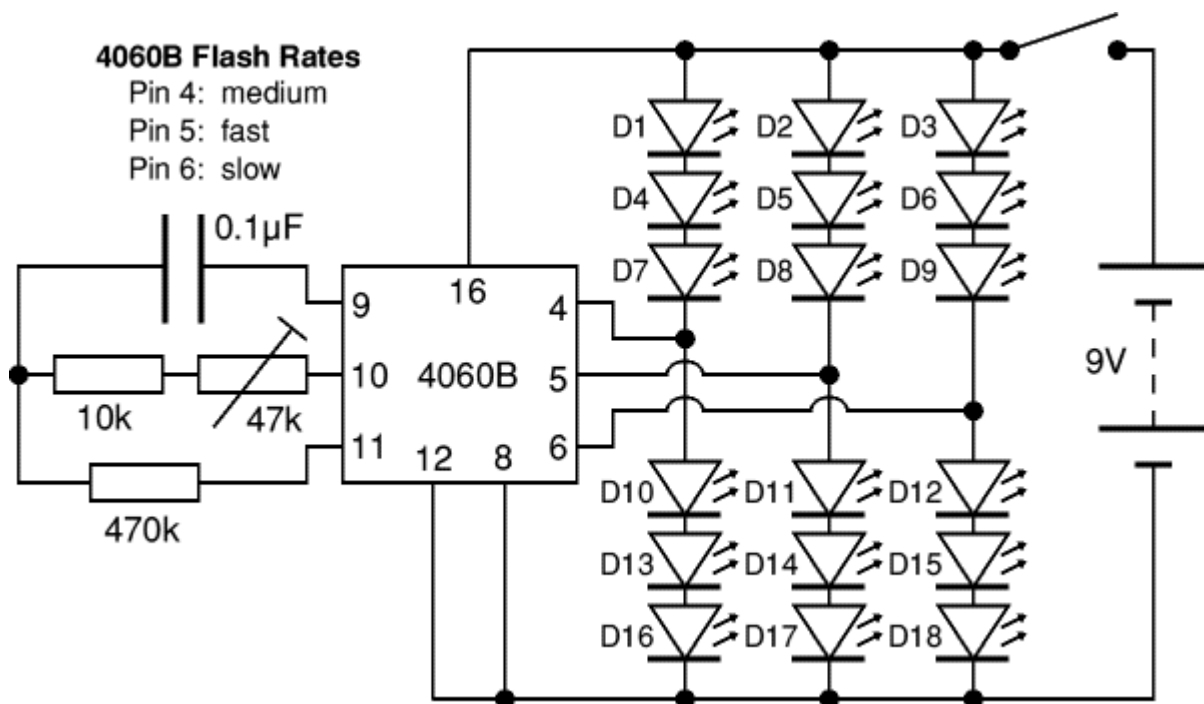

A kit for this project is available from [RSH Electronics](http://www.kpsec.freeuk.com/projects/valentine.htm).
 If you are new to electronics buying a kit is a good



way to be sure you have the correct parts for the project.

[Return to Projects page](#)

- [Electronics Club Home Page](#)
- [Site Map](#)
- [Example Projects](#)
- [Construction of Projects](#)
- [Soldering Guide](#)
- [Study Electronics](#)
- [Electronic Components](#)
- [555 Timer](#)
- [Circuit Symbols](#)
- [Frequently Asked Questions](#)
- [Links to other Electronics sites](#)



© John Hewes 2007, The Electronics Club, www.kpsec.freeuk.com