

Laboratory 2

8-bit pipelined ADC

2004-05-05

Homework

1. The reference voltage for each stage is $\pm 0.5 \cdot V_{ref} = \pm 0.25V$
2. The sampling accuracy is: $\frac{1}{2} LSB = \frac{1}{2} \cdot \frac{1}{2^7} = 3.9mV$. The accuracy required of the first stage multiplication is: $V_{out} = 2V_{in} \pm \frac{1}{2} LSB \Rightarrow MA = \pm \frac{1}{2} \cdot \frac{LSB}{2V_{in}} = \pm 0.195\%$

Part 1: Designing the pipelined ADC

The symbolic design of one out of seven cascaded stages in the pipelined ADC.

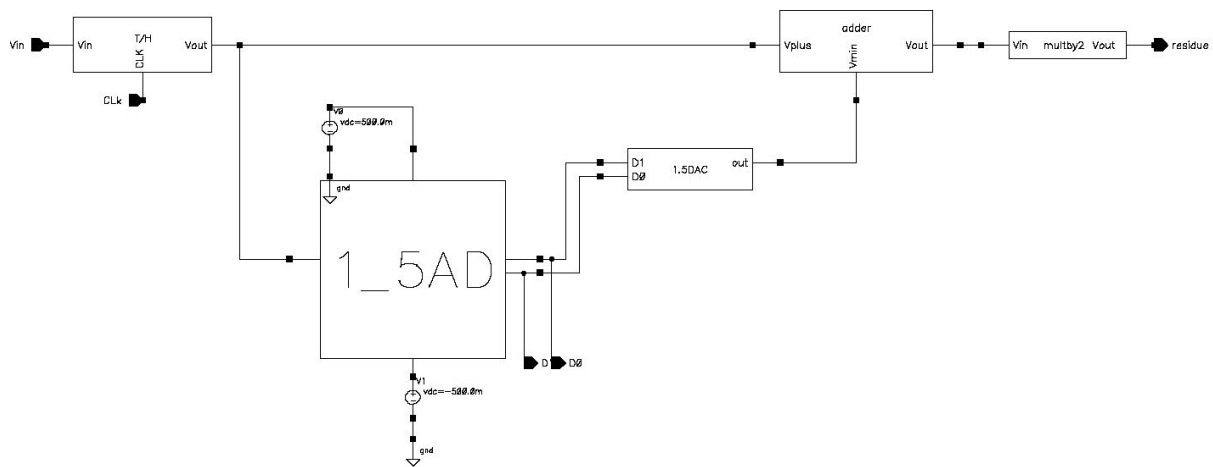


Fig 1.

The schematic for the 1.5bit ADC

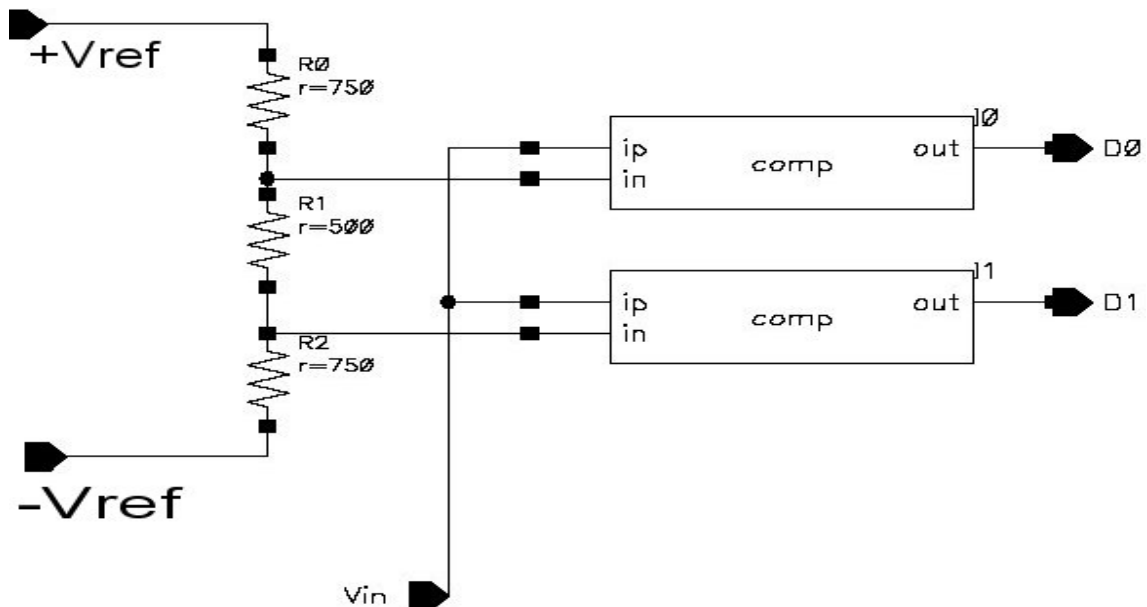


Fig 2

The ahdl code for the 1.5bit DAC

```
// Spectre AHDL for Lab2ADDA, DAC1_5, ahdl

module DAC1_5(D0, D1, out)
  node [V,I] D0, D1, out ;
  {
  analog {

if ((V(D0)>2.5) & (V(D1))>2.5) {
V(out) <- -0.25;
  }

  if ((V(D0)<2.5)&(V(D1))>2.5){
    V(out) <- 0;
  }

  if ((V(D0)<2.5)&(V(D1))<2.5){
    V(out) <- 0.25;
  }}}
}
```

Code 1

The ahdl code for the ADDER

```
// Spectre AHDL for Lab2ADDA, adder, ahdl

module adder(Vplus,Vmin,Vout)

node [V,I] Vplus, Vmin, Vout;
{
analog{

V(Vout) <- V(Vplus)-V(Vmin);

}}
```

Code 2

The ahdl code for the multiplierby2

```
// Spectre AHDL for Lab2ADDA, multiplyby2, ahdl

module multiplyby2(Vin, Vout)
node [V,I] Vin,Vout;
{
analog{

V(Vout) <- 2*V(Vin);

}}
```

Code 3

The schematic for the T/H circuit

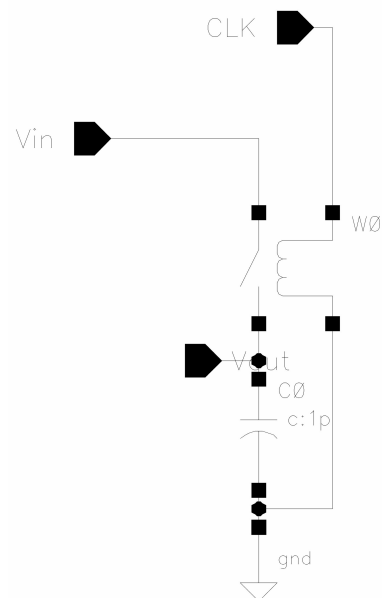


Fig 3

Part 2: Designing the digital correction circuit for the pipelined ADC

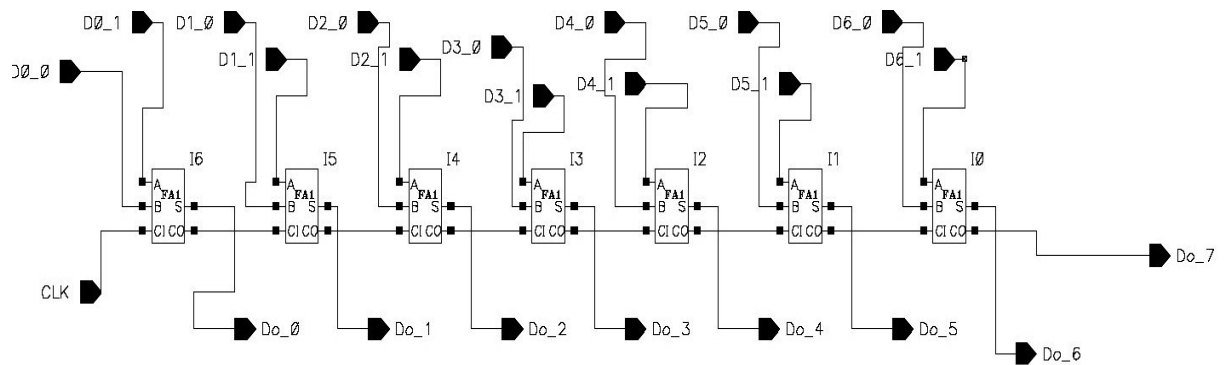


Fig 4

[illegible]

Part 4: Putting it all together.

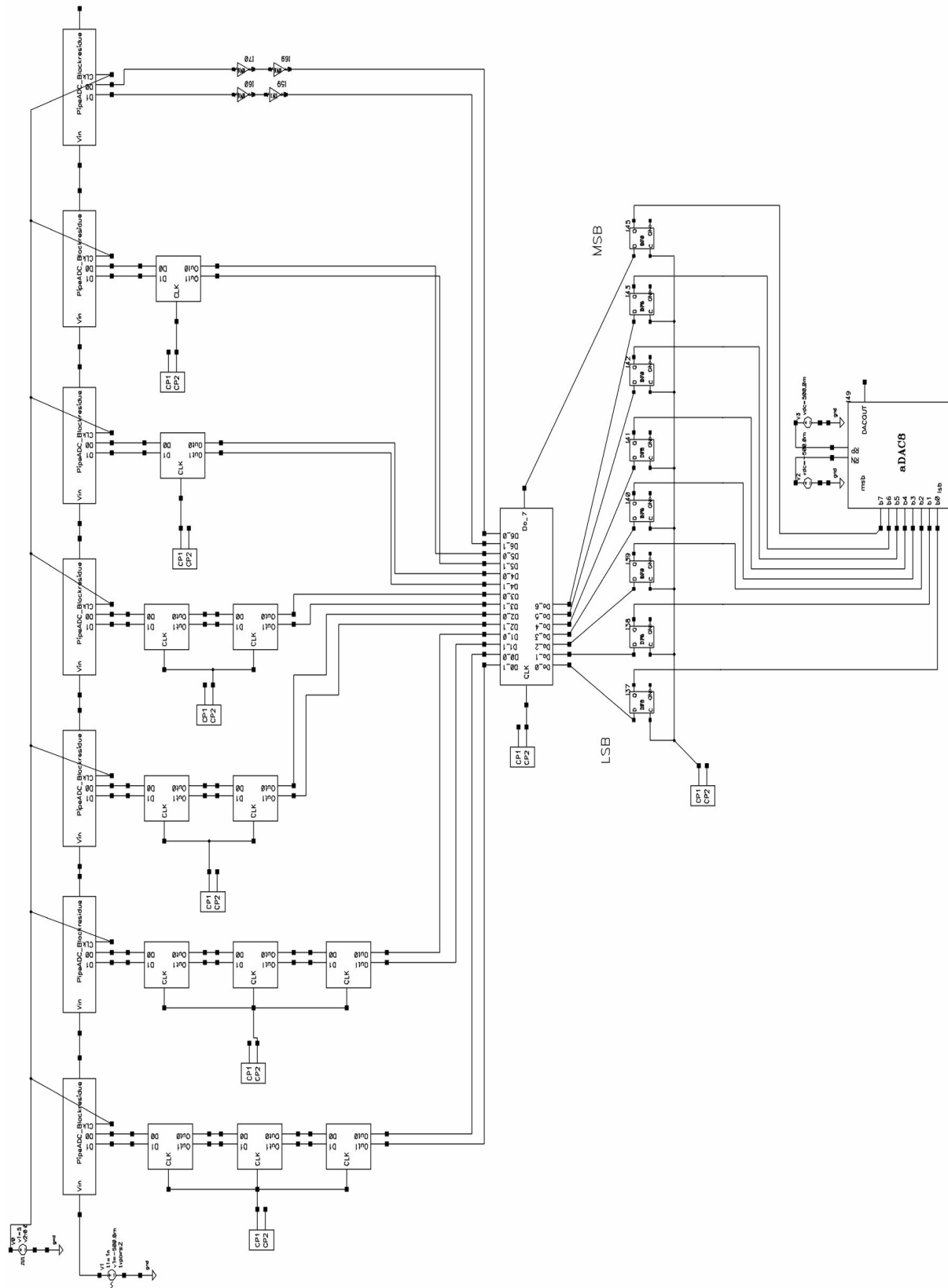


Fig 6

Simulation result of ramp input

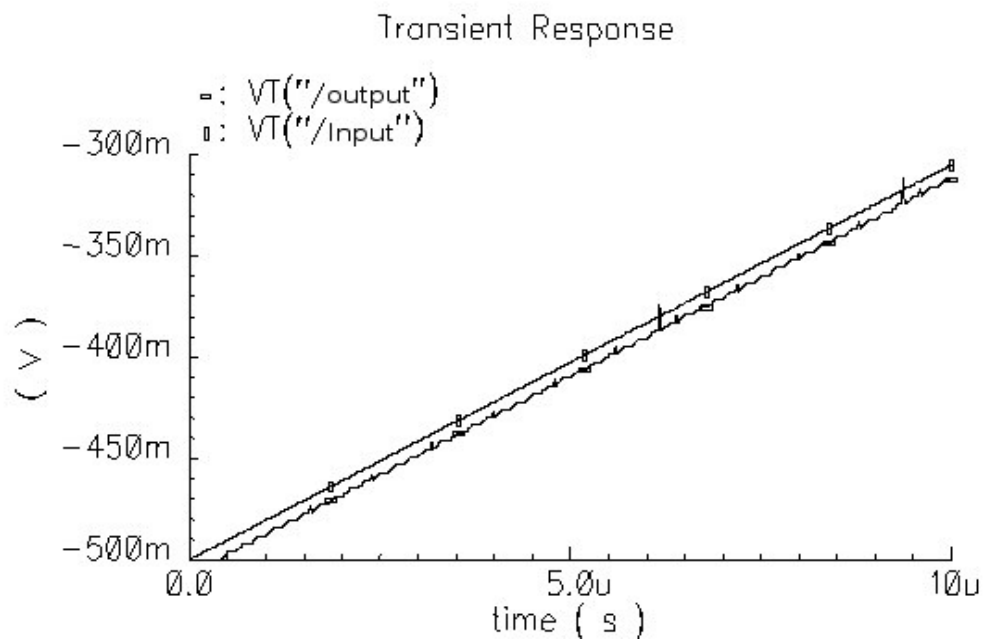


Fig 7

Part 5. SFDR using a 100kHz @500mV amplitude sinewave.

Using threshold voltage of $V_t=0.1\text{mV}$

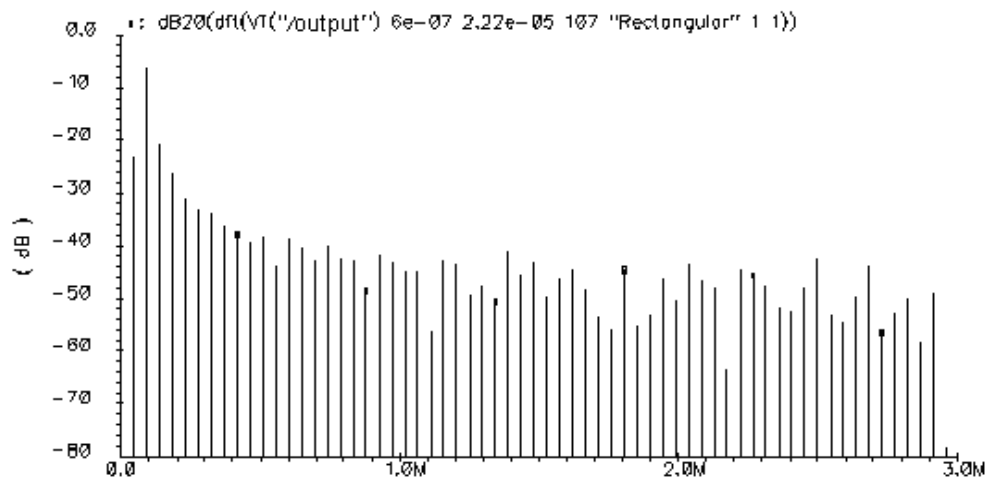


Fig 8

Using threshold voltage of $V_t=100\text{mV}$

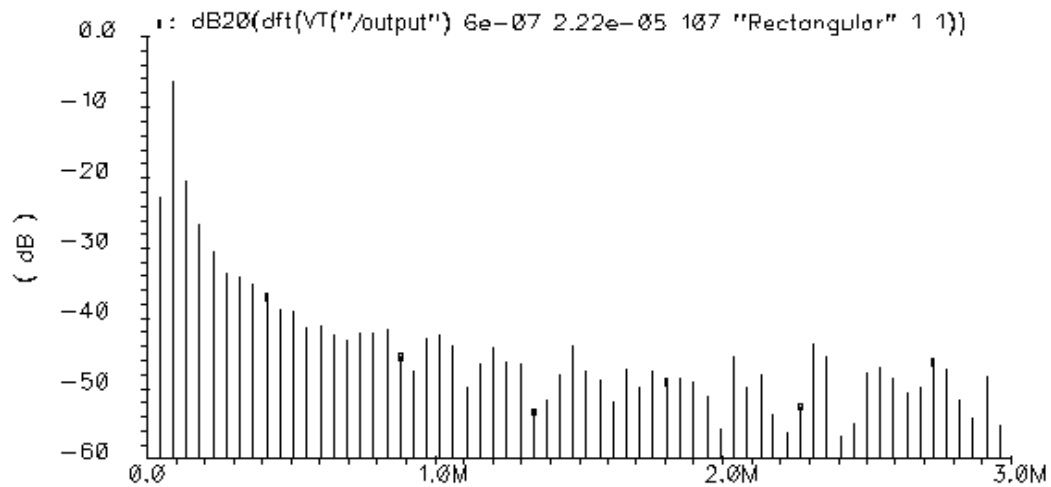


Fig 9

Result of SFDR:

When the threshold voltage is 0.1 mV, SFDR = 33 dB @ 1.39 MHz.

When the threshold voltage is 100 mV, SFDR = 38 dB @ 2.31 MHz.

Conclusion

Spurious Free Dynamic Range gives the ratio between the fundamental input signal and the highest distortion in the output spectrum. My conclusion is that a larger threshold voltage results in a larger value spurious free dynamic range.