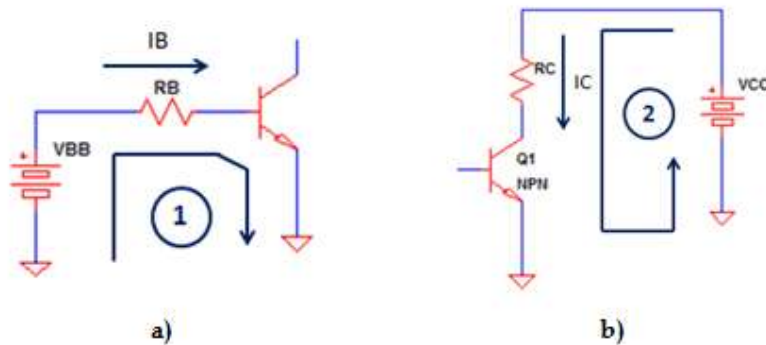




BJT Electronics

Complete Analysis of a Fixed Bias Circuit using NPN Transistor

by [electronicsbeliever](#) • 5 • BJT, Electronics

This article will uncover the complete analysis of a fixed bias circuit. Figure 73 below shows a simple common emitter configuration. It has a base resistor R_B , collector resistor R_C but no emitter resistor. In general, this biasing technique is called as non-emitter stabilized bias because there is no emitter resistor. By some, this is also called as the fixed bias.

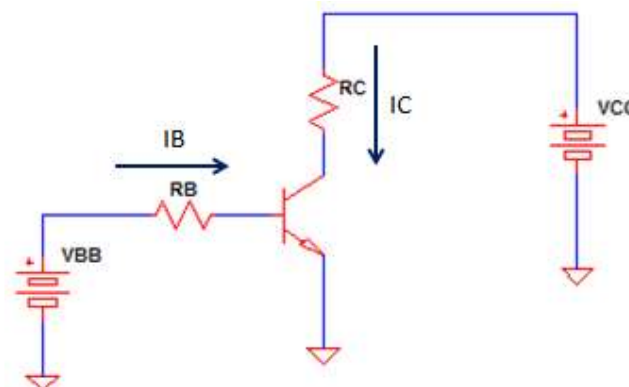


Figure 73 – Non-emitter stabilized circuit. Sometimes this bias technique is called as the fixed bias.

Base-Emitter Analysis

To start the analysis, let's consider the base-emitter loop (Loop 1) depicted in Figure 74a). We will perform KVL starting from V_{BB}

$$\begin{aligned} V_{BB} - I_B R_B - V_{BE} &= 0 \\ I_B &= \frac{V_{BB} - V_{BE}}{R_B} \end{aligned} \quad [\text{Eq. 115}]$$

The first requirement to turn on a bipolar junction transistor is to satisfy its base-emitter voltage requirement. So, it is obvious that the level of V_{BB} must be greater than the V_{BE} of the transistor which is typically 0.7V for a silicon made while 0.3V for a germanium one.

Collector-Emitter Analysis

Now, we will do KVL on the collector-emitter loop (Loop 2) starting from the V_{CC}

$$\begin{aligned} V_{CC} - I_C R_C - V_{CE} &= 0 \\ V_{CE} &= V_{CC} - I_C R_C \end{aligned} \quad [\text{Eq. 116}]$$

The collector current is a function of the base current and the device beta, so we can write it as

$$I_C = \beta I_B \quad [\text{Eq. 117}]$$

Above equation is only valid as long as the operation is within the active region. At the active region, the collector current of the circuit is not a function of the collector resistor. Changing the value of the resistor will give the same collector current considering the same base current. However, a change in the collector resistor will change the value of collector-emitter voltage described in [Eq. 116]. The change in the VCE has a big effect in the operation of the circuit.

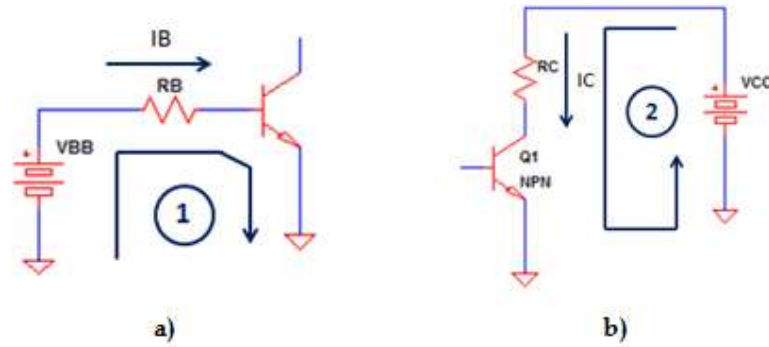


Figure 74 – a) Base-emitter loop of Figure 73, b) Collector-emitter loop of Figure 73

Notes:

V_{BE} is the voltage on the base-emitter junction. It can be stated as the voltage on the base minus the voltage on the emitter ($V_{BE} = V_B - V_E$). V_{CE} is the voltage across the emitter-collector. It can also be expressed as the voltage of the collector minus the voltage of the emitter ($V_{CE} = V_C - V_E$).

Power Dissipation

The power dissipation of a transistor is the sum of the base-emitter and the collector-emitter dissipations. So for Figure 73, the power dissipation of the base-emitter circuit is

$$P_{diss_{BE}} = V_{BE} I_B$$

While the power dissipation of the collector-emitter section is

$$P_{diss_{CE}} = V_{CE} I_C$$

The total power dissipation will be

$$P_{diss_{total}} = P_{diss_{BE}} + P_{diss_{CE}}$$

$$P_{diss_{total}} = V_{BE} I_B + V_{CE} I_C$$

[Eq. 118]

Operation at Saturation

When the circuit saturates, the collector current will settle to its maximum level which is dictated by the output circuitry or the collector-emitter loop. For Figure 73, the saturation collector current is

$$V_{CC} - I_C R_C - V_{CEsat} = 0$$

$$I_C = \frac{V_{CC} - V_{CEsat}}{R_C} \quad [\text{Eq. 119}]$$

(Where V_{CEsat} is the collector-emitter saturation voltage which is defined in the transistor datasheet.)

Measuring Actual Voltages using a Volt Meter

If we talk about VCE , it is the voltage across the collector-emitter section. When measuring it using a volt meter, the positive lead of the meter should be connected in the collector while the negative lead must be in the emitter as shown in Figure 75.

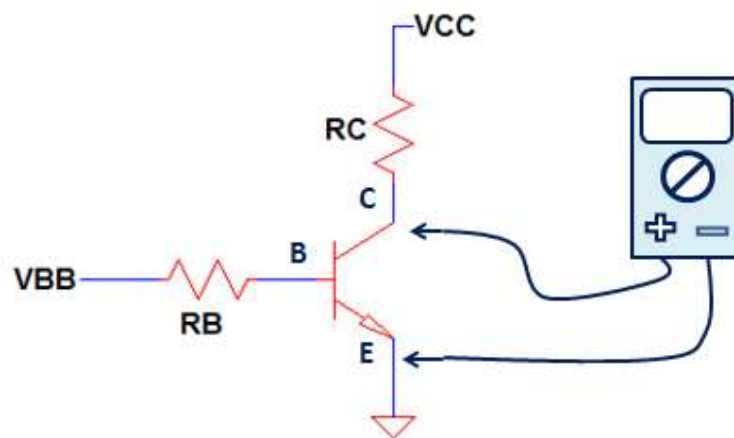


Figure 75 – Multi meter lead setup when measuring the voltage across the collector-emitter. VCE is the differential voltage of the collector and the emitter leads. The voltmeter leads should be connected to the respected terminal such that the positive lead to the collector whiles the negative one to the emitter. In this example, the negative lead is can be connected to the circuit ground directly because there is no emitter resistor which makes the emitter voltage the same level with the ground. For circuits having a resistor in the emitter, the negative lead should be on the emitter to get the real collector-emitter voltage.

Figure 76 shows the volt meter lead arrangement when measuring the voltage across base-emitter junction and the voltage drop of the base resistor R_B . As

a general rule, always insert or tap the positive lead of the measuring device to the section where higher potential is expected and the negative lead to the lower potential.

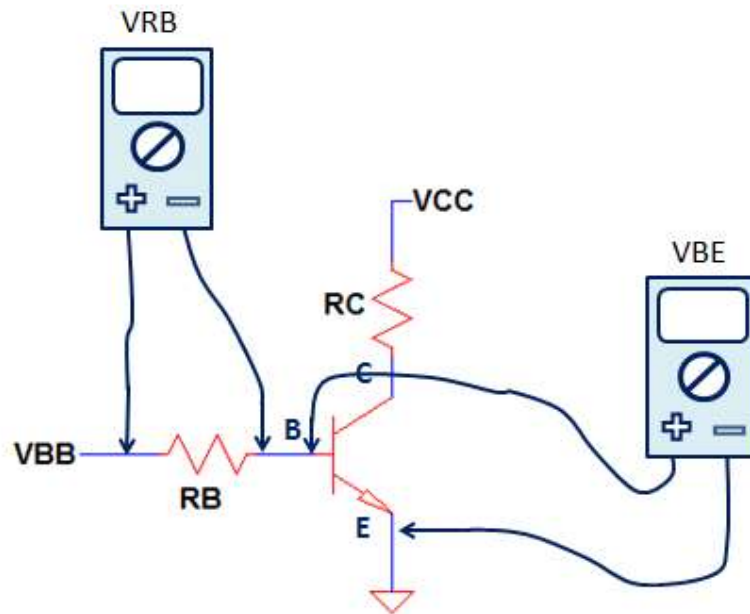


Figure 76

Example 21

Solve for the following using the circuit in Figure 77.

- Base current,
- Collector current
- V_{CE}
- V_C
- V_B
- V_{BC}
- Power Dissipation

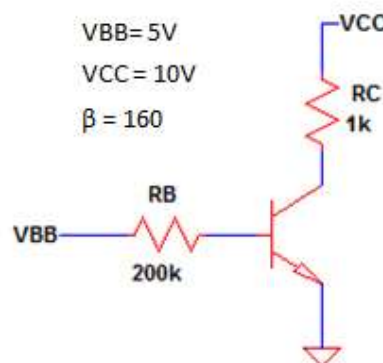


Figure 77 – Circuit model for Example 21.

Solution

a) Solving base current using [Eq. 115]

$$I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{5V - 0.7V}{200k\Omega} = 21.6\mu A$$

b) Solving collector current using [Eq. 117]

$$I_C = \beta I_B = 160 \times 21.6\mu A = 3.456mA$$

c) Solving for using [Eq. 116]

$$V_{CE} = V_{CC} - I_C R_C = 10V - 3.456mA \times 1k\Omega = 6.544V$$

d) The collector voltage is can be solved using the expression as below

$$\begin{aligned} V_{CE} &= V_C - V_E \\ V_C &= V_{CE} + V_E \end{aligned}$$

The collector-emitter voltage is already available and the value of the emitter voltage is just zero since emitter is connected directly to the circuit ground. Thus,

$$V_C = V_{CE} + V_E = 6.544V + 0V = 6.544V$$

e) is likewise can be derived from the expression of as below

$$\begin{aligned} V_{BE} &= V_B - V_E \\ V_B &= V_{BE} + V_E \end{aligned}$$

The value of V_{BE} is not defined in the problem so it is by default 0.7V as silicon is the widely used material for transistor. As mentioned above, the value of emitter voltage is zero since it is directly connected to the circuit ground. Therefore,

$$V_B = V_{BE} + V_E = 0.7V + 0V = 0.7V$$

f) The voltage is the difference of the base and the collector voltage

$$V_{BC} = V_B - V_C = 0.7V - 6.544V = -5.844V$$

The negative voltage means that the base-collector junction is reversed biased. This is really expected because the circuit is operating in the active region. As defined earlier, at active region the base-emitter junction is forward biased while the base-collector is reversed biased.

g) The power dissipation of the transistor is the sum of the base-emitter and the collector-emitter dissipations. Using [Eq. 118]

$$P_{diss_total} = V_{BE} \times I_B + V_{CE} \times I_C = 0.7V \times 21.6\mu A + 6.544V \times 3.456mA = 22.63mW$$

Checking for Beta Variation Effect

The major contributor for the operation shift or Q-point change of a transistor circuit is the big variation of the transistor current gain, β . For instance, a BC817-25 transistor has a beta which is ranging from 160 to 400. This is a huge range and surely changes the operating point of the circuit if not properly designed.

With the same circuit in Figure 77, let us solve for the **a)** base current, **b)** collector current and **c)** Collector-emitter voltage but this time doubling the beta.

a) Solving base current using [Eq. 115]

$$I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{5V - 0.7V}{200k\Omega} = 21.5\mu A$$

b) Solving collector current using [Eq. 117]

$$I_C = \beta I_B = 320 \times 21.6\mu A = 6.912mA$$

c) Solving for using [Eq. 116]

$$V_{CE} = V_{CC} - I_C R_C = 10V - 6.912mA \times 1k\Omega = 3.088V$$

As you notice, the base current is the same because in the first place beta is not a factor of it. The collector current has been doubled in value and the collector-emitter voltage is less than half the original value. The operation of the circuit is very affected by doubling the current gain. If you are designing a critical application, this bias type is not a good choice.

To summarize, the complete analysis of a fixed bias circuit is can be done by doing KVL in the base-emitter and collector-emitter loop.

[Follow](#) [electronicsbeliever.com](#).

[electronicsbeliever](#)

[More by electronicsbeliever](#)

Previous Article

[How to Sweep Current in LTSpice Step by Step Tutorials](#)

Next Article

[Fixed Bias Configuration with a Divider Resistor in the Base Complete Analysis](#)

5 thoughts on “Complete Analysis of a Fixed Bias Circuit using NPN Transistor”

Asma July 17, 2020 at 8:34 PM

Design a fixed bias circuit using silicon npn transistor which has a dc current gain 150, to operate the transistor with collector-emitter voltage of 5v, and collector current of 5mA and supply voltage is 10v. Explain operation of the circuit and discuss advantages and disadvantages of fixed bias circuit.

REPLY

izhar July 19, 2020 at 1:48 PM

Design a fixed bias circuit using silicon npn transistor which has a dc current gain 150, to operate the transistor with collector-emitter voltage of 5v, and collector current of 5mA and supply voltage is 10v. Explain operation of the circuit and discuss advantages and disadvantages of fixed bias circuit.
I have need solution of this urgently plz help me

REPLY

electronicsbeliever July 31, 2020 at 1:56 PM

Hi,

Sorry for late reply. Just read this lately due to busy sked. For the design aspects of the fixed bias circuit, you can make use of the design template I made. Play around to that by changing the value.

<https://electronicsbeliever.com/downloads/npn-transistor-fixed-bias-circuit-design-template/>

REPLY

Sylba November 21, 2023 at 1:47 PM

Bravo. The article is superb. Analysis is clear and simple. One remark, Example 21 solution e should be 22,63 mW not in 22,63 mA.

REPLY

electronicsbeliever November 26, 2023 at 10:31 AM

Hi Sylba,

Thank you for the remarks. You indeed go through the details of the article and caught the error.
I had already updated solution g to 22.63mW. Thank you.


REPLY

Follow Us



Electronics Believer
2,470 followers

Follow Page

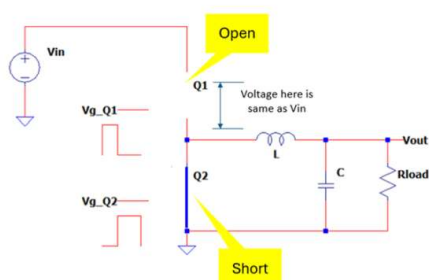


Quick Facts About Synchronous Buck Converter

This article will uncover the complete analysis of a fixed bias circuit. Figure 73 below shows a simple common emitter configuration. ... [Read more](#)

SUPPLY VOLTAGE		
Parameters	Value	Unit
V _{DS}	5	volt
V _{DO}	5	volt
This is the typical value of V _{DS} . See the figure. This is the typical value of V _{DO} . See the figure.		
AMBIENT TEMPERATURE		
Parameters	Value	Unit
T _{amb} max	60	°C
T _{amb} min	-30	°C
This is the maximum operating ambient temperature. This is a design given. This is the minimum operating ambient temperature. This is a design given.		
RESISTOR DATA		
Parameters	Value	Unit
R _{G1}	1500	ohms
R _{G2}	100000	ohms
P _{RG1} rating	0.1	watt
P _{RG2} rating	0.1	watt
Input here the resistance of R _{G1} . See figure. Input here the resistance of R _{G2} . See figure. Input here the power dissipation rating of R _{G1} . Get this from the datasheet. Input here the power dissipation rating of R _{G2} . Get this from the datasheet.		
RELAY DATA		
Parameters	Value	Unit
R _{COIL} typical	100	ohms
L _{COIL}	100	uH
P _{COIL} rating	1	watt
T _{min} relay	-40	°C
T _{max} relay	125	°C
Input here the coil resistance of the relay. Get this from the datasheet. Input here the coil inductance of the relay. Get this from the datasheet. Input here the power dissipation rating of the relay coil. Get this from the datasheet. Input here the minimum operating temperature of the relay. Get this from the datasheet. Input here the maximum operating temperature of the relay. Get this from the datasheet.		

Design Template for NMOS Lowside Relay Driver

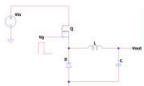This article will uncover the complete analysis of a fixed bias circuit. Figure 73 below shows a simple common emitter configuration. ... [Read more](#)




Buck Converter Design Template

Notes:
1. Values in green are typical. The user must enter values into them.
2. Values in orange are calculated or derived from the user inputs. The user should not alter them.
3. This template is applicable to CCM and Boundary mode (or BCM) operation.
4. This is not applicable to synchronous buck.

Buck Converter Design Using Excel Calculator

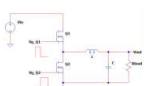This article will uncover the complete analysis of a fixed bias circuit. Figure 73 below shows a simple common emitter configuration. ... [Read more](#)



Synchronous Buck Converter Design Template

Notes:
1. Values in green are typical. The user must enter values into them.
2. Values in orange are calculated or derived from the user inputs. The user should not alter them.
3. This template is applicable to CCM and Boundary mode (or BCM) operation.
4. This is not applicable to synchronous buck.

Synchronous Buck Converter Design Calculator Excel-External Switches


This article will uncover the complete analysis of a fixed bias circuit. Figure 73 below shows a simple common emitter configuration. ... [Read more](#)

Parameter	Symbol	Value	Unit
Input Voltage			
Input voltage	V _{in}	100	V
Output voltage	V _o	50	V
Output current	I _o	1	A
Output Voltage			
Output voltage	V _o	15	V
Output current	I _o	1	A
Load Inductor			
Load inductor	L _o	24	uH
Load inductor current	I _o	24	A
Load inductor current	I _o	24	A
Load inductor current	I _o	24	A
Frequency			
Frequency	f _s	100	kHz
Frequency	f _s	100	kHz
Frequency	f _s	100	kHz
Capacitor			
Capacitor	C _o	100	uF
Capacitor	C _o	100	uF
Capacitor	C _o	100	uF
Inductor			
Inductor	L _o	10	uH
Inductor	L _o	10	uH
Inductor	L _o	10	uH
Resistor			
Resistor	R _o	1	ohm
Resistor	R _o	1	ohm
Resistor	R _o	1	ohm

Template Legend

Input values. User must provide.
Calculated values. User should not alter.
Derived values. User should not alter.
Derived values. User should not alter.
Derived values. User should not alter.

LLC AC Circuit

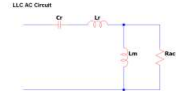

Half Bridge LLC Resonant Converter Power Section Calculator

This article will uncover the complete analysis of a fixed bias circuit. Figure 73 below shows a simple common emitter configuration. ... [Read more](#)

- [BJT \(11\)](#)
- [Boost Converter \(3\)](#)
- [Buck Converter \(7\)](#)
- [Circuit Analysis \(1\)](#)
- [Circuit Analysis \(1\)](#)
- [Control System \(1\)](#)
- [Design Template \(5\)](#)
- [Diode \(2\)](#)

[Electronics](#) (45)
[EMI/EMC](#) (1)
[ESD](#) (2)
[EV Charging](#) (1)
[Flyback Converter](#) (1)
[Fuse](#) (3)
[How To](#) (14)
[Inverting Buck-Boost](#) (1)
[LED Drivers](#) (1)
[LLC](#) (5)
[LTSpice](#) (9)
[Mathcad](#) (1)
[Matlab](#) (2)
[Miscellaneous](#) (3)
[MOSFET](#) (17)
[Optocoupler](#) (11)
[Others](#) (1)
[Power Electronics](#) (26)
[Power Supply](#) (6)
[Quasi Resonant Flyback](#) (9)
[RC Circuit](#) (1)
[Regulators](#) (2)
[Relay](#) (2)
[Reviews](#) (5)
[Simulink](#) (2)
[Thermal Management](#) (1)
[Troubleshooting](#) (3)
[Tutorials](#) (31)

