

- Kursansvarig/examinator: Jörgen Olsson
- Undervisningsteam:
 - Jörgen Olsson
 - Uwe Zimmermann
 - Lars Vestling
 - Labassar
- Hemsida:
<http://www.teknik.uu.se/fte/education.html>

Kursliteratur

Electronics: A Systems Approach



Electronics: A Systems Approach

3rd Edition

by Neil Storey
published by
Prentice Hall

Kursplan

- **Förkunskaper:** Elektromagnetism I. Mätteknik. Transformmetoder förutsätts läsas samtidigt.
Utbildningsnivå: Grundnivå
Betygsskala: För denna kurs ges betygen U underkänd, 3 godkänd, 4 icke utan beröm godkänd och 5 med beröm godkänd
- **Huvudområde**
- Teknik
- **Mål**
- Efter fullgjord kurs skall studenten kunna:
- analysera frekvensgång och fasgång för passiva och aktiva filter och använda bodediagram
- konstruera förstärkare med hjälp av OP-förstärkare
- använda dioder och transistorer i enkla kopplingar
- konstruera kombinatoriska nät och sekvensnät med D-vippor
- använda ett simuleringsprogram för analys och konstruktion av elektroniska kretsar

- **Innehåll**
- Tvåpoler och tvåpolssatsen. Överföringsfunktioner, gränsfrekvens, bodediagram. Operationsförstärkaren, dioden. Fälteffekt- och bipolära transistorer. Digitala grundkretsar, Boolsk algebra, Karnaughdiagram. Analys och syntes av kombinatoriska kretsar och synkrona sekvenskretsar.
- **Undervisning**
- Föreläsningar, lektioner och laborationer
- **Examination**
- Skriftlig tentamen vid kursens slut (4 hp). För godkännande fordras även godkända laborationer (1 hp).
- **Kursen går på halvfart!**

Två områden: Analog och Digital Elektronik

- Kursen innehåller både analog och digital elektronik.
- Grundläggande koncept för respektive område går igenom med stöd av labbar och räkneövningar
- Period I: Analog elektronik
- Period II: Digital elektronik
- Tenta vid slutet av period II

Planering period I

- **Föreläsningar**

- Introduktion, repetition kap. 1, 3.2-3.4
- Tvåpol, förstärkning, bode kap. 3.5-3.9
- OP kap. 5.1-5.7, 4.4 inkluderas i 5.3
- -- “ -- -- “ --
- Filter, oscillatorer kap. 10.-10.2, 11.1-11.2.2
- Dioden kap. 6.4-6.6, (6.7.1-6.7.2 översiktligt), 6.8.1-6.8.2
- fälteffekttransistorn kap. 7.1-7.4 översiktligt, 7.5-7.6 (valda delar)
- bipolärtransistorn kap. 8.1-8.4 översiktligt, 8.5-8.6 (valda delar)

- **Labbar**

- R, C, OP, mätningar och simuleringar
- Diod och transistor (+R,C,OP) mätningar och simuleringar

- **Övningar**



- tvåpol, fyrcpol, bode, etc
- OP-kretsar
- filter, osc, dioder
- transistorkopplingar

- **Tidsschema**


- F1, F2, F3, Ö1, F4, F5, Ö2, F6, Ö3, Lab1, F7, F8, Lab2, Ö4

Kretssimulering

OrCAD
PSpice

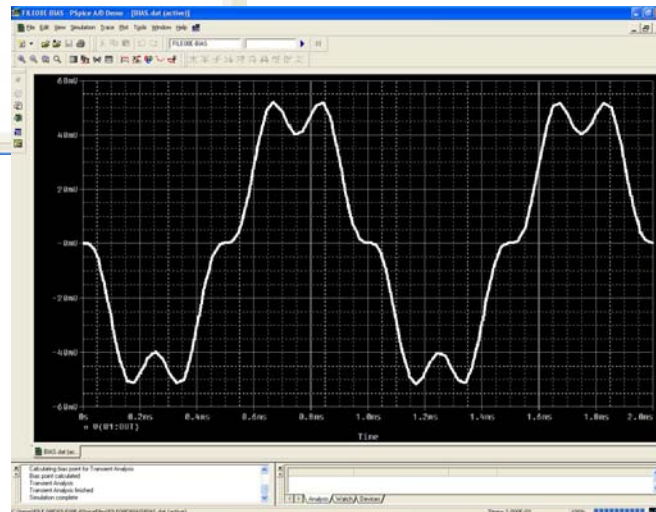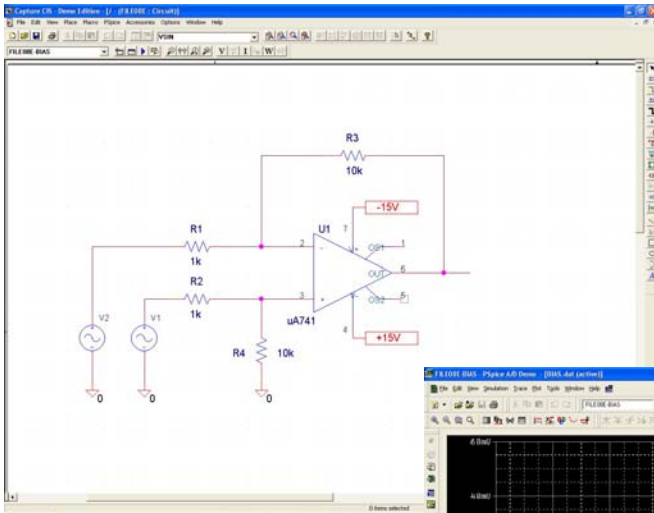


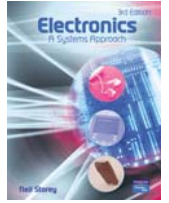- Simulering ingår i labbar
- Även övnings-simuleringar finns kopplade till texten i boken
- Både simulatorer och övningsfiler finns att komma åt i från hemsidan



Electronic systems

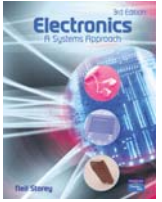- Introduction
- Electronic systems
- Distortion and noise
- System design.



1.1

Introduction


- The world in which we live is constantly changing.
- To survive, we need to respond to changes in our environment.
 - To respond we sense a changing quantity (the **input**).
 - And modify some other quantity (the **output**).
- We often use machines to respond on our behalf.
 - The nature of these machines is that they **sense** some input quantity, **process** the information, and then **control** some output quantity.

Introduction (contd.)

- The world about us is characterised by a number of **physical properties** or **quantities**.
 - e.g. temperature, pressure, humidity, etc.
- Physical quantities may be *continuous* or *discrete*.
- **Continuous quantities** change smoothly and can take an infinite number of values.
- **Discrete quantities** change abruptly from one value to another.
 - Most real-world quantities are continuous.
 - Many man-made quantities are discrete.

Introduction (contd.)

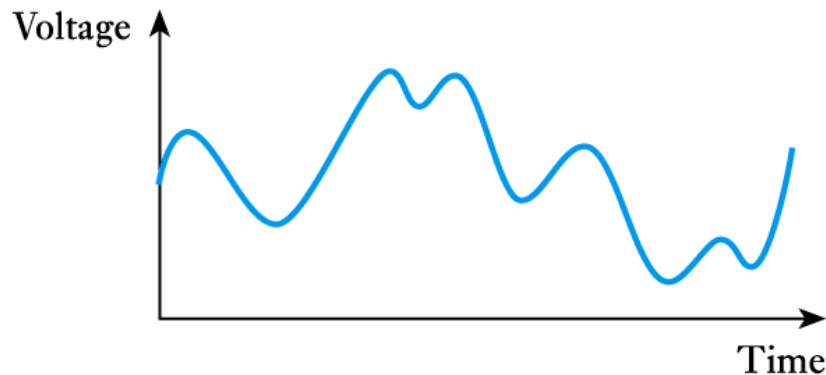
- It is often convenient to represent physical quantities by electrical signals. These can also be continuous or discrete.
- Continuous signals are often described as **analogue**.



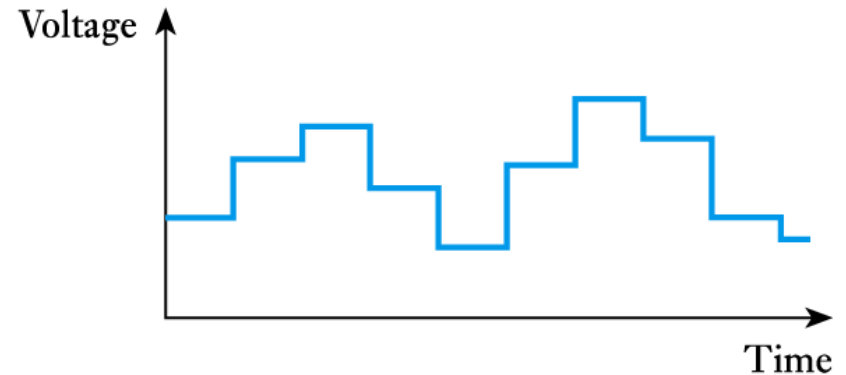(a) An analogue signal


Introduction (contd.)

- Discrete signals are often described as **digital signals**.




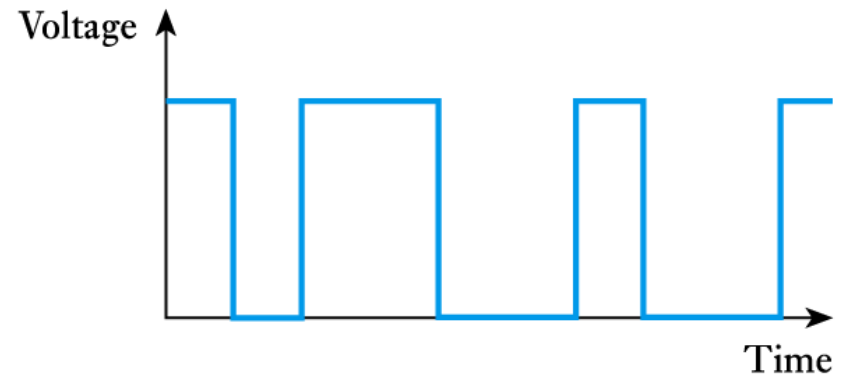(b) A multi-valued digital signal

- Many digital signals take only two values and are referred to as **binary signals**.



(c) A binary signal

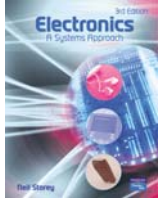

1.2


Electronic systems

- A system can be defined as


Any closed volume for which all the inputs and output are known.
- Examples include:
 - an engine management system
 - an automotive system
 - a transportation system
 - an ecosystem.
- Inputs and outputs will reflect the nature of the system.

Electronic systems (contd.)

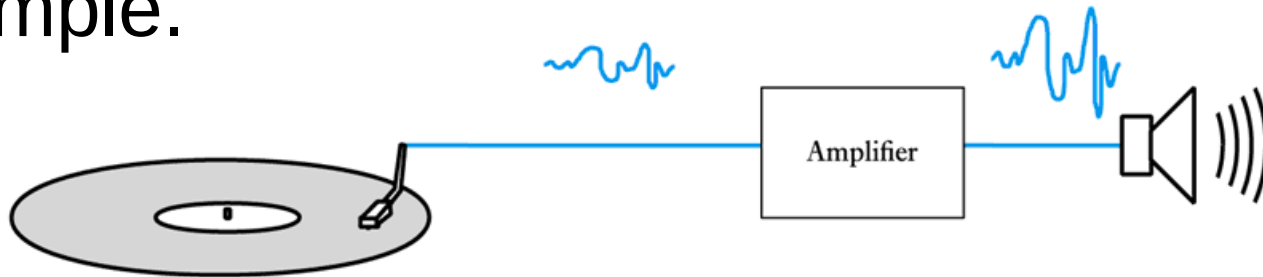- Electronic systems can take many forms, for example.



(a) A record player

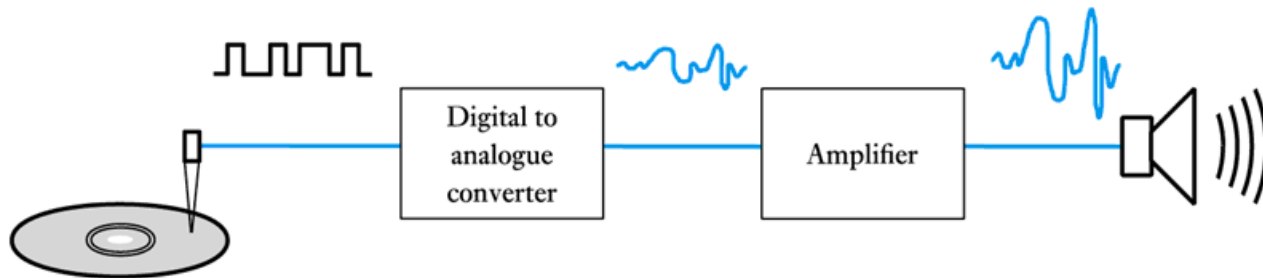


(b) A compact disc player

Electronic systems (contd.)


- Components that interact with the outside world are termed **sensors** and **actuators**.
 - In the previous examples the **pickup** or **laser scanner** represents a sensor.
 - In the previous examples the **loudspeaker** represents an actuator.
- We will look at sensors and actuators in more detail in later lectures.

Distortion and noise

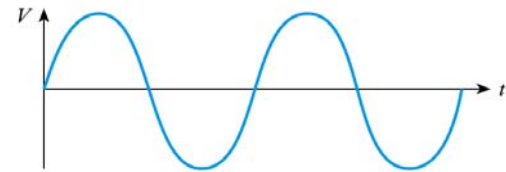
- All systems distort electrical signal to some extent
 - examples include clipping, crossover distortion and harmonic distortion.
- Distortion is **systematic** and is **repeatable**.




(a) Sine wave

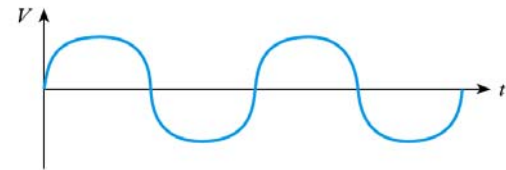

(b) Clipping

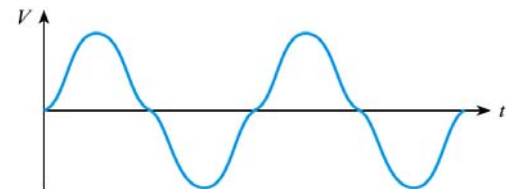


(c) Crossover distortion

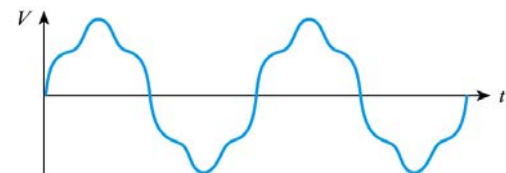

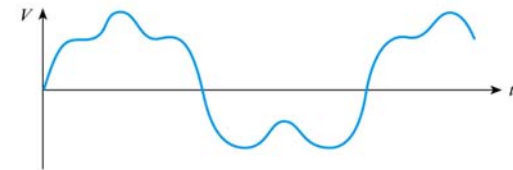
(d) Harmonic distortion

Distortion and noise (contd.)


- All systems also add noise to the signals that pass through them.
- Unlike distortion, noise is **random** and not repeatable.
- Noise can often be removed from digital signals but this is often impossible with analogue signals.




(a) Original analogue signal

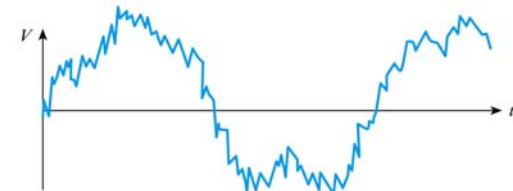


(b) Analogue signal with noise

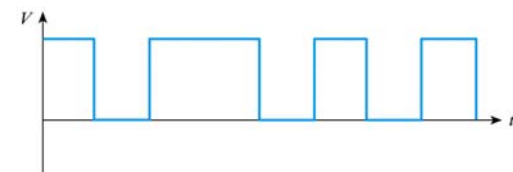

(c) Original digital signal

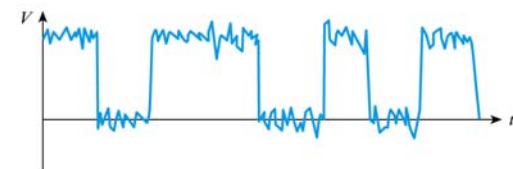

(d) Digital signal with noise

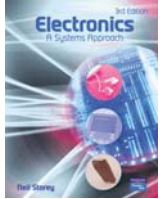

1.4

System design


- The task of designing an electronic system can be simplified by adopting a methodical approach.
- Generally this involves a **top-down approach**.
 - Customer requirements
 - Top-level specification
 - Choice of technology
 - Top-level design
 - Detailed design
 - Module construction and testing
 - System testing.

System design (contd.)

- **Electronic design aids**
 - schematic capture
 - circuit simulation
 - PCB or VLSI layout packages.
- Circuit simulation greatly assists our understanding of the operation of a circuit.
 - Common examples include PSpice and Multisim.
 - Simulation **demonstration files** are available to support the material in the course text.

Key points

- Systems interact with the world using sensors and actuators.
- Physical quantities can be either continuous or discrete.
- Physical quantities are often represented by signals.
- Useful electronic systems take input signals, process this information and produce appropriate outputs.
- Distortion and noise are always present.
- System design normally follows a top-down approach.
- Electronic design tools, such as simulators, are invaluable.

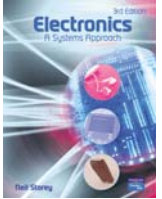

2.5

Laboratory measuring instruments

- Often the object of sensing a physical quantity is to **measure** it.
- Here we will look at three forms of measuring instrument:
 - analogue oscilloscope
 - digital oscilloscope
 - digital multimeter.

- An oscilloscope displays voltage waveforms.




Analogue oscilloscope (contd.)

- A typical analogue oscilloscope



Digital oscilloscope

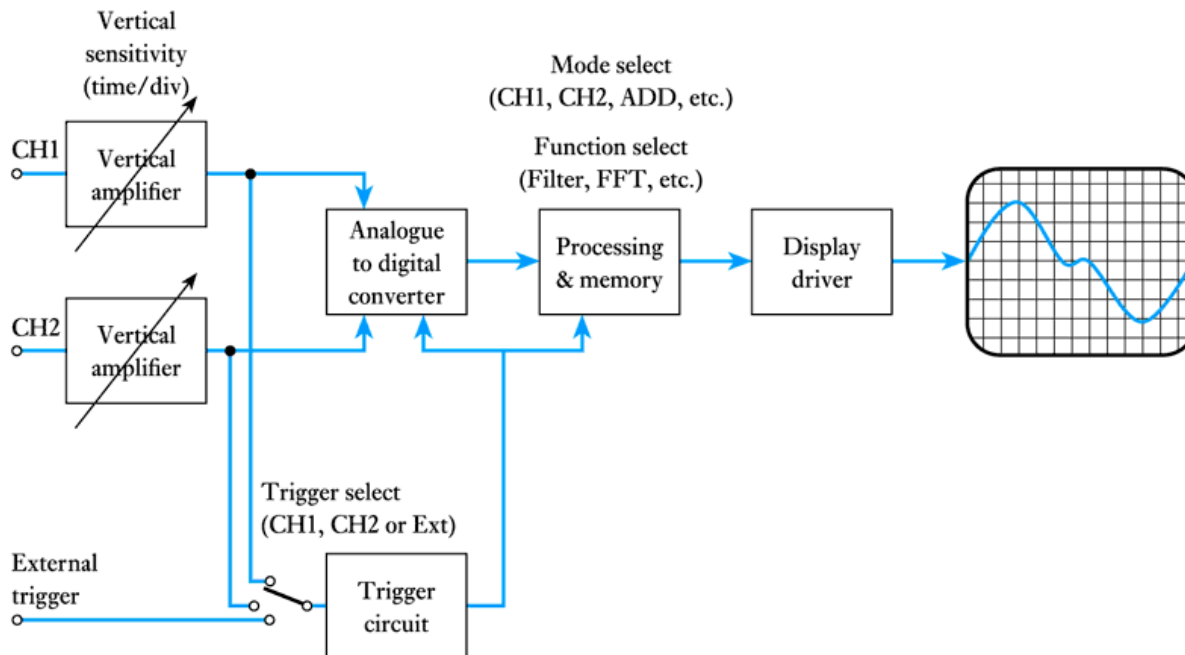
- Digital oscilloscopes use an analogue-to-digital converter (ADC) and appropriate processing.



A simplified block diagram


Digital oscilloscope (contd.)

- A typical digital oscilloscope

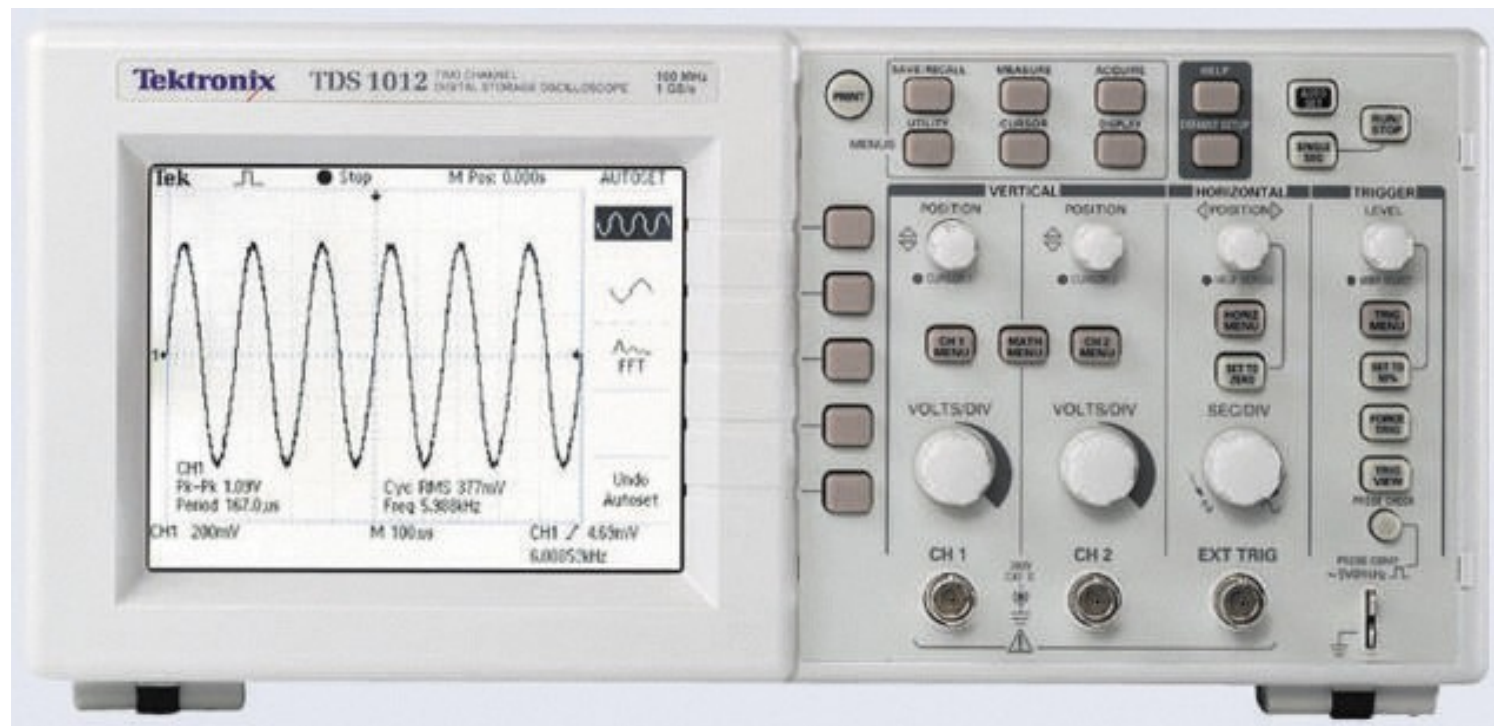

Digital multimeters

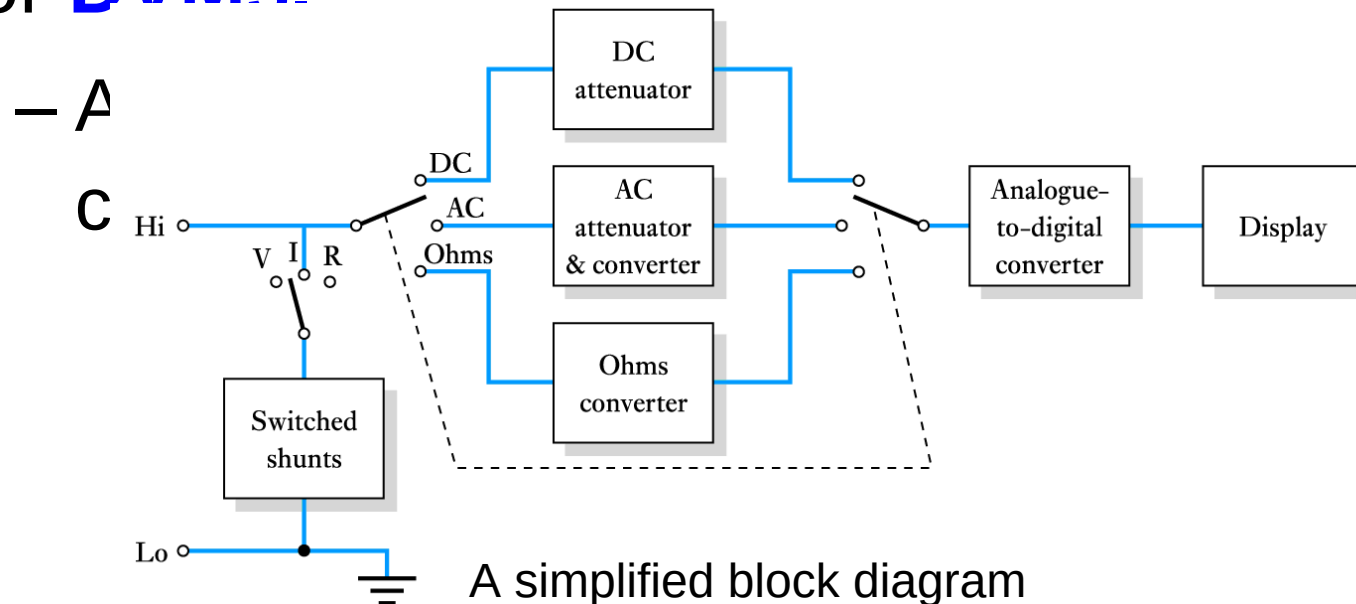- **Digital multimeters (DMMs)** are often (inaccurately) referred to as **digital voltmeters** or **DVMs**.



A simplified block diagram

Digital multimeters (contd.)

- Measurement of voltage, current and resistance is achieved using appropriate circuits to produce a voltage proportional to the quantity to be measured.
 - In simple DMMs alternating signals are rectified as in analogue multimeters to give their average value which is multiplied by 1.11 to directly display the r.m.s. value of sine waves.
 - More sophisticated devices use a **true r.m.s. converter**, which accurately produces a voltage proportional to the r.m.s. value of an input waveform.



A typical digital multimeter

Key points

- A wide range of sensors is available.
- Some sensors produce an output voltage related to the measured quantity and therefore supply power.
- Other devices simply change their physical properties.
- Interfacing may be required to produce signals in the correct form.
- Most actuators take power from their inputs in order to deliver power at the output – the efficiency is often low.
- We often sense quantities in order to measure them – there are a number of standard measuring instruments.

Repetition

- Ohms lag


$$V = R I$$

- Kirchhoffs lagar


$$\sum_i I_i = 0 \quad (\text{summan av strömmarna i en nod lika med noll})$$


$$\sum_i V_i = 0 \quad (\text{summan av spänningsfall i en sluten slinga lika med noll})$$

Exempel

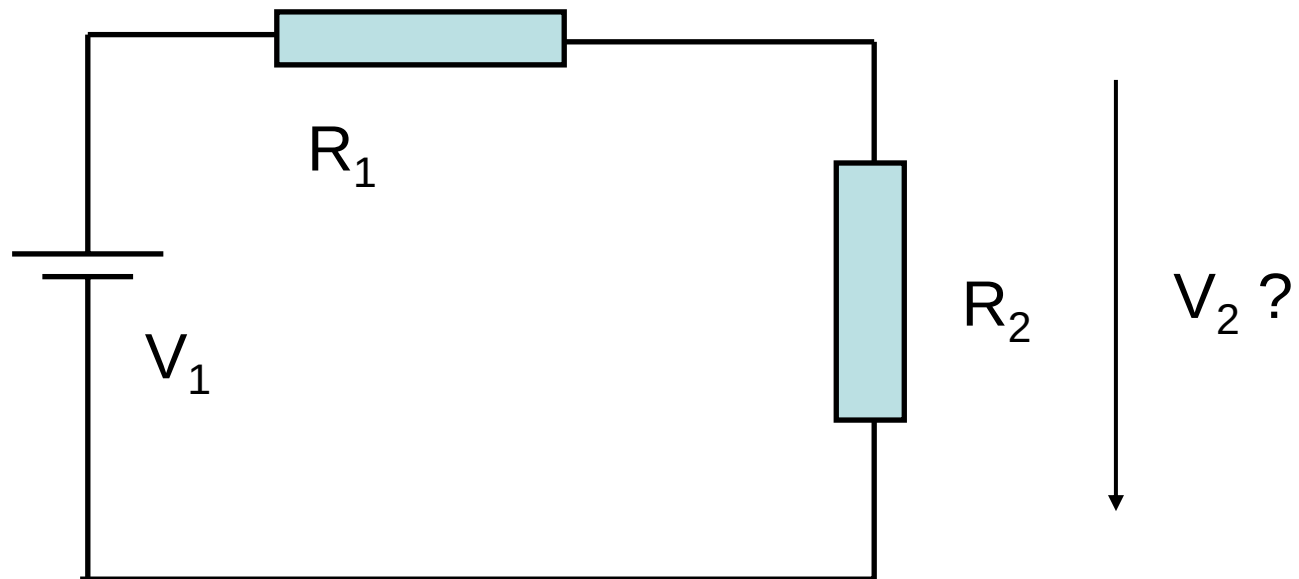


Exempel 1.11

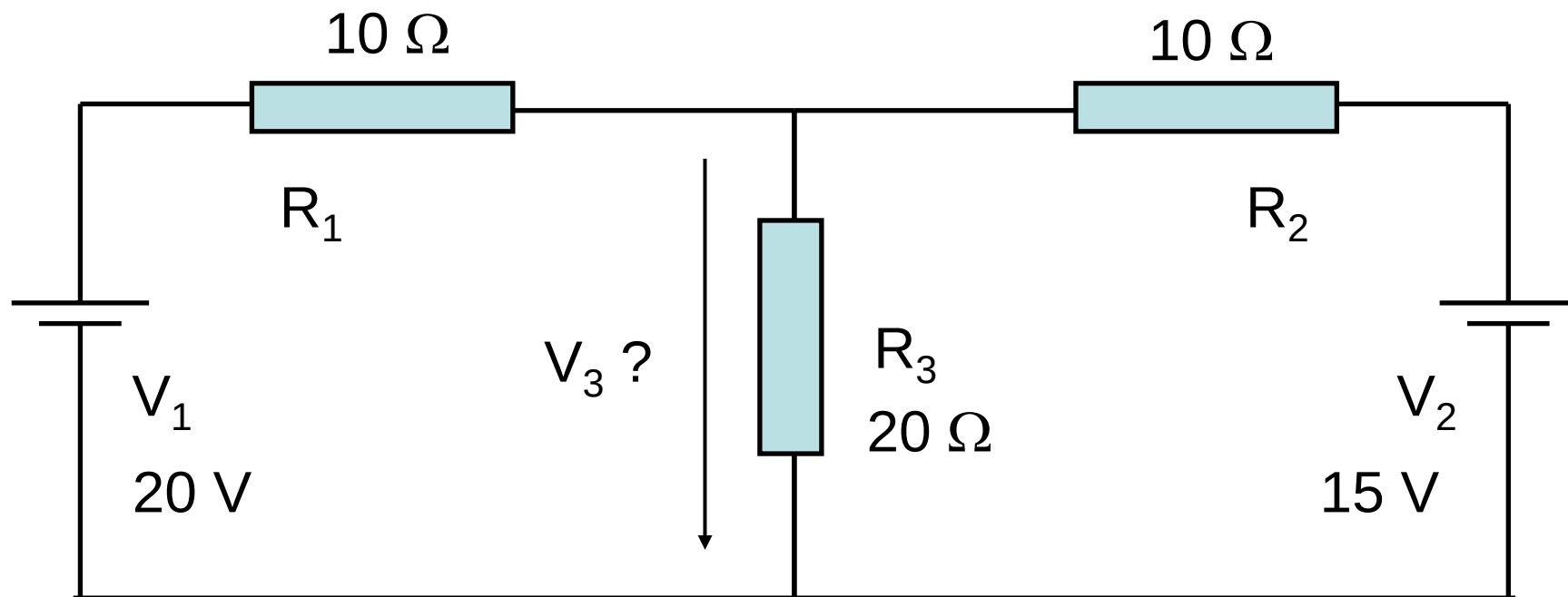

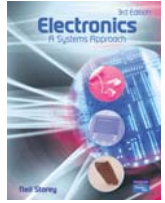

Amplification

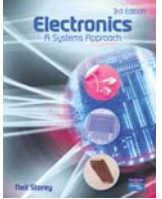- **Introduction**
- **Electronic amplifiers**
- **Sources and loads**
- **Equivalent circuit of an amplifier**
- Thévenin and Norton equivalent circuits
- Output power
- Power gain
- Frequency response and bandwidth
- Low- and high-frequency effects
- Noise
- Differential amplifiers
- Simple amplifiers.



3.1

Introduction


- Amplification is one of the most common processing functions.
- **Amplification** means making things bigger.
- **Attenuation** means making things smaller.
- There are many non-electronic forms of amplification.

Amplifiers

■ Non-electronic amplifiers

– Levers

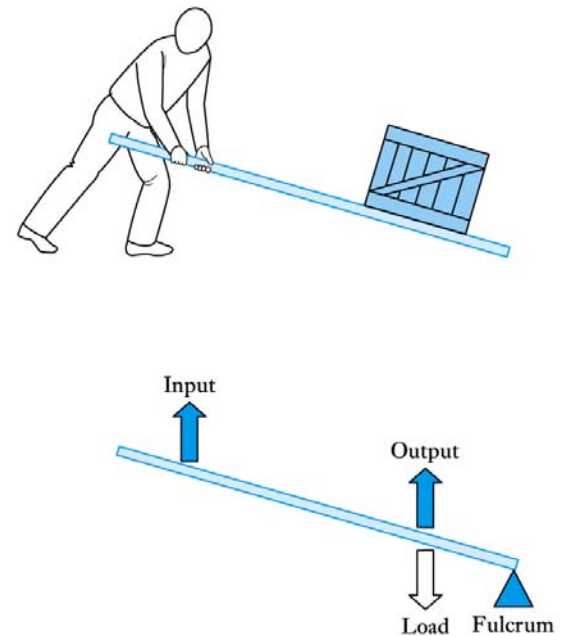- Example shown on the right is a force *amplifier*, but a displacement *attenuator*.
- Reversing the position of the input and output would produce a force *attenuator* but a displacement *amplifier*.
- This is an example of a **non-inverting amplifier** (since the input and output are in the same direction).





A lever arrangement

Amplifiers (contd.)

■ Non-electronic amplifiers

– Pulleys

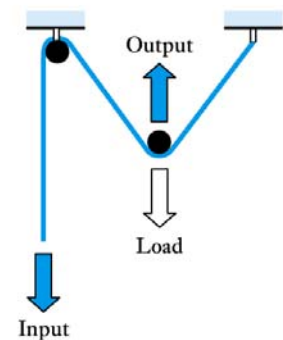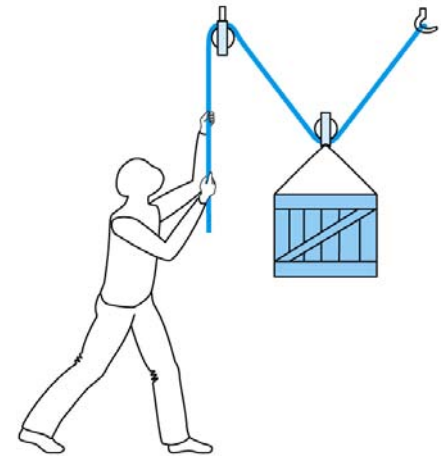- Example shown right is a force *amplifier*, but a displacement *attenuator*.
- This is an example of an **inverting amplifier** (since the input and output are in opposite directions) but other pulley arrangements can be non-inverting.




A pulley arrangement

Amplifiers (contd.)

- **Passive and active amplifiers**
 - Levers and pulleys are examples of **passive amplifiers** since they have no external energy source.
 - In such amplifiers the power delivered at the output must be less than (or equal to) that absorbed at the input.
 - Some amplifiers are not passive but are **active amplifiers** in that they have an external source of power.
 - In such amplifiers the output can deliver more power than is absorbed at the input

Amplifiers (contd.)

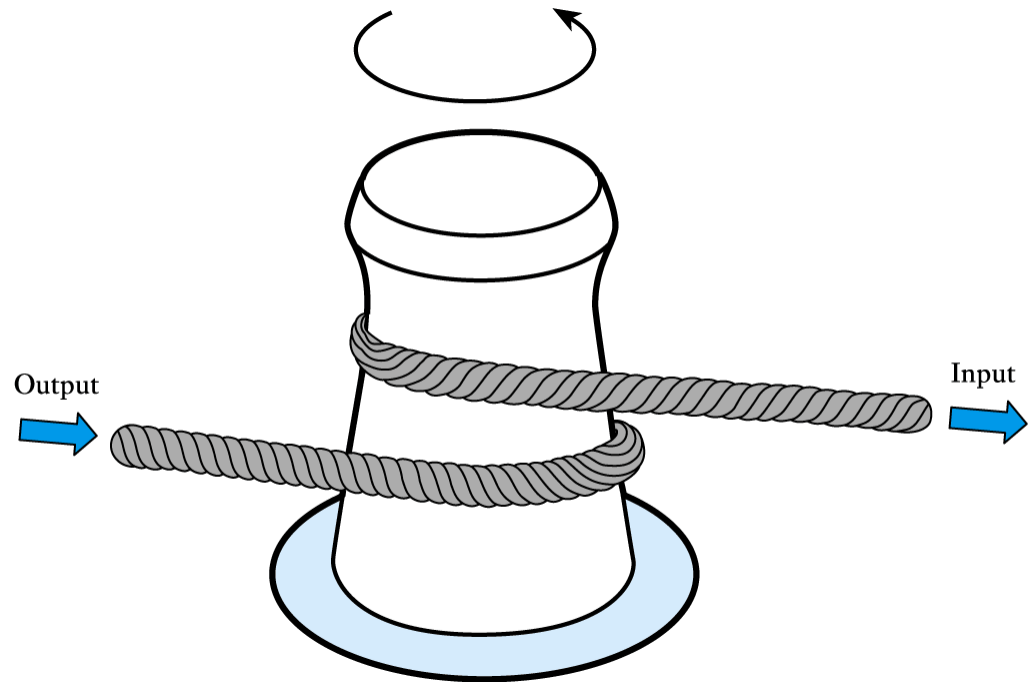- **Non-electronic active amplifiers**
 - an example is the torque amplifier shown here



A torque amplifier


Electronic amplifiers

- Can be passive (e.g. a transformer) but most are active
- We will concentrate on *active* electronic amplifiers
 - take power from a power supply
 - amplification described by gain

$$\text{Voltage Gain } (A_v) = \frac{V_o}{V_i}$$


$$\text{Current Gain } (A_i) = \frac{I_o}{I_i}$$
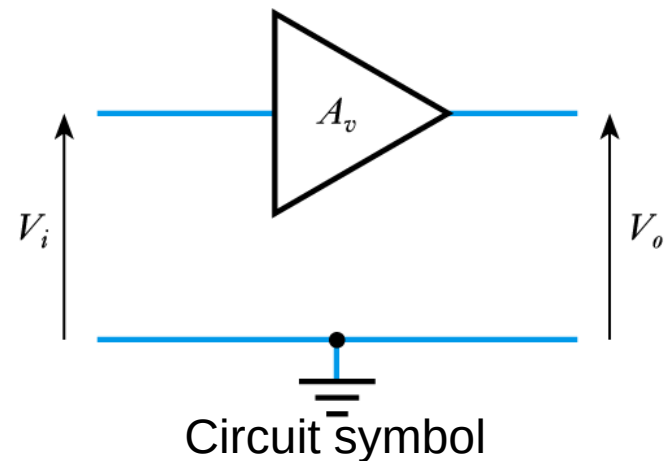
$$\text{Power Gain } (A_p) = \frac{P_o}{P_i}$$



Sources and loads

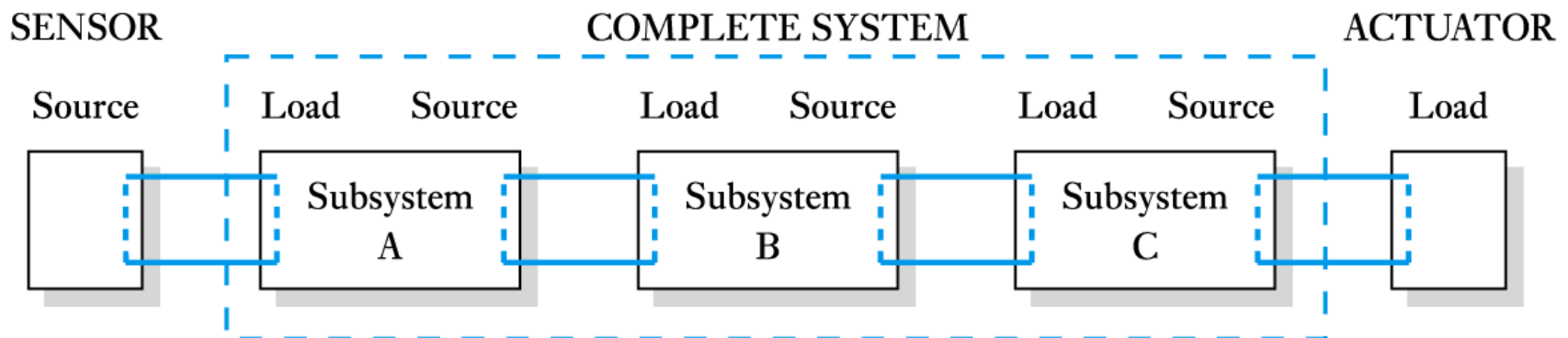
- An *ideal* voltage amplifier would produce an output determined only by the input voltage and its gain.
 - irrespective of the nature of the source and the load
 - in real amplifiers this is not the case
 - the output voltage is affected by **loading**.



Modelling sources and loads

- **Modelling the input of an amplifier**


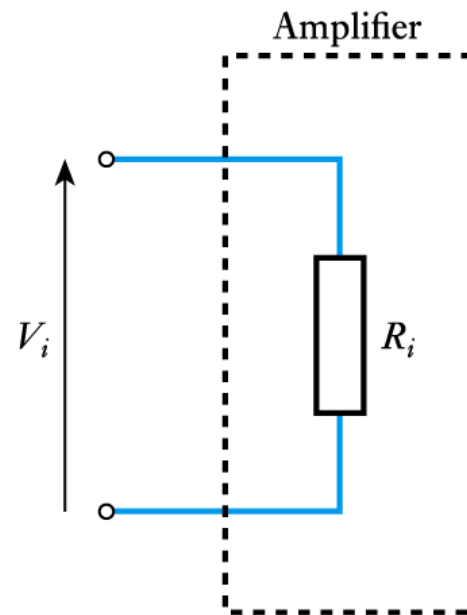
- the input can often be adequately modelled by a simple resistor
- the **input resistance**.



Modelling sources and loads (contd.)

■ Modelling the output of a circuit

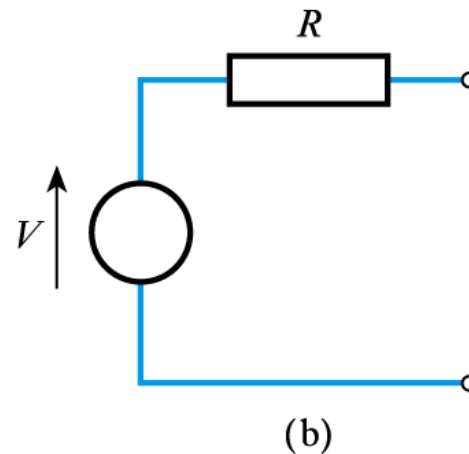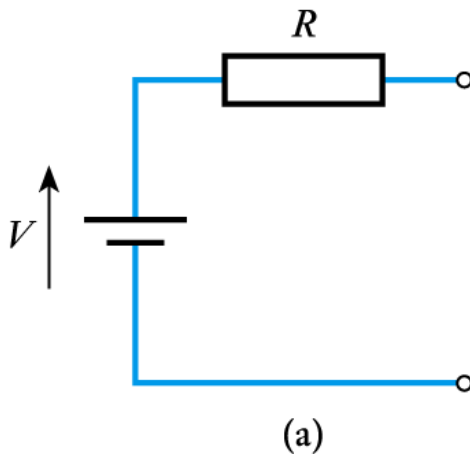
- all real voltage sources have an output resistance
- for example, a battery can be represented by an ideal voltage source and a series resistance representing its **output resistance**.



Modelling sources and loads (contd.)


■ Modelling the output of an amplifier

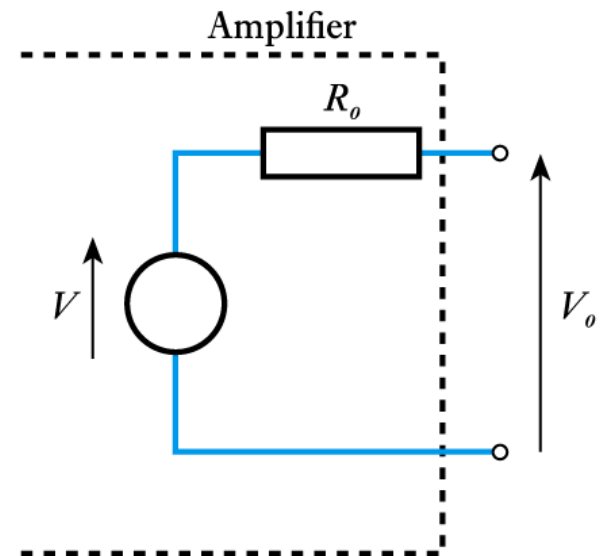- Similarly, the output of an amplifier can be modelled by an ideal voltage source and an output resistance.
- This is an example of a **Thévenin equivalent circuit** (we will return to such circuits later).




Modelling sources and loads (contd.)

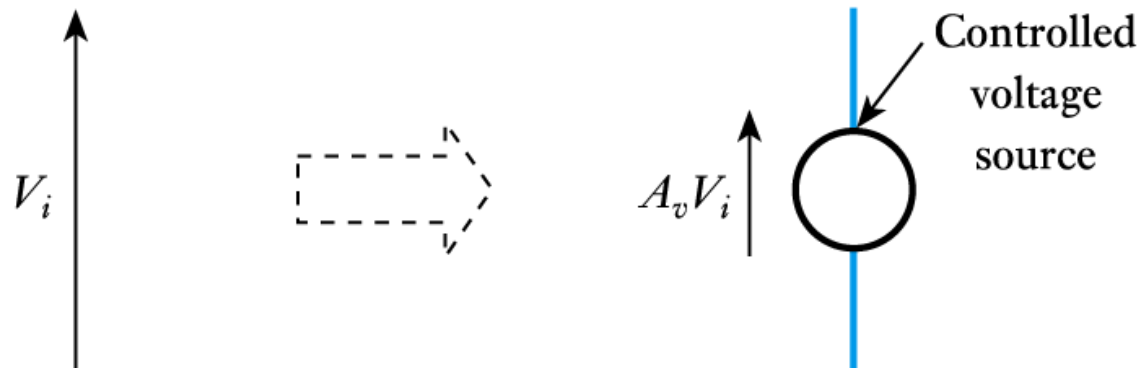- **Modelling the gain of an amplifier**
 - can be modelled by a controlled voltage source
 - the voltage produced by the source is determined by the input voltage to the circuit.



Equivalent circuits of amplifiers

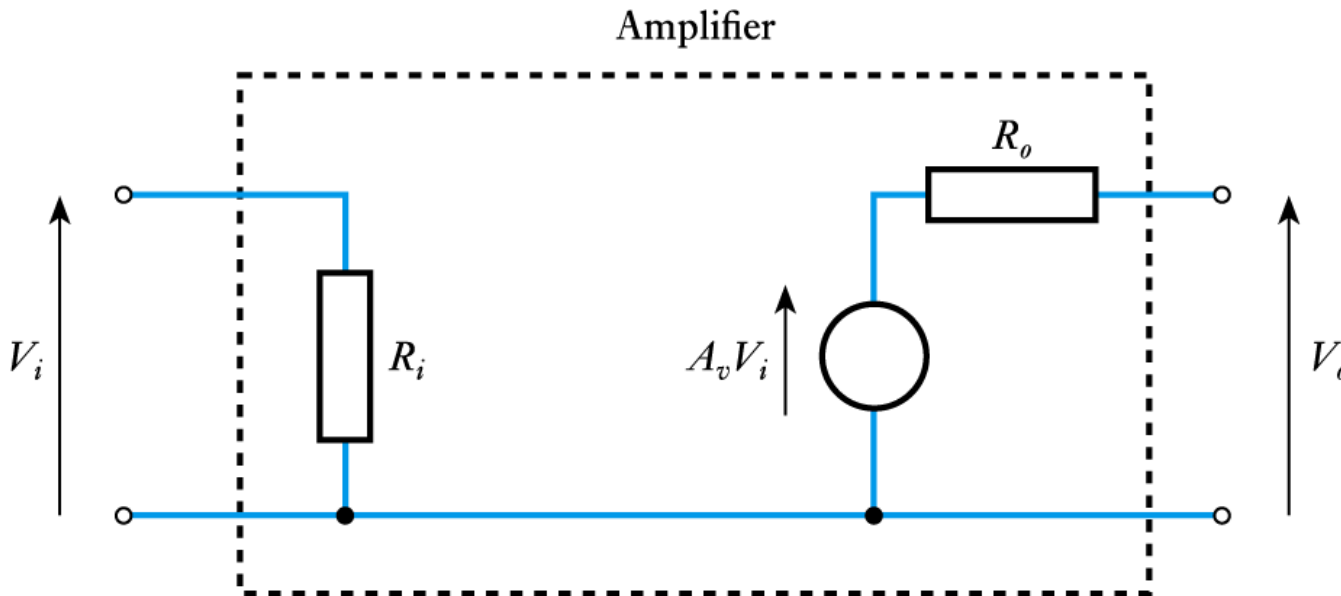- Having modelled the input, the output and the gain, we can now model the entire amplifier.




Equivalent circuits of amplifiers (contd.)

- **The use of an equivalent circuit**
(see **Example 3.1** in the course text):

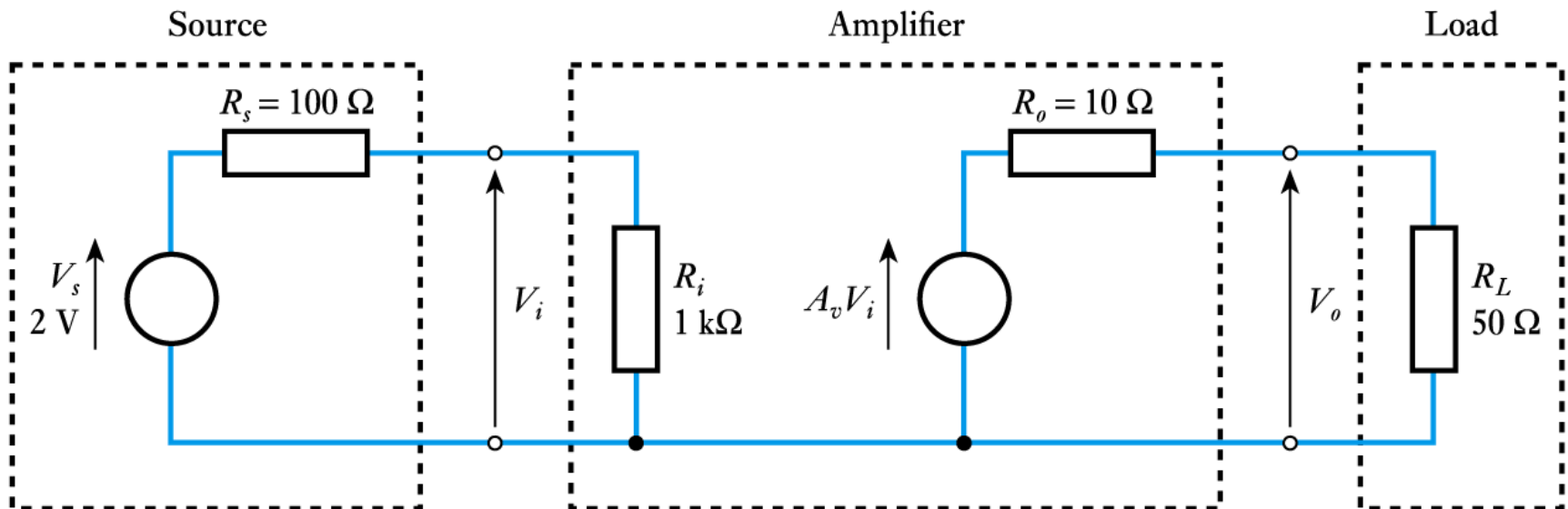Example: An amplifier has a voltage gain of 10, an input resistance of $1\text{ k}\Omega$ and an output resistance of $10\ \Omega$. The amplifier is connected to a sensor that produces a voltage of 2 V and has an output resistance of $100\ \Omega$, and to a load of $50\ \Omega$. What will be the output voltage of the amplifier (that is, the voltage across the load resistance)?

Equivalent circuits of amplifiers (contd.)

- We start by constructing an equivalent circuit of the amplifier, the source and the load.



Equivalent circuits of amplifiers (contd.)

- From this we can calculate the output voltage:

$$\begin{aligned} V_i &= \frac{R_i}{R_s + R_i} V_s \\ &= \frac{1\text{k}\Omega}{100\ \Omega + 1\text{k}\Omega} 2\text{ V} = 1.82\text{ V} \end{aligned}$$

$$\begin{aligned} V_o &= A_v V_i \frac{R_L}{R_o + R_L} \\ &= 10\ V_i \frac{50\ \Omega}{10\ \Omega + 50\ \Omega} \\ &= 10 \times 1.82 \frac{50\ \Omega}{10\ \Omega + 50\ \Omega} = 15.2\text{ V} \end{aligned}$$

Equivalent circuits of amplifiers (contd.)


- The **voltage gain** of the circuit in the previous example is given by:

$$\text{Voltage gain } (A_V) = \frac{V_o}{V_i} = \frac{15.2}{1.82} = 8.35$$

- note that this is considerably less than the stated gain of the amplifier (which is 10)
- this is due to **loading effects**
- the gain of the amplifier in isolation is its **unloaded voltage gain**.

Equivalent circuits of amplifiers (contd.)

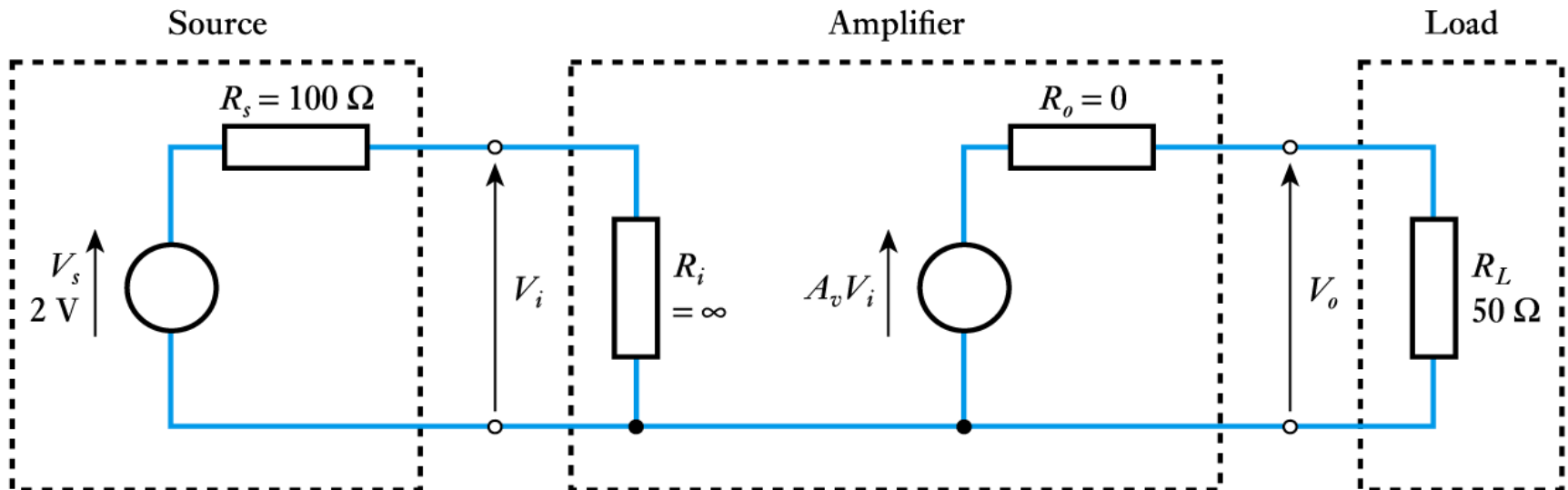- An **ideal voltage amplifier** would not suffer from loading
 - it would have $R_i = \infty$ and $R_o = 0$
 - consider the effect on the previous example.



Equivalent circuits of amplifiers (contd.)

- If $R_i = \infty$, then $\frac{R_i}{R_s + R_i} \approx \frac{R_i}{R_i} = 1$

- Therefore

$$V_i = \frac{R_i}{R_s + R_i} V_s \approx V_s = 2 \text{ V}$$

$$\begin{aligned} V_o &= A_v V_i \frac{R_L}{R_o + R_L} \\ &= 10 V_i \frac{50 \text{ } \Omega}{0 \text{ } \Omega + 50 \text{ } \Omega} \\ &= 10 \times 2 \frac{50 \text{ } \Omega}{50 \text{ } \Omega} = 20 \text{ V} \end{aligned}$$

– the effects of loading are removed (see **Example 3.3**).